
Clock and Data Recovery Architectures & Circuits


Pavan Hanumolu

hanumolu@illinois.edu


Dept. of Electrical and Computer Engineering
University of Illinois, Urbana-Champaign

Feb. 22, 2015


Serial Link Applications

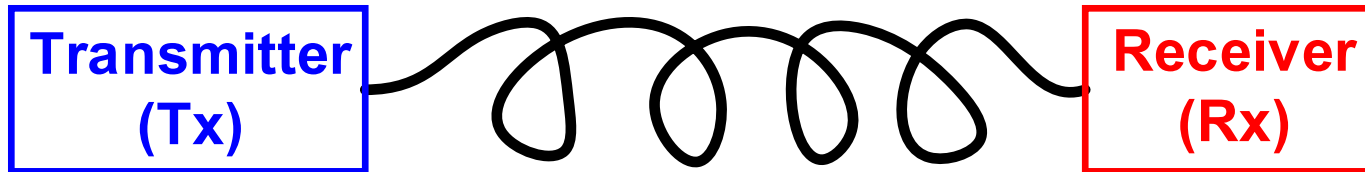


**Chip-to-chip
Electrical link**

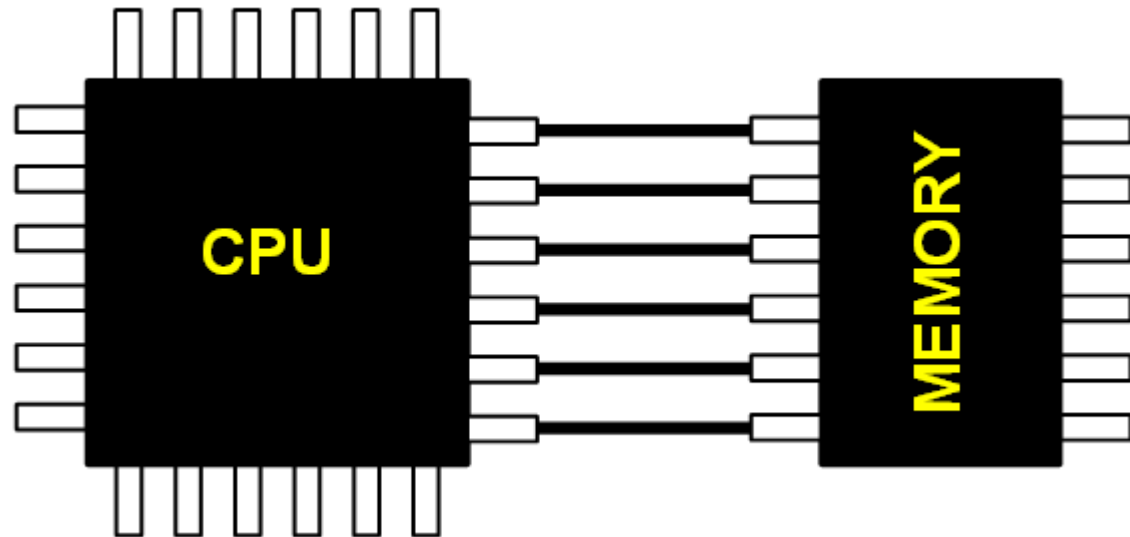

Optical link

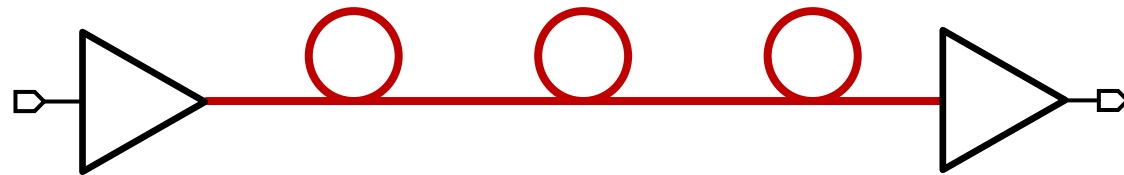

Serial Link Components

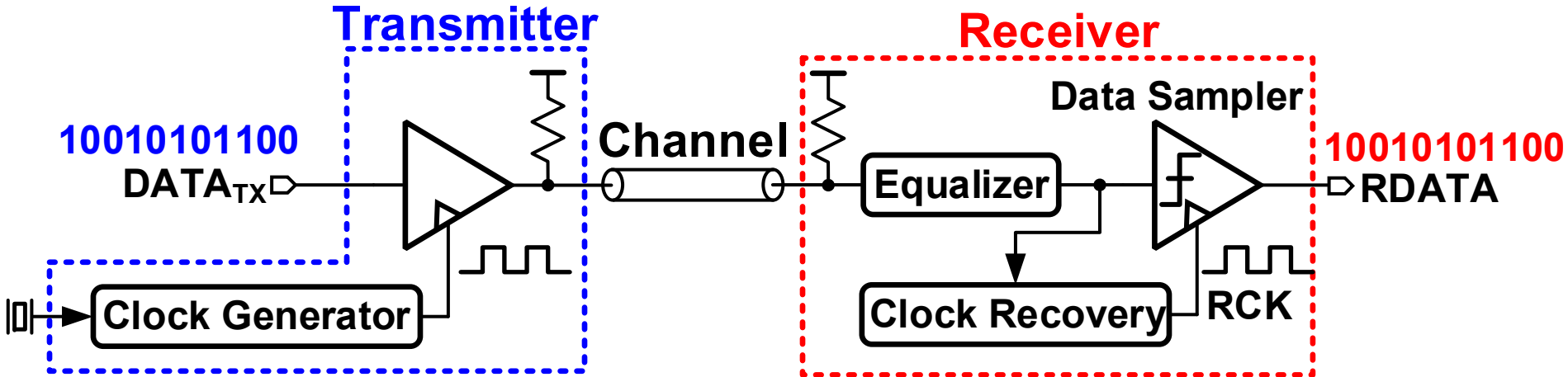


□ Transmitter

□ Channel


□ Receiver

□ Clock Recovery (CR) + Data sampler = CDR


Serial Link Waveforms

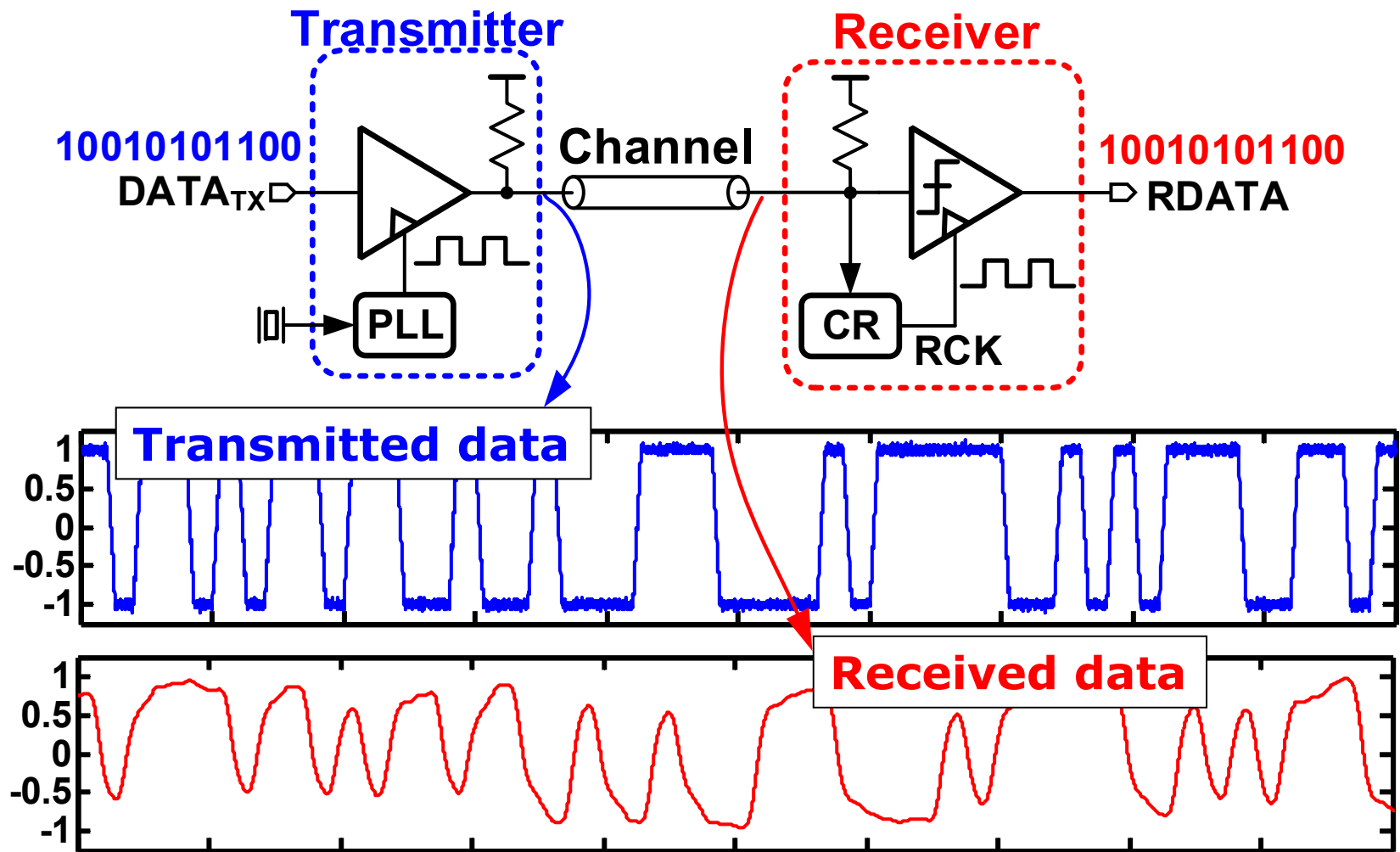


Serial Link Eye Diagrams

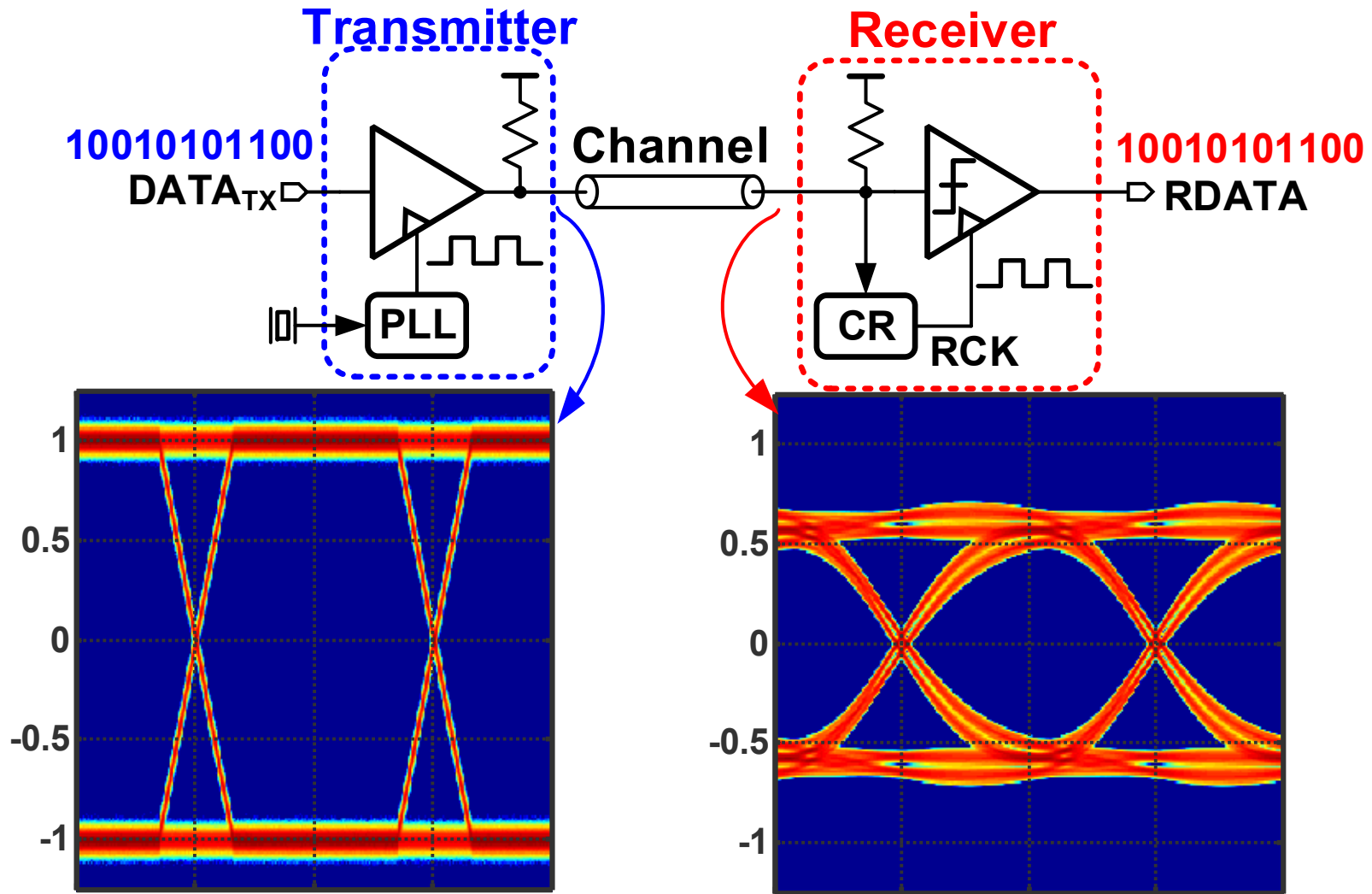

This Tutorial Focus: CDR

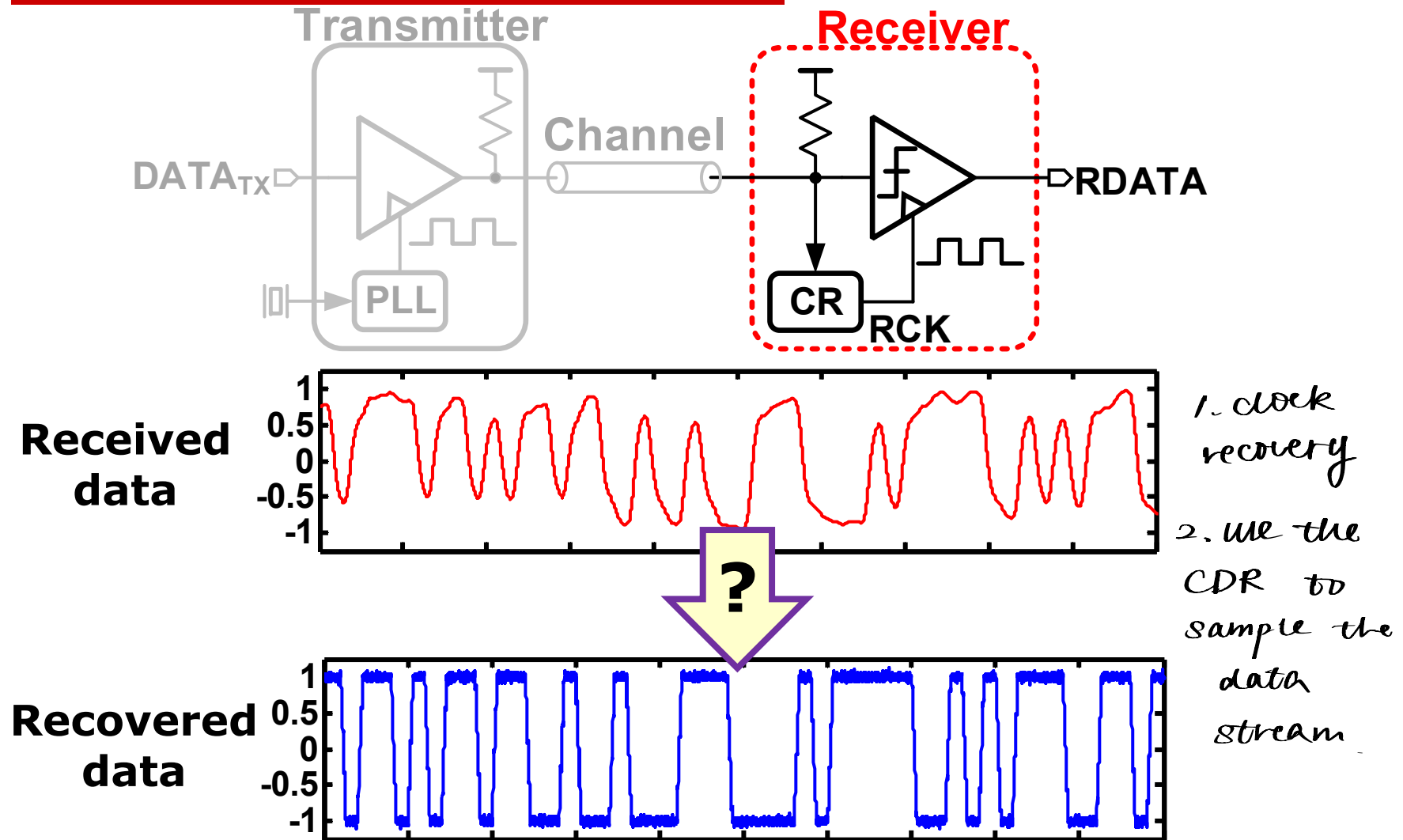

Tutorial Goals

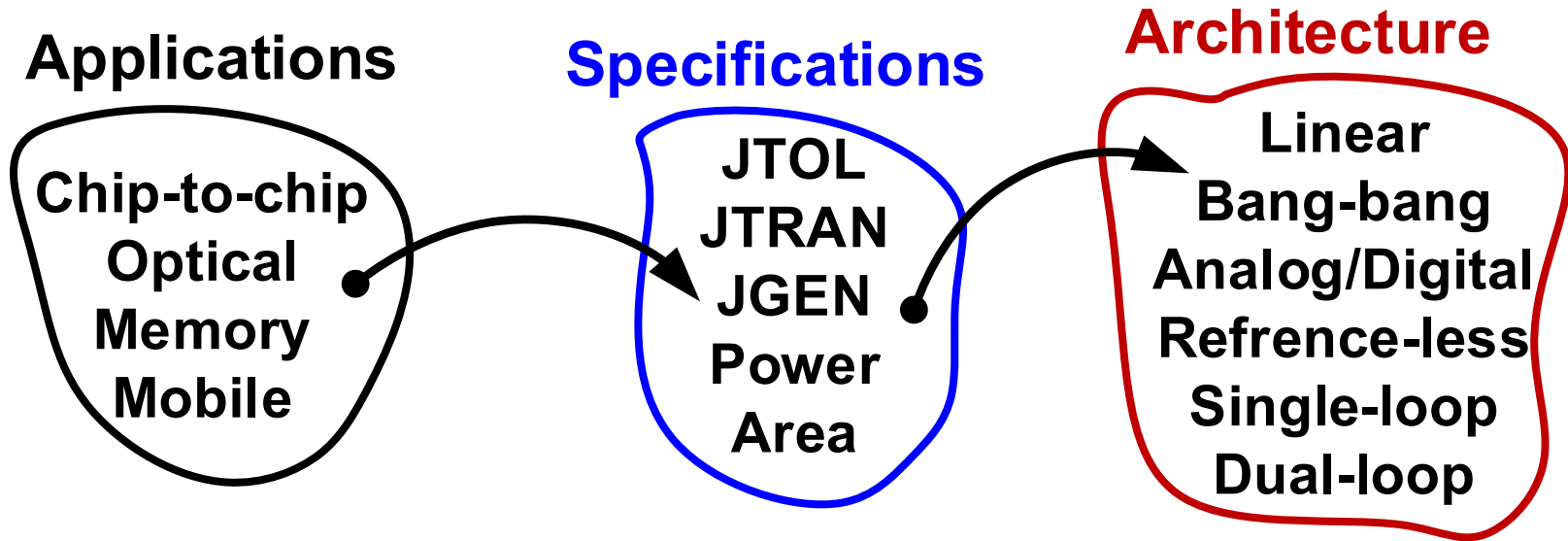

- ❑ Map application requirements to CDR specifications
- ❑ Optimal architecture choice based on CDR specs.
 - Exposure to different CDR architectures
 - Develop intuition for design tradeoffs
 - Awareness to practical considerations

Tutorial Roadmap

- Performance metrics *unique to CDR*
 - Basic architectures
 - Linear/Bang-bang
 - Digital
 - Hybrid
 - Application-specific CDRs
 - Multi-lane chip-to-chip links
 - Repeaters for optical links and active cables
 - Summary
-

CDR Performance Metrics

- ❑ Jitter tolerance (JTOL)
- ❑ Jitter generation (JGEN)
- ❑ Jitter transfer (JTRAN)

Jitter metrics

Scalability


Power

CDR

Supply noise sensitivity

Area

Operating range


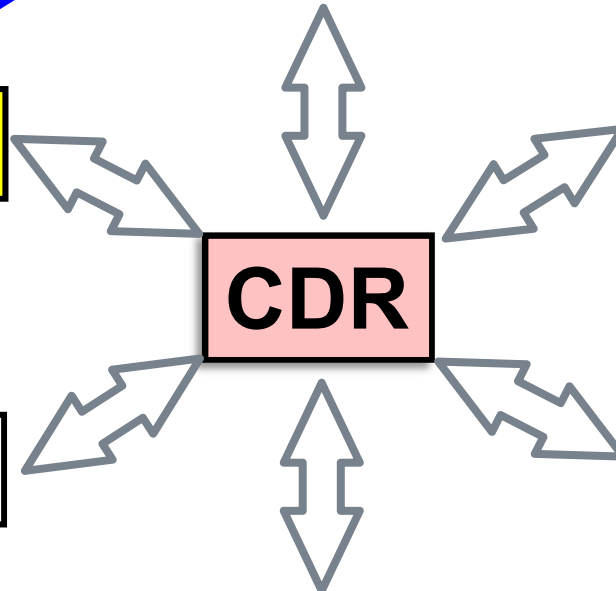


Jitter Tolerance (JTOL)


- Maximum tolerable input jitter for a given BER

$$\text{BER} = \frac{\text{Number of bit errors}}{\text{Number of transmitted bits}}$$

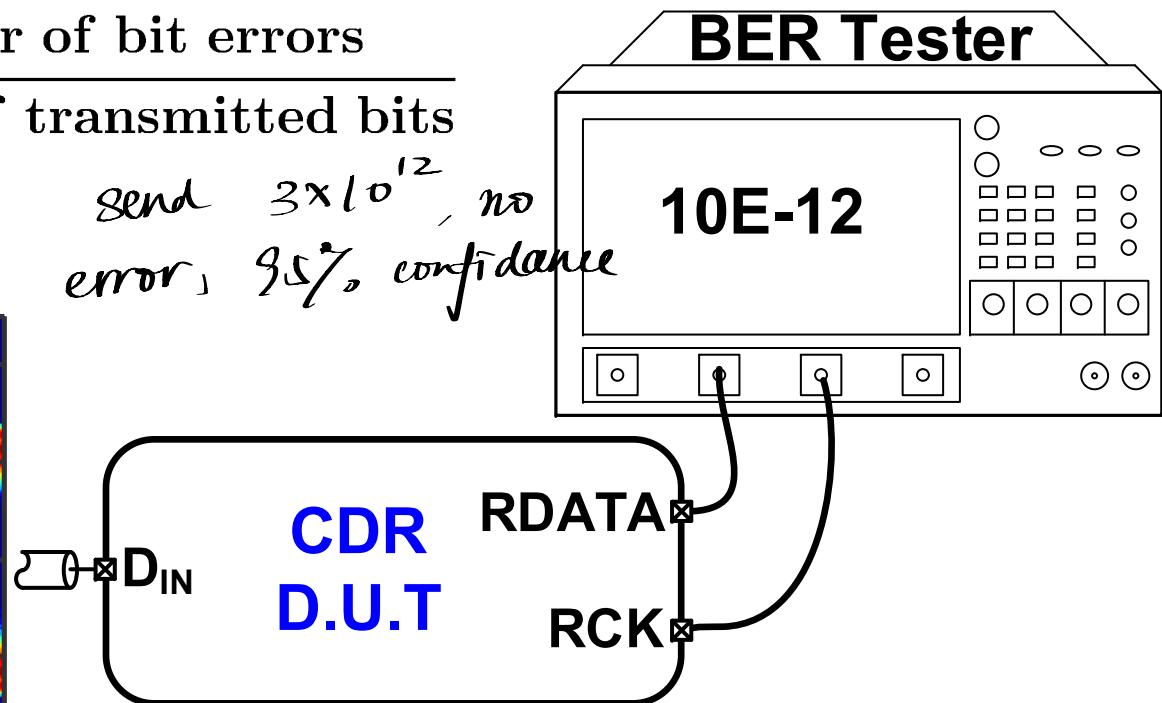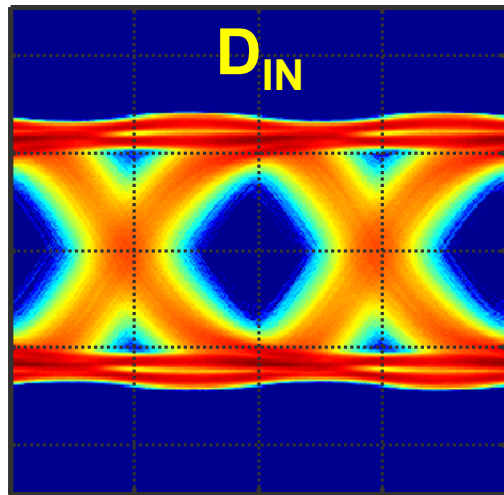send 3×10^{12} , no error, 95% confidence




JTOL Mask

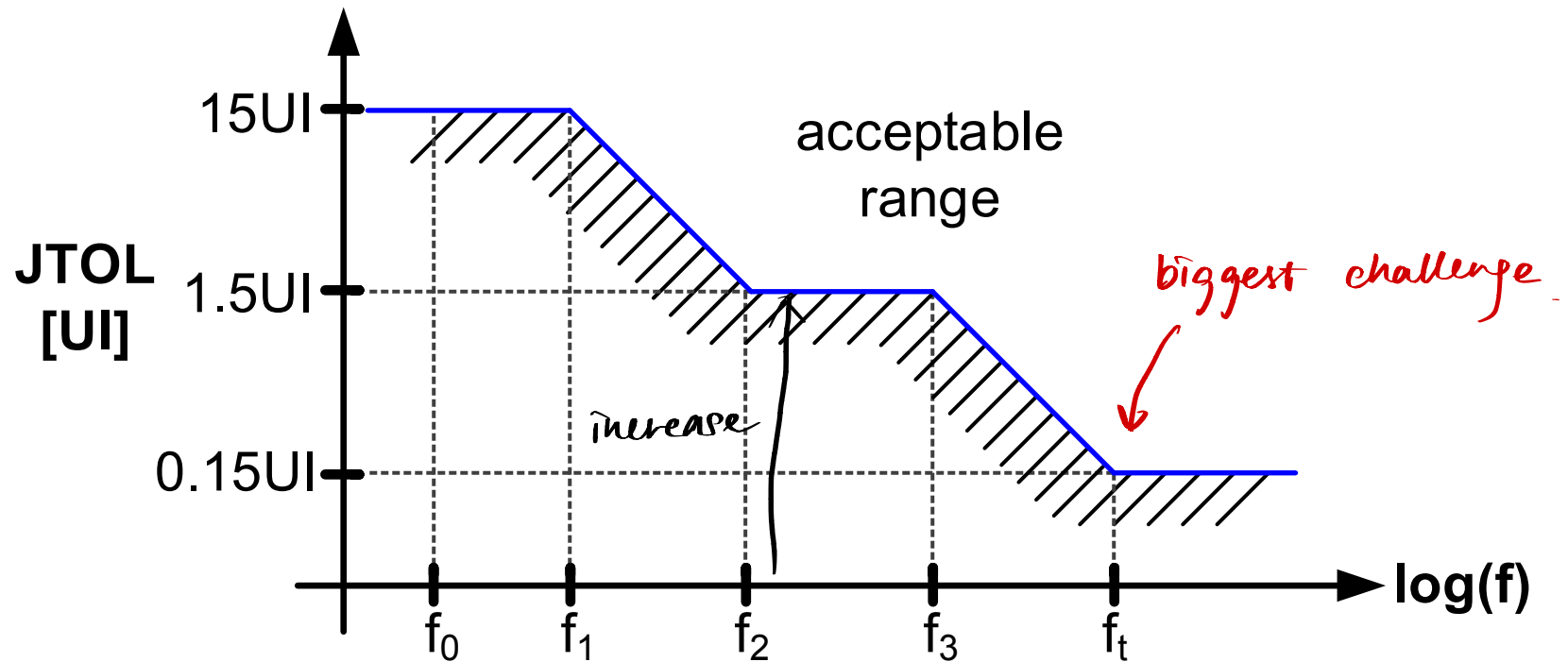


- Increase data input sinusoidal jitter until BER exceeds target

Jitter Transfer (JTRAN)

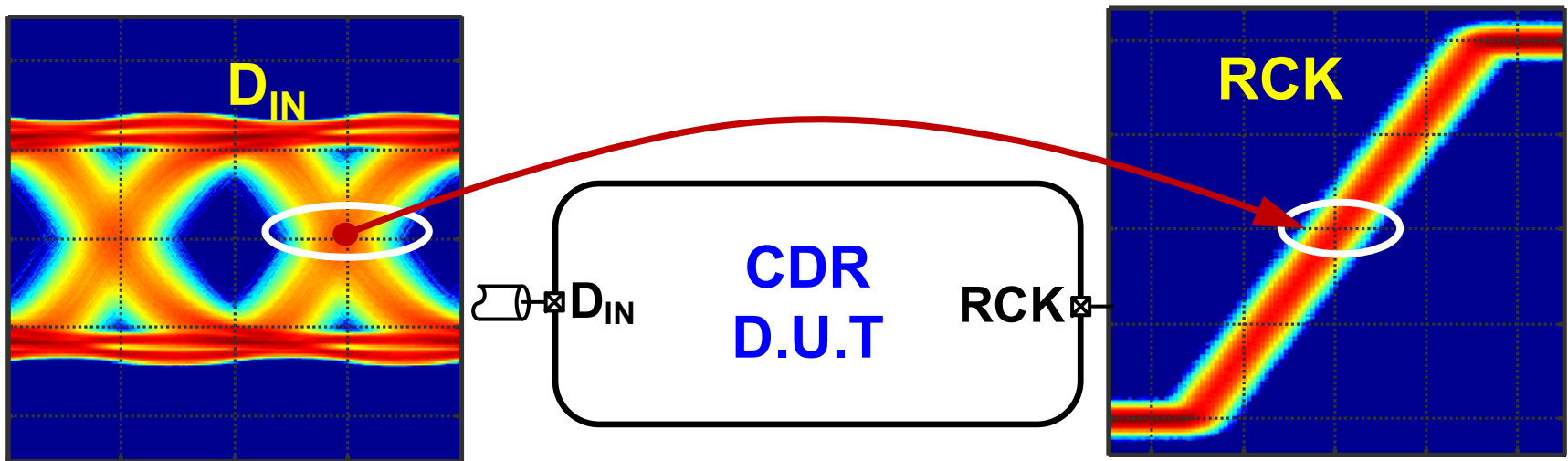- Amount of jitter attenuation provided by CDR



JTRAN Mask

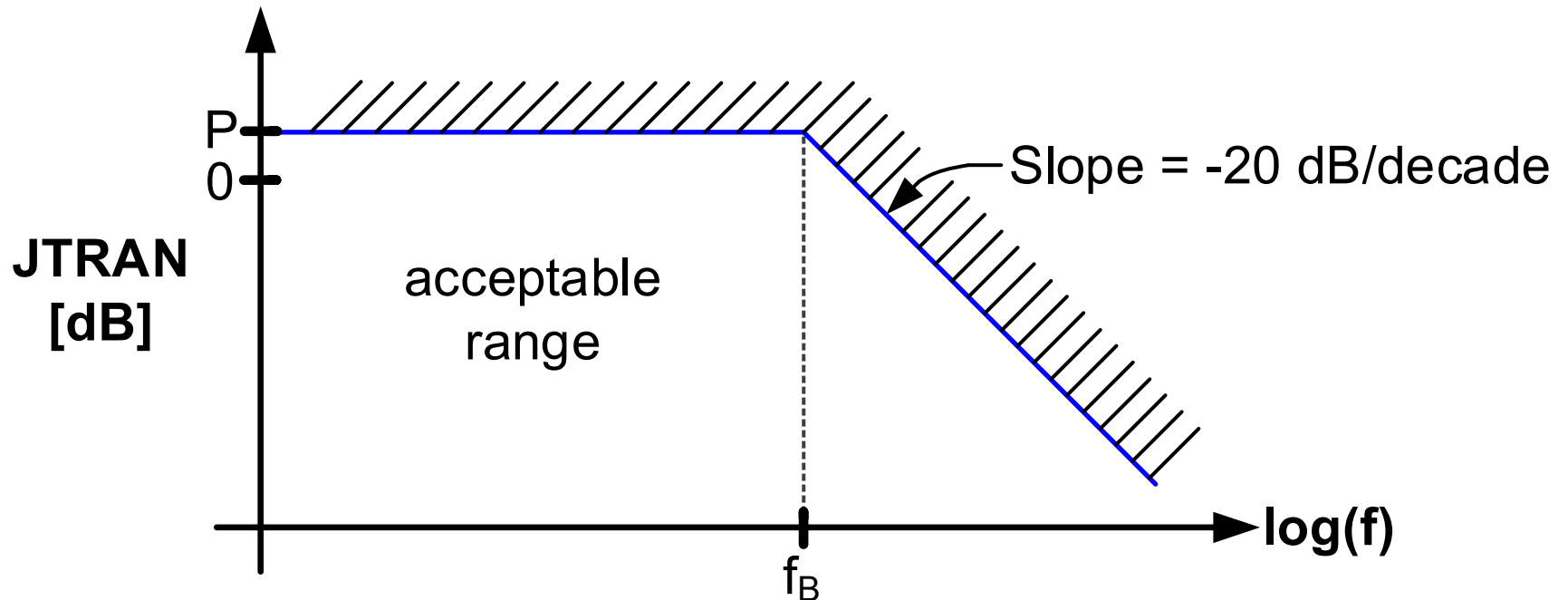


- Modulate data input with sinusoidal jitter and measure resulting output jitter

Jitter Generation (JGEN)

- Amount of output jitter when fed with clean data

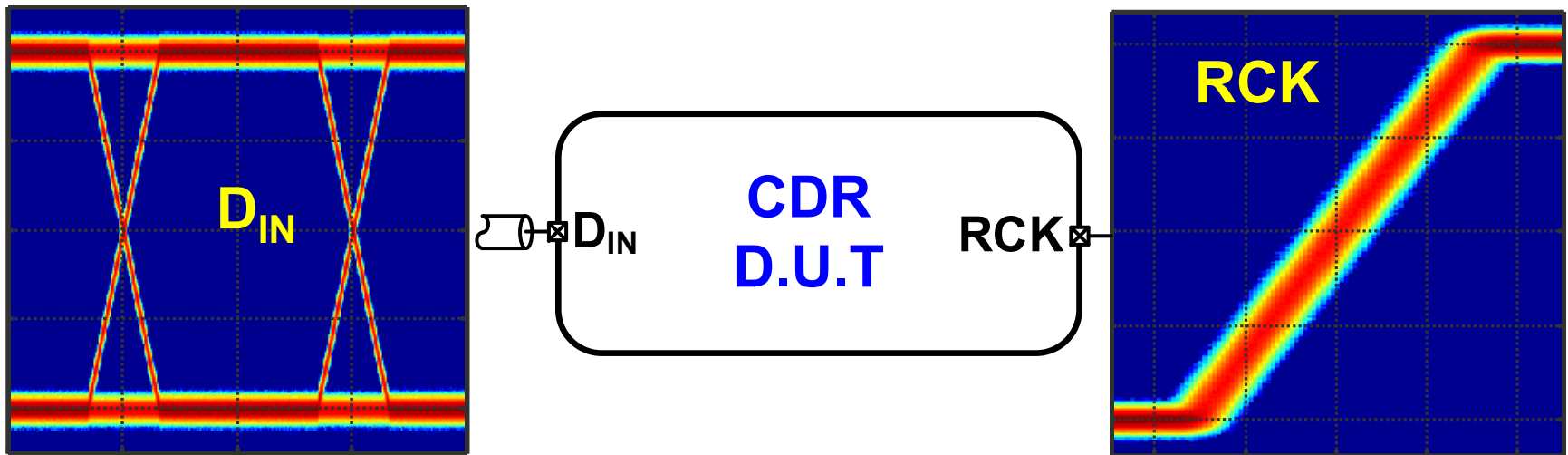
How does jitter getting generated by CDR w/ clean input



Tutorial Roadmap

- Performance metrics
 - **Basic architectures**
 - **Linear/Bang-bang**
 - **Digital**
 - **Hybrid**
 - Application-specific CDRs
 - Multi-lane chip-to-chip links
 - Repeaters for optical links and active cables
 - Summary
-

Phase-Locked Loop based CDR

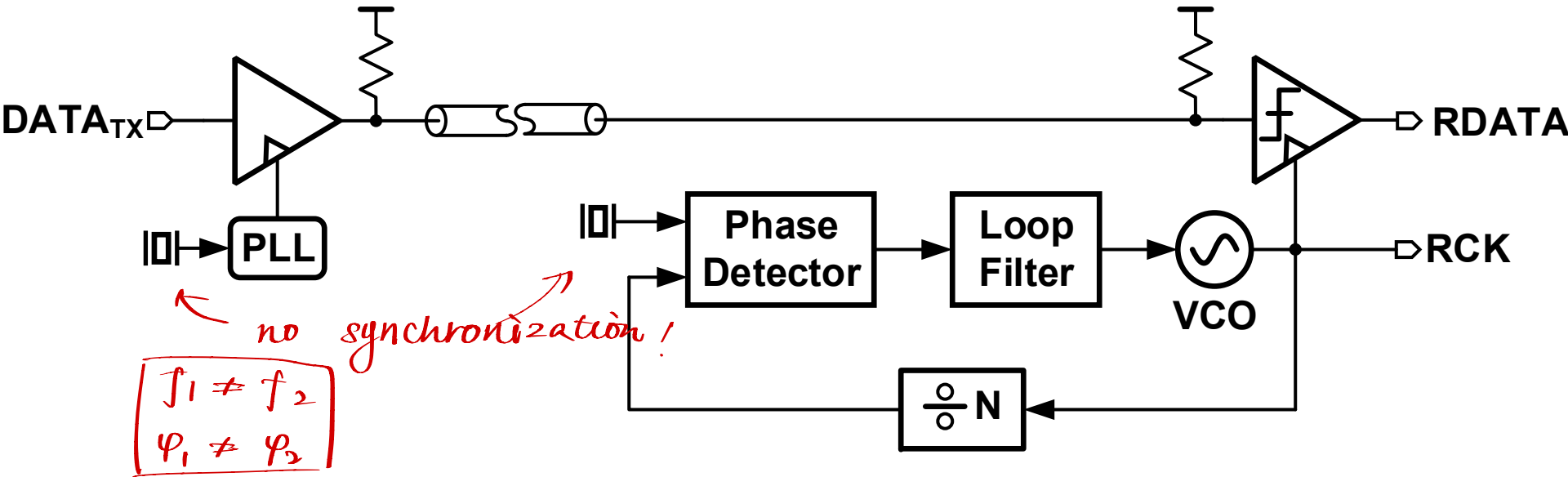


❑ This **WON'T work** because:

- Crystal oscillators at TX and RX do not match
- No phase relationship between received data and RCK


❑ **Need:** Acquire freq. & phase information from data

PLL-based CDR

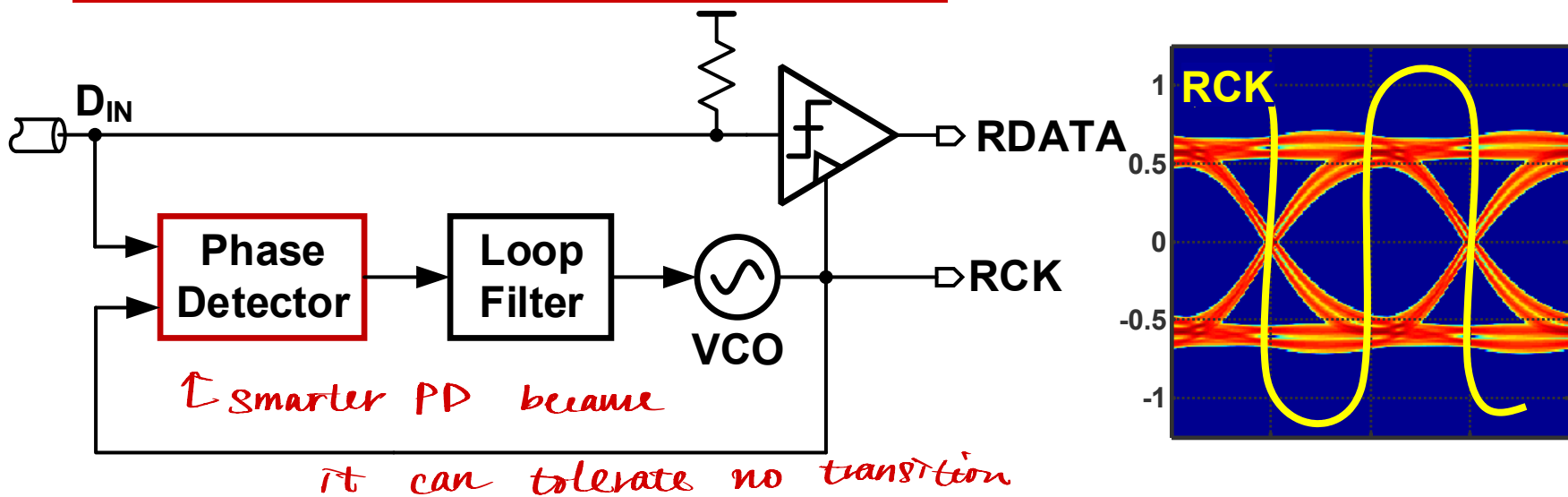

- ❑ Phase detector should tolerate missing transitions
- ❑ Rest of the building blocks similar to a PLL
- ❑ Neg. edge of recovered clock locks to data edge
- ❑ Pos. edge samples data in the middle of the eye



Linear (Hogge) Phase Detector^[1]

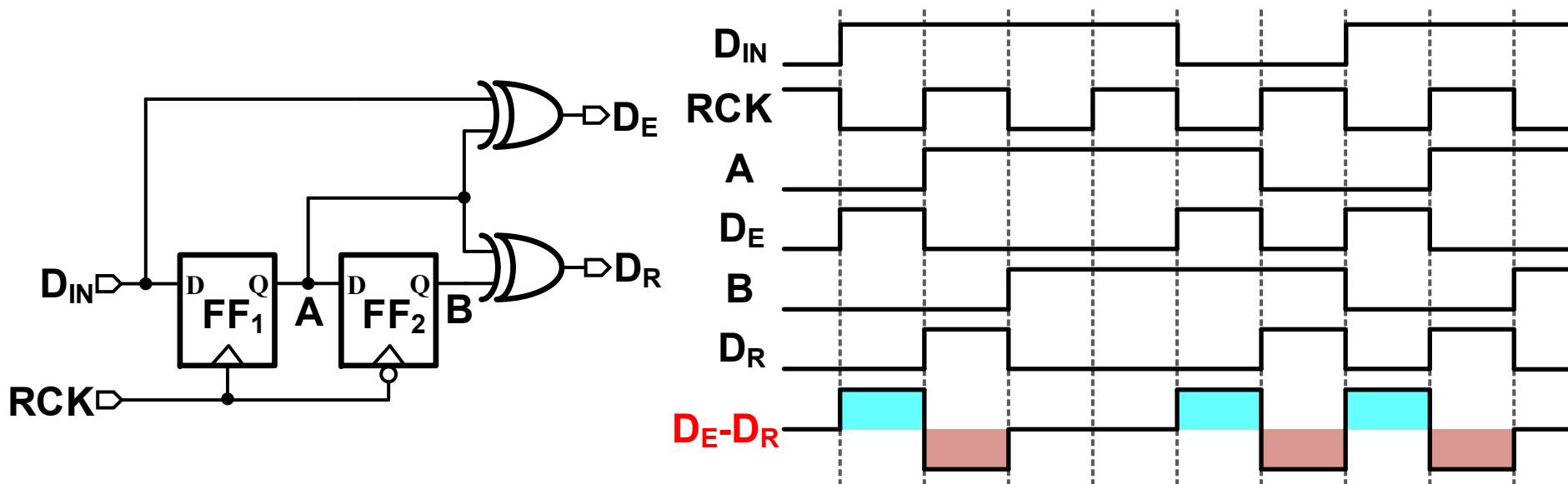

- Error output ($D_E - D_R$) is difference of 2 pulses
 - Pulse width of D_E is proportional to phase error
 - Pulse width of D_R is fixed and is equal to $T_{RCK}/2$
- Area under $D_E - D_R$ is proportional to phase error
 - Area is zero when RCK is aligned with D_{IN}


*when there is a transition, D_E pulses $\Delta\phi$, D_R pulses $\frac{T}{2}$.
They are quite if no transition presents. Compare D_E to D_R.*

Hogge PD Waveforms

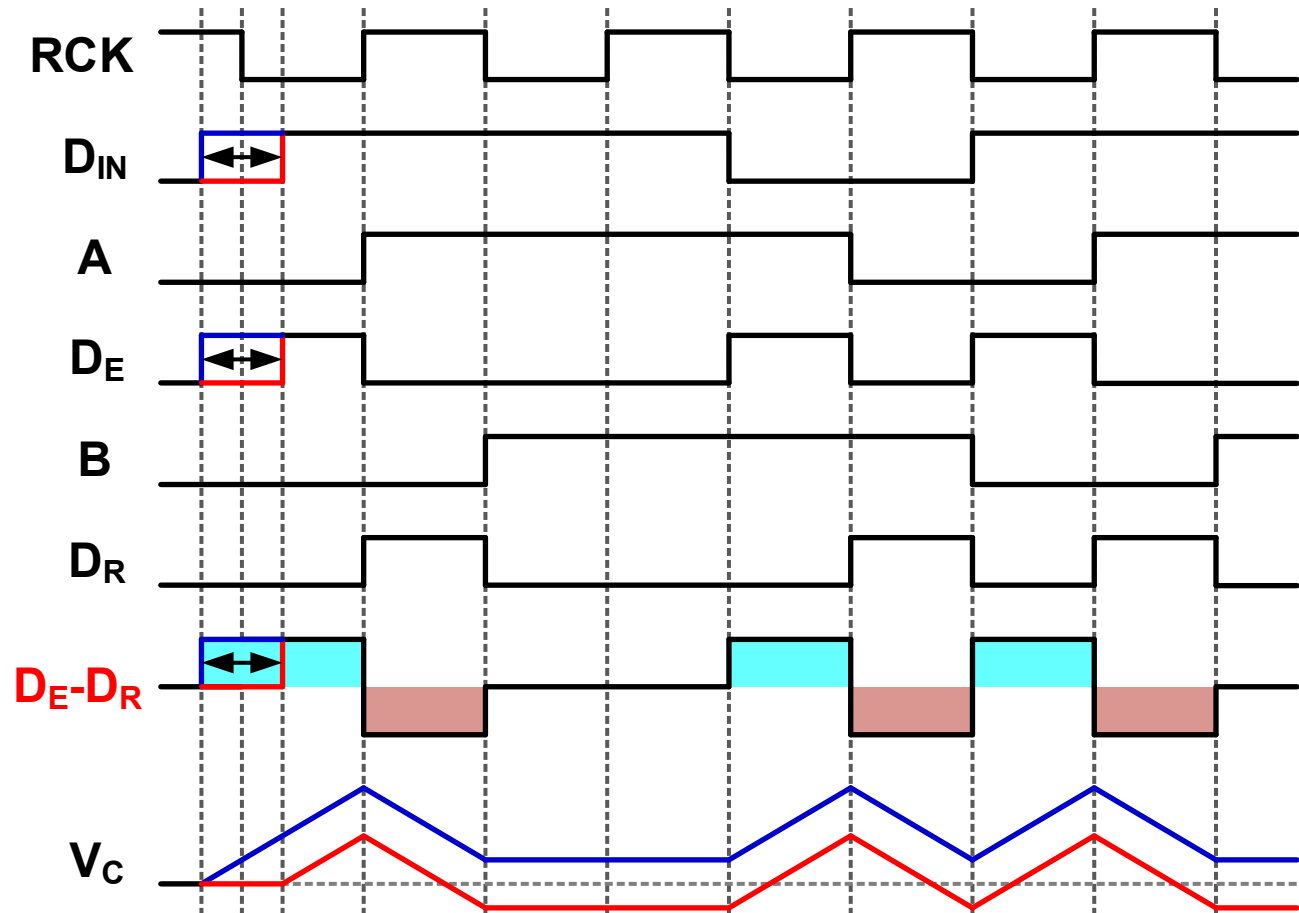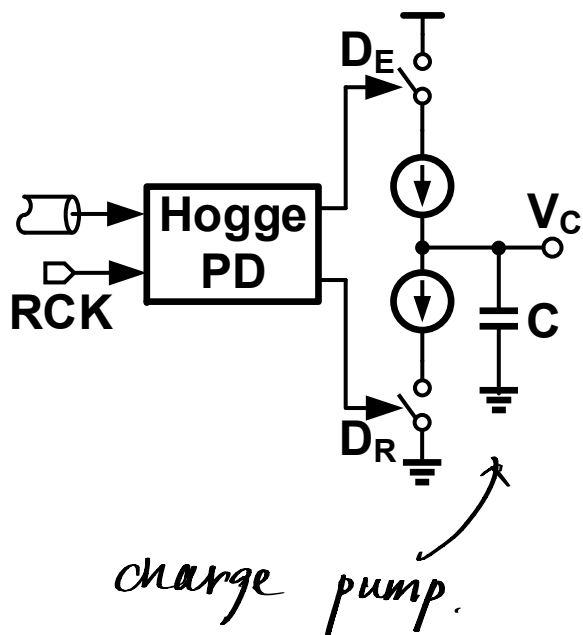


Hogge PD Transfer Function

Average Phase Detector Output

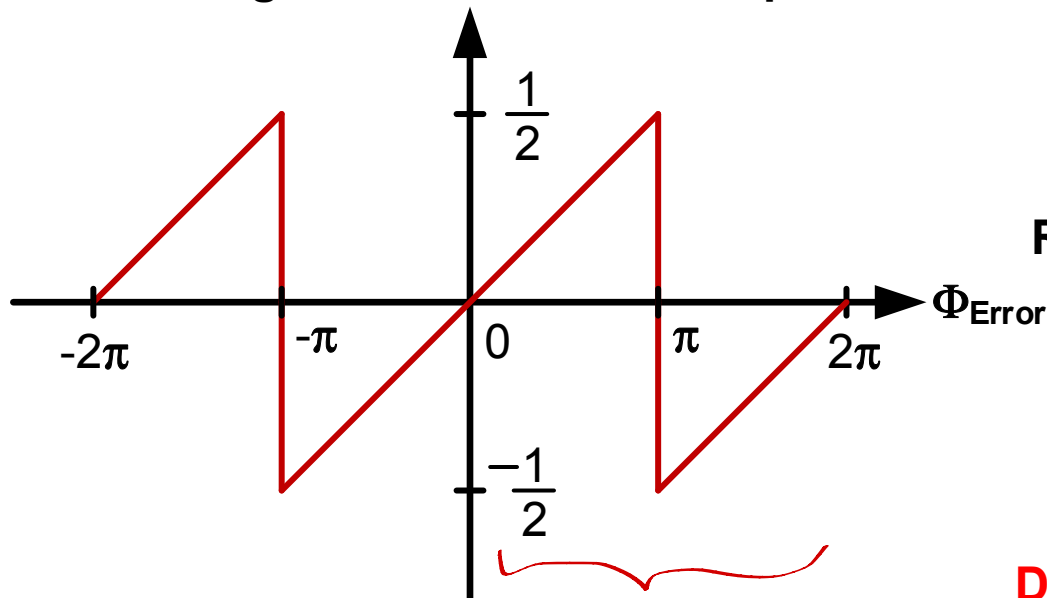


Linear range : $\pm\pi$
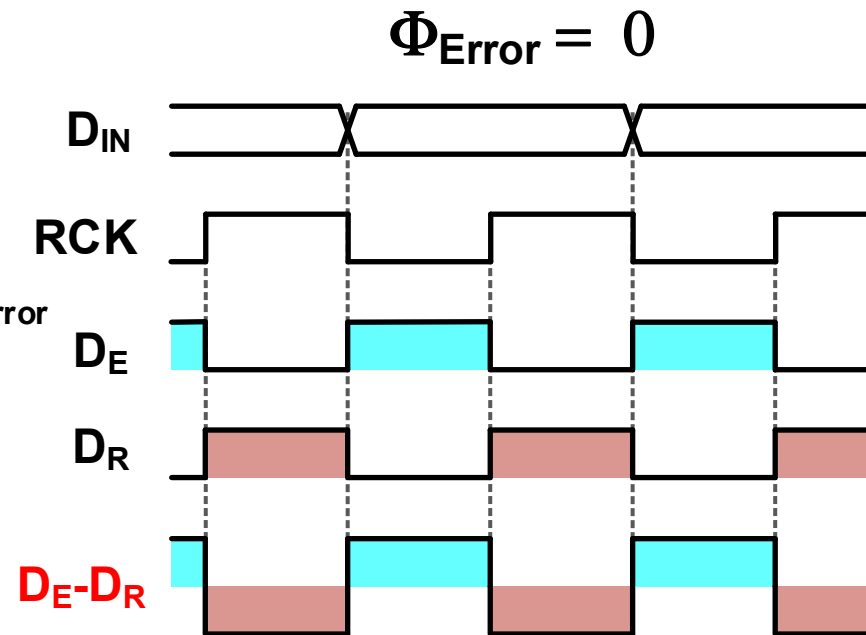
$$\text{Gain } K_{\text{pd}} = \frac{1}{2\pi}$$



when $\Phi_{\text{ERROR}} \neq 0$ because
 $\exists \Delta f$, Hogge PD is not a
 frequency detector.

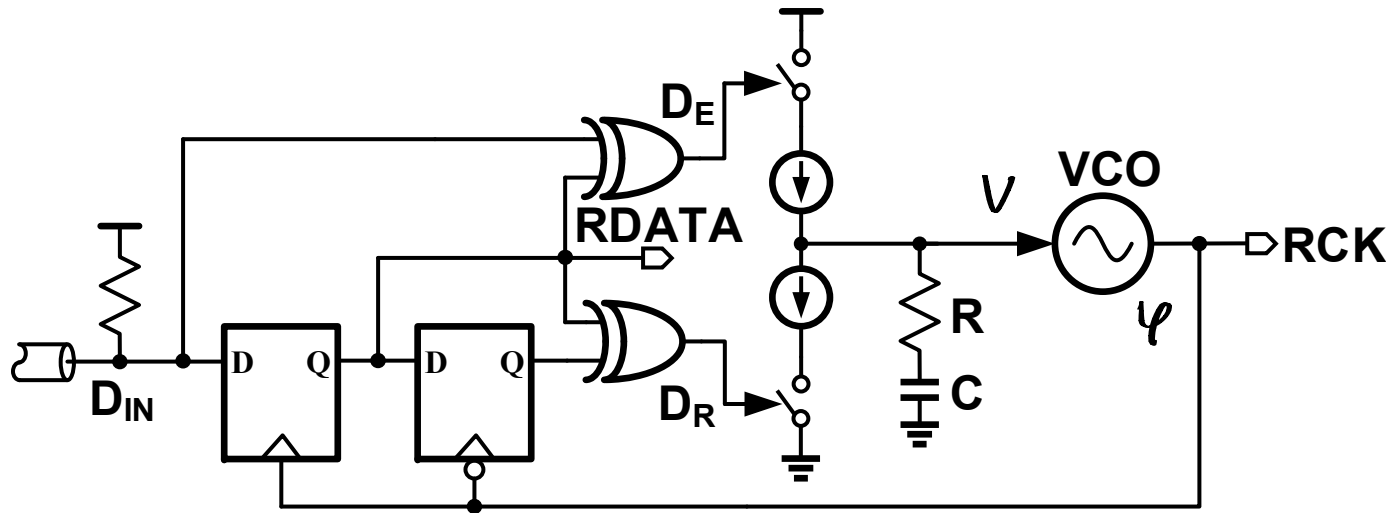[illegible]

□ Type-II response

- 2 integrators – one in the loop filter and the other is VCO


- ❑ Zero static phase offset (ideally)

- CP output should be zero in steady state
- Implies input phase error = 0

most CDR is type 2 because we don't tolerate $\Delta\varphi$

b/w data & clock $\leftarrow$ in the middle of the eye.

Choosing Loop Parameters

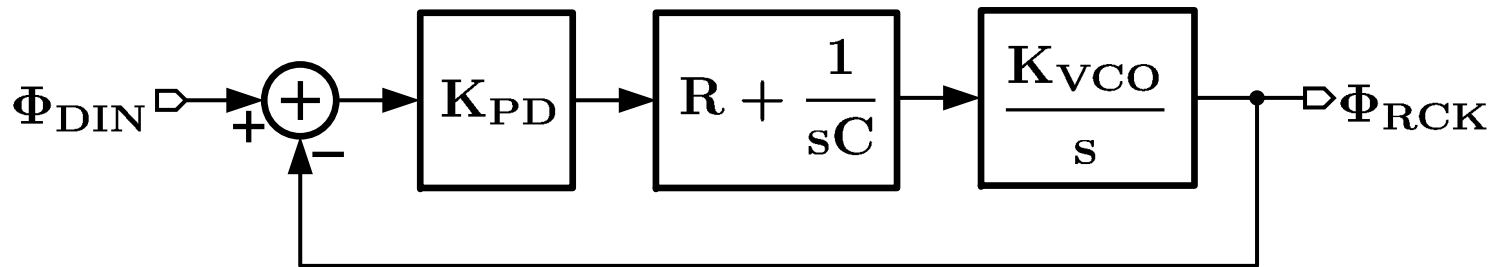


$$LG(s) = K_{PD} \cdot \left(R + \frac{1}{sC} \right) \cdot \frac{K_{VCO}}{s}$$


$$\omega_z = \frac{1}{RC}, \quad \omega_{p1} = 0, \quad \omega_{p2} = 0$$

$R \sim \text{few } k\Omega s$,
JTRAN BW $\approx \omega_{ugf}$ *unit gain freq*,
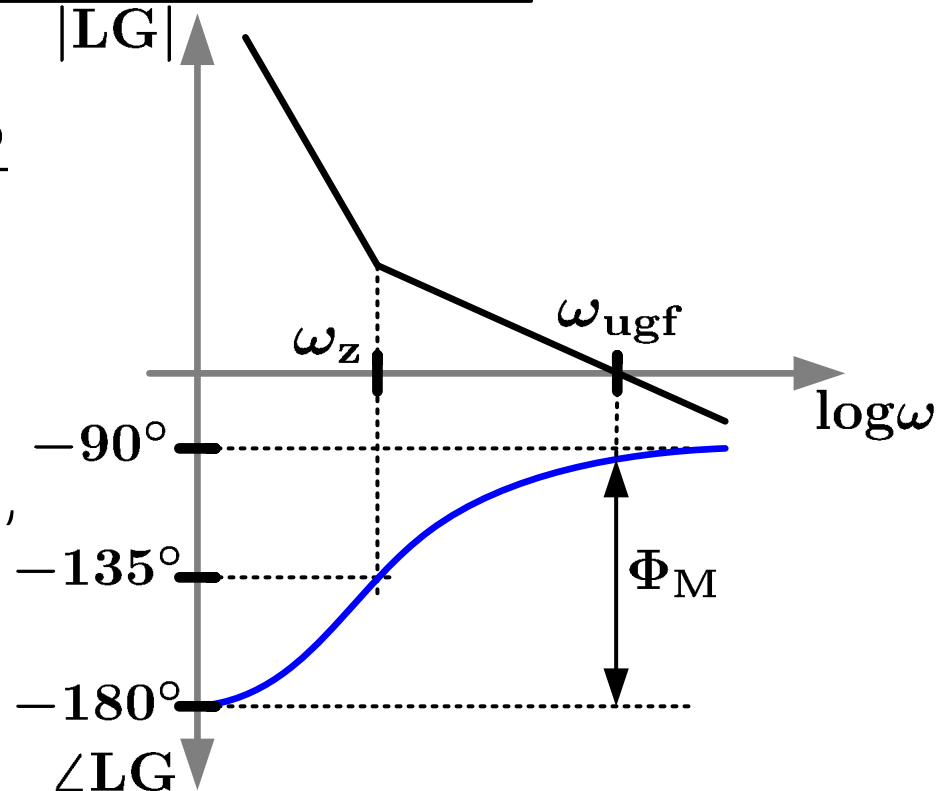
$$\Phi_M = \arctan \left(\frac{\omega_{ugf}}{\omega_z} \right)$$



Jitter Transfer Function *Mason's Rule*

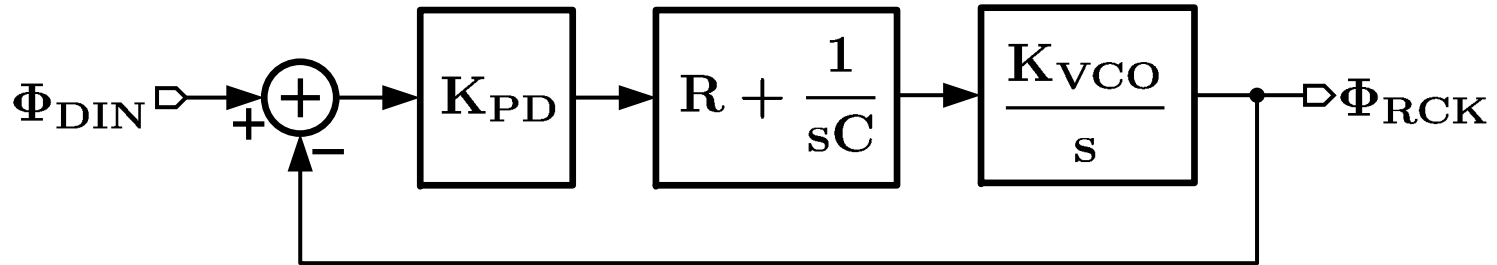

$$\begin{aligned}
 H_{\text{JTRAN}}(s) &= \frac{\Phi_{\text{RCK}}(s)}{\Phi_{\text{DIN}}(s)} = \frac{\text{FPG}(s)}{1 + \text{LG}(s)} \\
 &= \frac{1 + sRC}{1 + sRC + s^2 \cdot \frac{C}{K_{\text{VCO}}K_{\text{PD}}}} \\
 &\equiv \frac{1 + s/\omega_z}{(1 + s/\omega_{\text{PL}})(1 + s/\omega_{\text{PH}})}
 \end{aligned}$$


usually $\omega_z \sim \omega_{\text{PL}}$

$\omega_z = 1/RC$
 $\omega_{\text{PL}} \approx 1/RC$
 $\omega_{\text{PH}} \approx K_{\text{VCO}} \cdot K_{\text{PD}} \cdot R$

JTRAN BW = $\omega_{-3\text{dB}} \approx \omega_{\text{PH}} \approx K_{\text{VCO}} \cdot K_{\text{PD}} \cdot R$

• *usually overdamped.*

Linear CDR Drawbacks

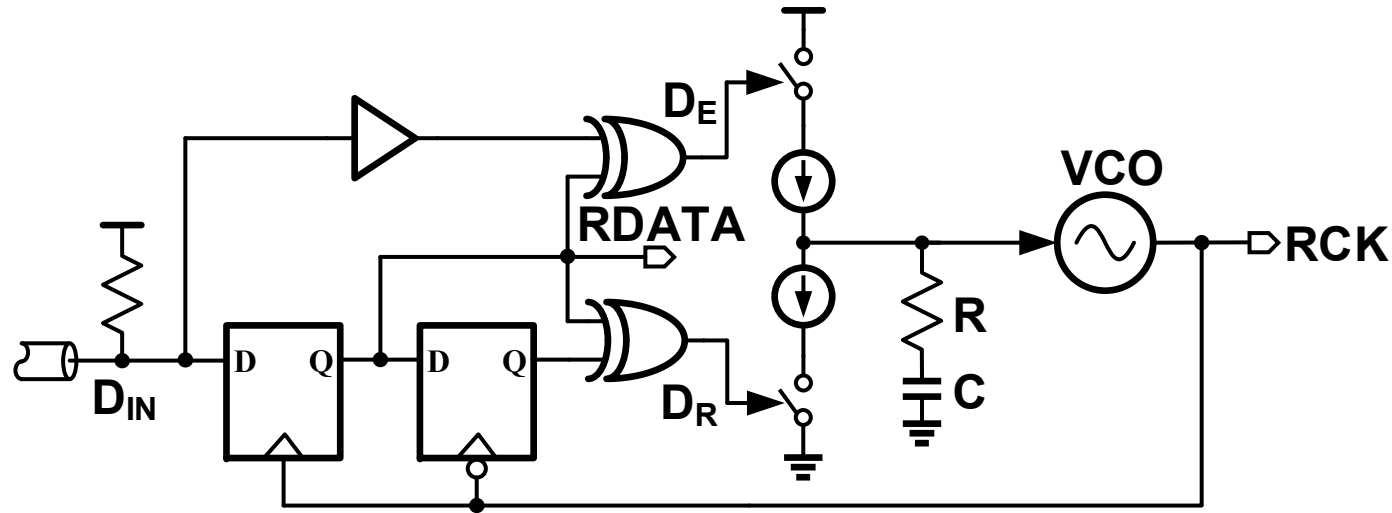

- ❑ Jitter peaking (large loop filter area)
- ❑ Coupled JTRAN and JTOL
can't choose one over another
- ❑ Hogge PD non-idealities

Jitter Peaking (I)

□ Zero in feed-forward path → inevitable peaking


$$H_{JTRAN}(s) = \frac{1 + sRC}{1 + sRC + s^2 \cdot \frac{C}{K_{VCO}K_{PD}}}$$

ω_z has to be
less than $\omega_{p1,2}$.

$$\omega_z = 1/RC$$

$$\omega_{PL} \approx 1/RC$$
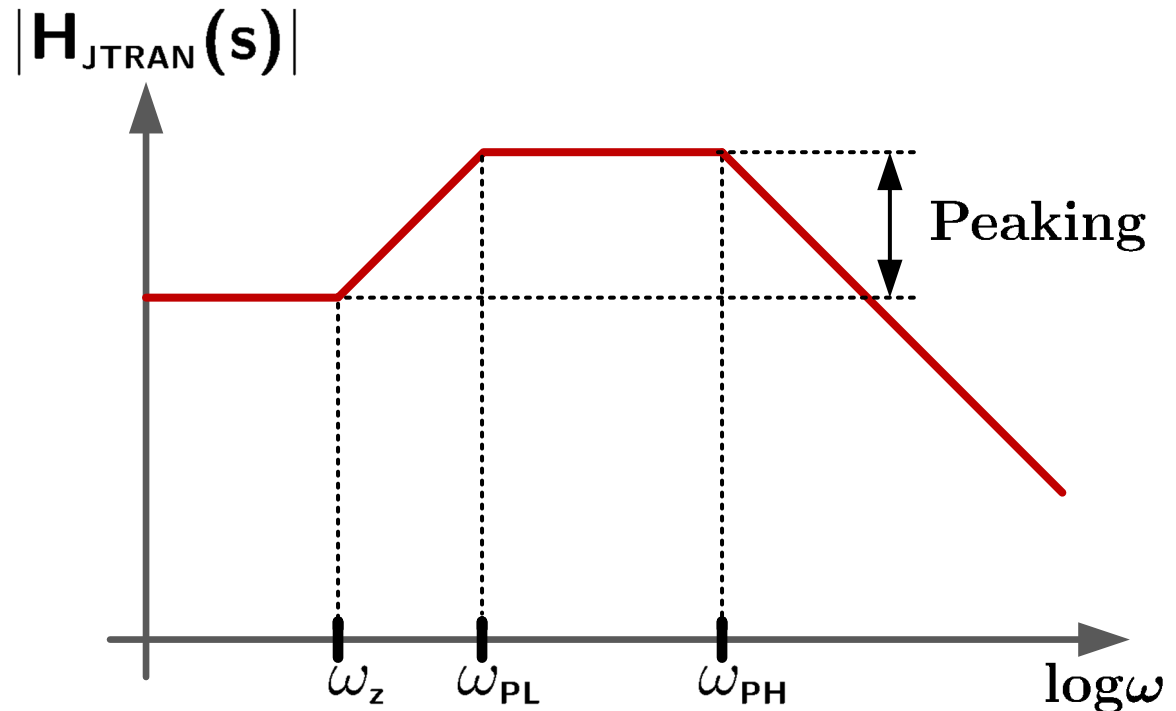
$$\omega_{PH} \approx K_{VCO} \cdot K_{PD} \cdot R$$



• Assume the system is like $H(s) = \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

Then the system has $\omega_z = -\frac{\omega_n}{2\zeta} = -\frac{1}{RC}$

and $\omega_{p_{1,2}} = (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n$

• If $\zeta = 1$, then $\omega_{p_1} = \omega_{p_2} = -\omega_n$ where $|\omega_{p_1}| > |\omega_z|$.

• If $\zeta \gg 1$, then $\sqrt{\zeta^2 - 1} \approx \zeta(1 - \frac{1}{2\zeta^2}) = \zeta - \frac{1}{2\zeta}$, and

• $\omega_{p_1} \approx (-\zeta + \zeta - \frac{1}{2\zeta})\omega_n = \frac{\omega_n}{2\zeta} \approx \omega_z$

• $\omega_{p_2} \approx (-\zeta - \zeta + \frac{1}{2\zeta})\omega_n \approx -2\zeta\omega_n$.

vanish

Razavi, "Design of CMOS
Phase-Locked Loops", Chapter
8.1.

8.1 More on PLL Transfer Functions

Our study of simple charge-pump PLLs has led to various closed-loop transfer functions from different points to the output. In summary, we have found that (a) the input phase fluctuations experience a second-order low-pass transfer with one zero, and (b) noise voltages in series with the control or supply of the VCO see a band-pass response. In this section, we further explore the PLL transfer functions.

The input/output transfer function expressed by (7.23) can be rewritten as

$$H(s) = \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}. \quad (8.1)$$

The zero is located at $\omega_z = -\omega_n/(2\zeta)$ and the poles at

$$\omega_{p1,2} = (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n. \quad (8.2)$$


For $\zeta = 1$, we have $\omega_z = -\omega_n/2$ and $\omega_{p1} = \omega_{p2} = -\omega_n$. If, on the other hand, $\zeta^2 \gg 1$, then $\sqrt{\zeta^2 - 1} \approx \zeta[1 - 1/(2\zeta^2)] = \zeta - 1/(2\zeta)$, yielding

$$\omega_{p1} \approx -\frac{\omega_n}{2\zeta} = -\frac{1}{R_1 C_1} \quad (8.3)$$

$$\omega_{p2} \approx -2\zeta\omega_n = -\frac{R_1 I_p K_{VCO}}{2\pi}. \quad (8.4)$$

Jitter Peaking (II)^[2]
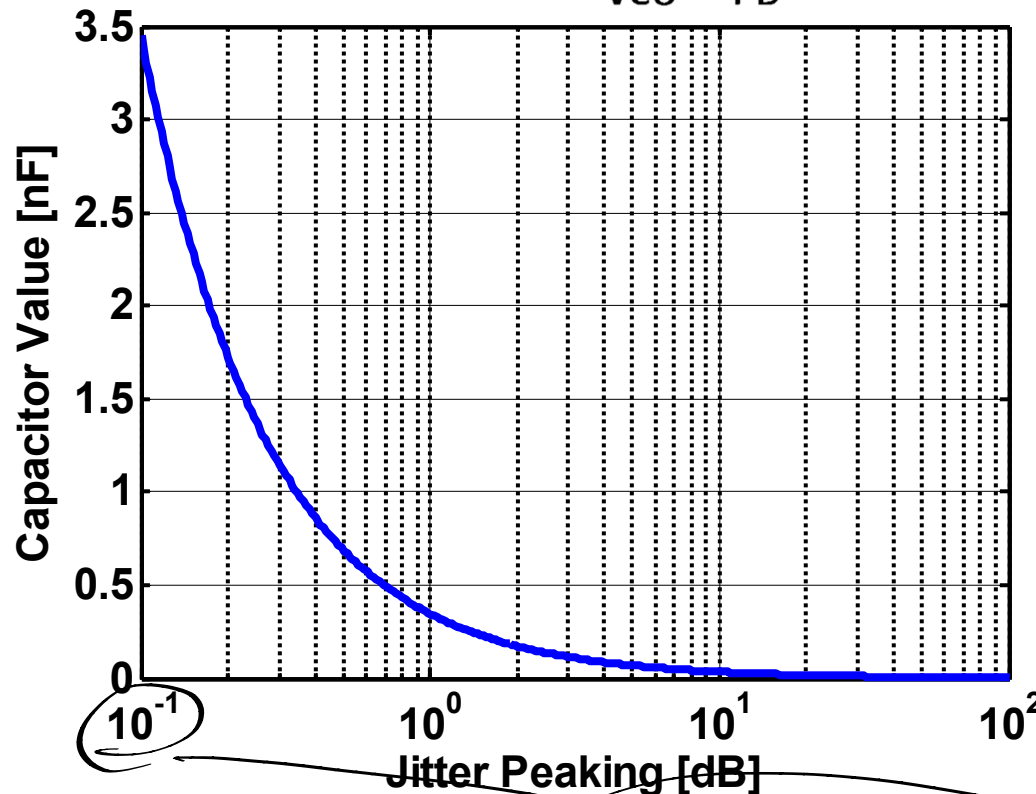
$$\text{Jitter Peaking [dB]} \approx \frac{8.686}{K_{\text{VCO}} K_{\text{PD}} C R^2} \approx \frac{8.686}{\omega_{-3\text{dB}} C R}$$




□ BW = 4MHz, R = 1kΩ & 0.1dB peaking, C ~ 3.5nF

repeaters : can't tolerate any jitter peaking.

expensive

Jitter Tracking

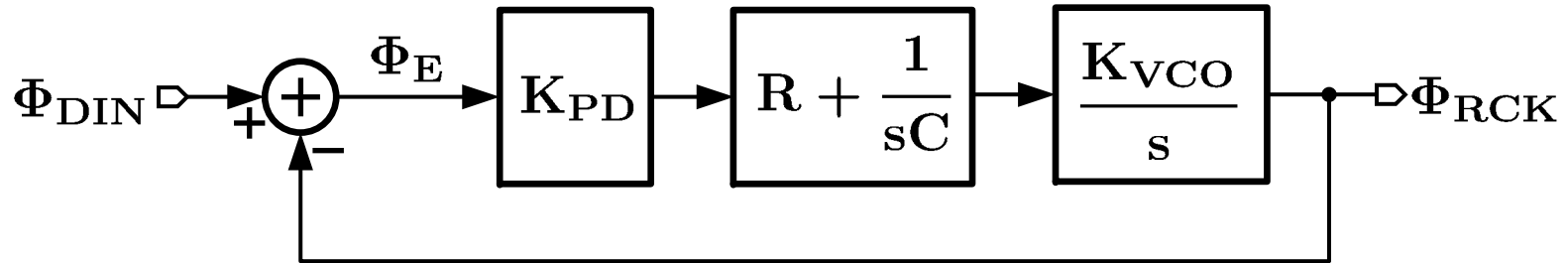


$$\begin{aligned}
 H_{\text{JTRACK}}(s) &= \frac{\Phi_E(s)}{\Phi_{\text{DIN}}(s)} = \frac{1}{1 + \mathbf{LG}(s)} \\
 &= \frac{s^2 \cdot \frac{C}{K_{\text{VCO}} K_{\text{PD}}}}{1 + sRC + s^2 \cdot \frac{C}{K_{\text{VCO}} K_{\text{PD}}}} \\
 &\equiv \frac{s^2 / \omega_{\text{PL}} \omega_{\text{PH}}}{(1 + s/\omega_{\text{PL}})(1 + s/\omega_{\text{PH}})}
 \end{aligned}$$

$$\text{JTRACK BW} = \underbrace{\omega_{-3\text{dB}}}_{\approx \omega_{\text{PH}}} \approx K_{\text{VCO}} \cdot K_{\text{PD}} \cdot R$$

When jitter $f \ll \text{BW}$, fully tracked.

Jitter Tolerance (JTOL) (I)

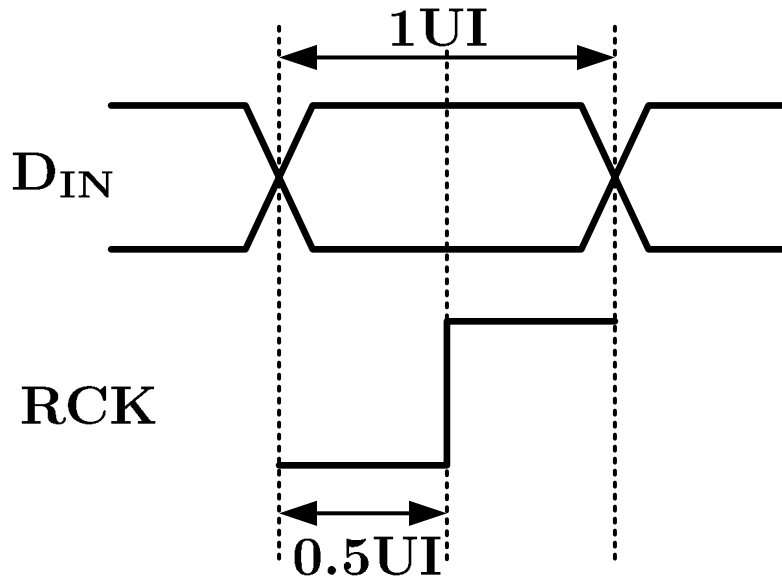

$$|\Phi_E| < 0.5 UI$$


$$\Phi_{DIN} \times H_{JTRACK}(s) < 0.5 UI$$

$$\Rightarrow \Phi_{DIN} < \frac{0.5 UI}{H_{JTRACK}(s)}$$

$$\underline{\underline{H_{JTOL}(s) = \frac{0.5}{H_{JTRACK}(s)}}}$$

$$H_{JTOL}(s) = \frac{0.5 (1 + s/\omega_{PL}) (1 + s/\omega_{PH})}{s^2 / \omega_{PL} \omega_{PH}}$$

Jitter Tolerance (JTOL) (II)

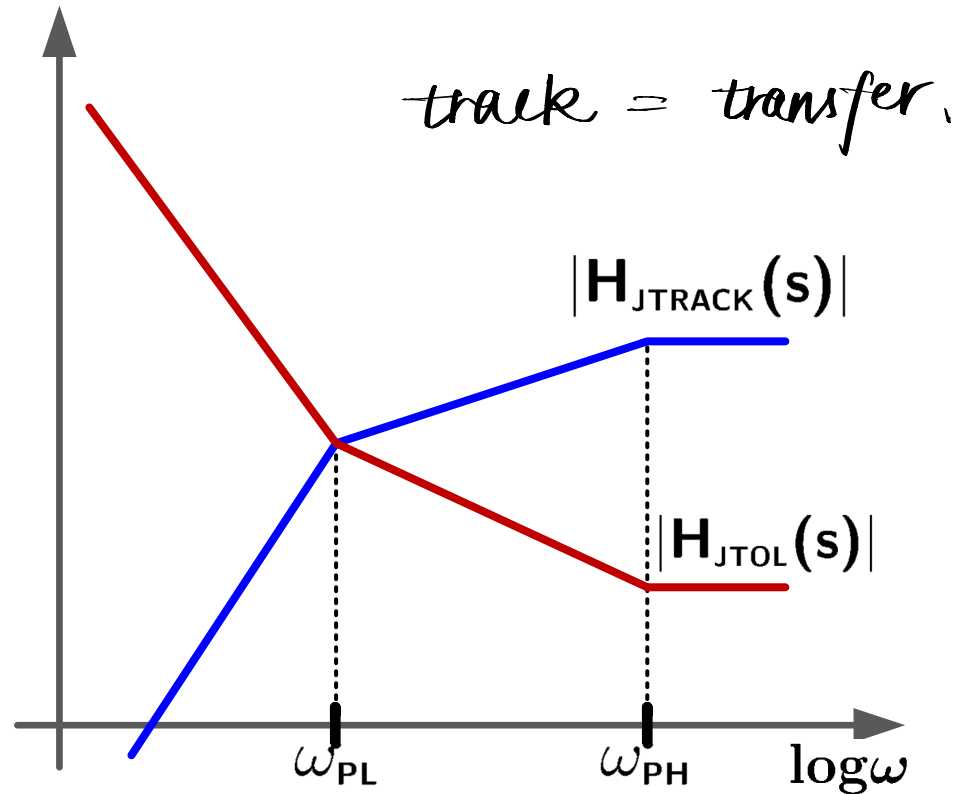


- JTOL improves w/ better jitter tracking
 - Better jitter tracking → wider JTRAN bandwidth!

Coupled JTRAN/JTOL Behavior

$$H_{JTRAN}(s) = \frac{1 + sRC}{1 + sRC + s^2 \cdot \frac{C}{K_{VCO}K_{PD}}}$$

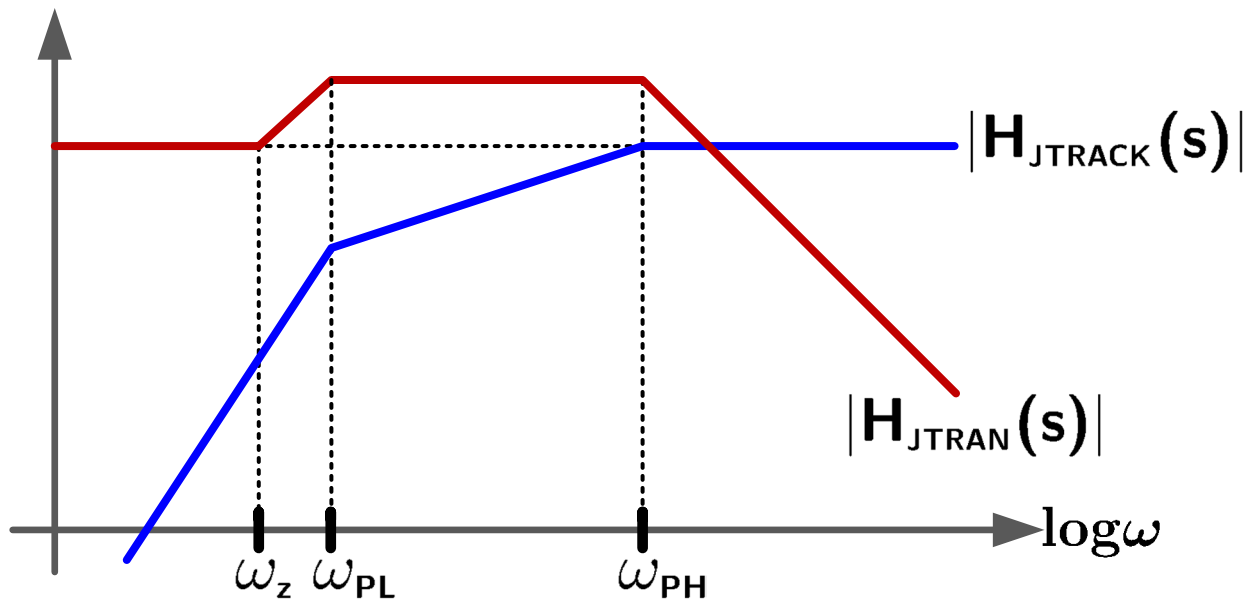
$$H_{JTRACK}(s) = \frac{s^2 \cdot \frac{C}{K_{VCO}K_{PD}}}{1 + sRC + s^2 \cdot \frac{C}{K_{VCO}K_{PD}}}$$



□ Both JTRAN and JTOL are governed by ω_{PH}


* JTOL

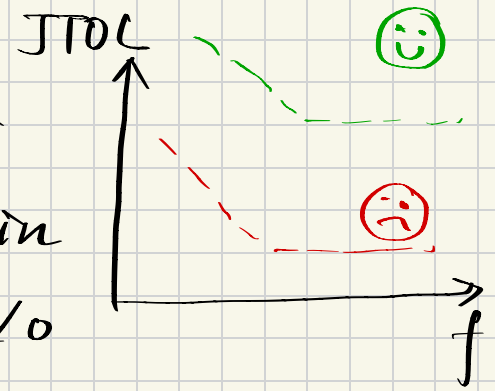usually JTOL is the larger the better since it characterizes how much jitter in the data stream can CDR tolerate w/o causing a bit error.




* Jtran

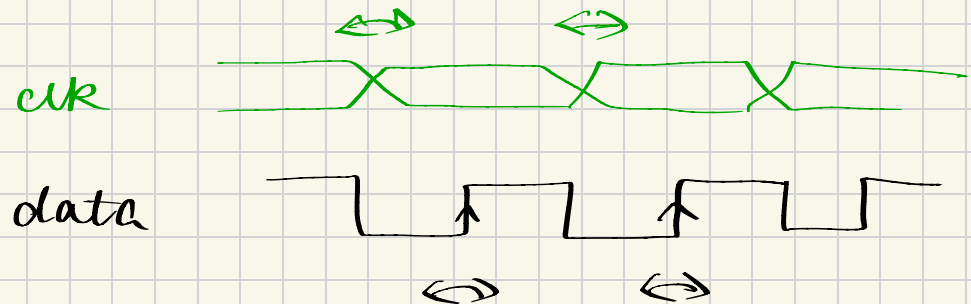however, this does require the recovered clock to "track" the jittery data in order to track the behavior well.



Δ this can cause the recovered clock to be jittery, or even sometimes missing edges.


Hogge PD Non-idealities: Offset^[2]

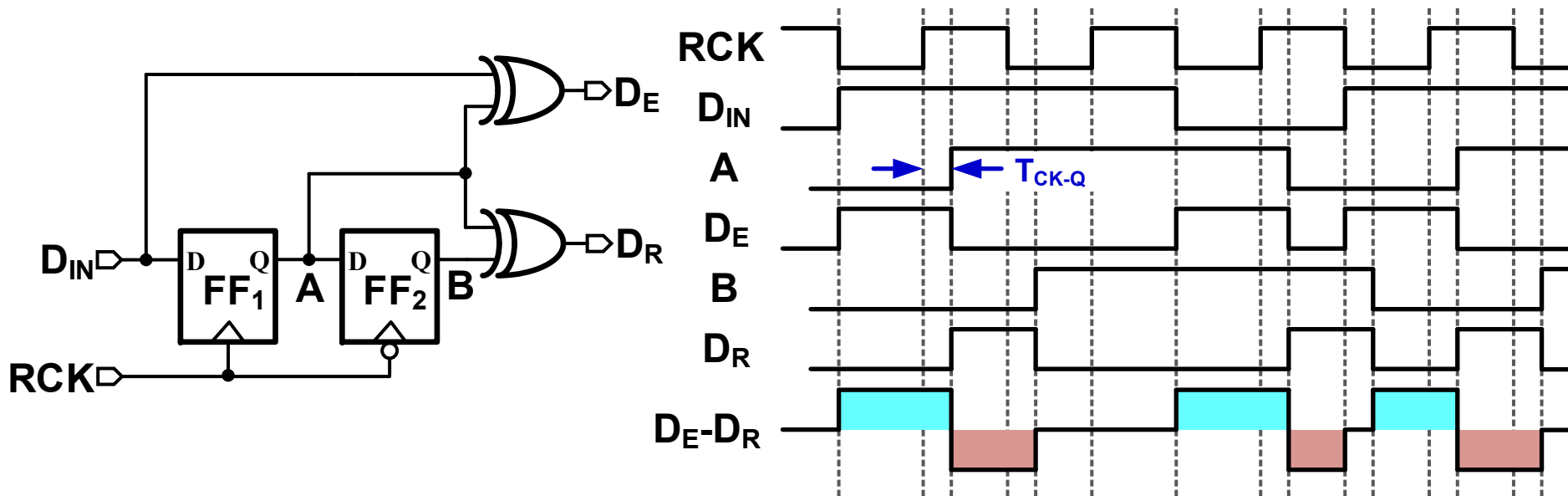

- FF1 clock-to-Q delay introduces phase offset
causing locking errors.

Hogge PD Offset Mitigation^[2]


hard to track PVT

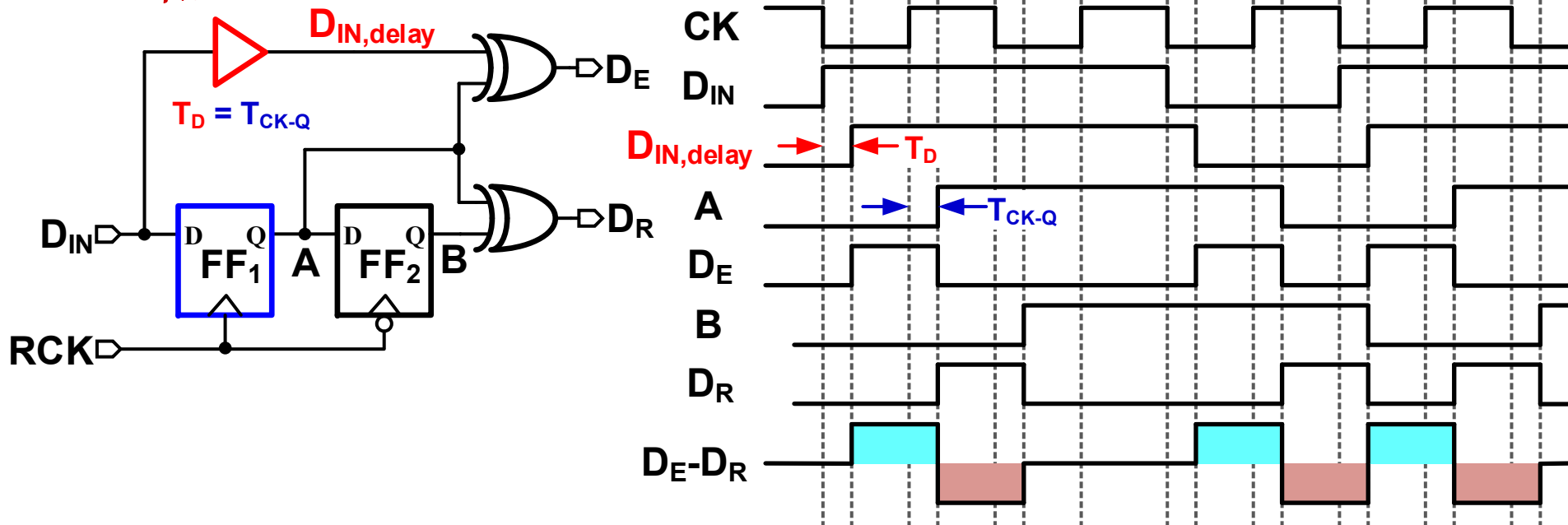

- ❑ FF1 clock-to-Q delay introduces phase offset
- ❑ FF1 delay compensated by inserting buffer
 - T_D may not track T_{CK-Q} across supply and temperature
 - Generating small well controlled T_D is also difficult

main reason Hogge PD not used in high f.



Hogge PD Non-idealities: DDJ^[2]

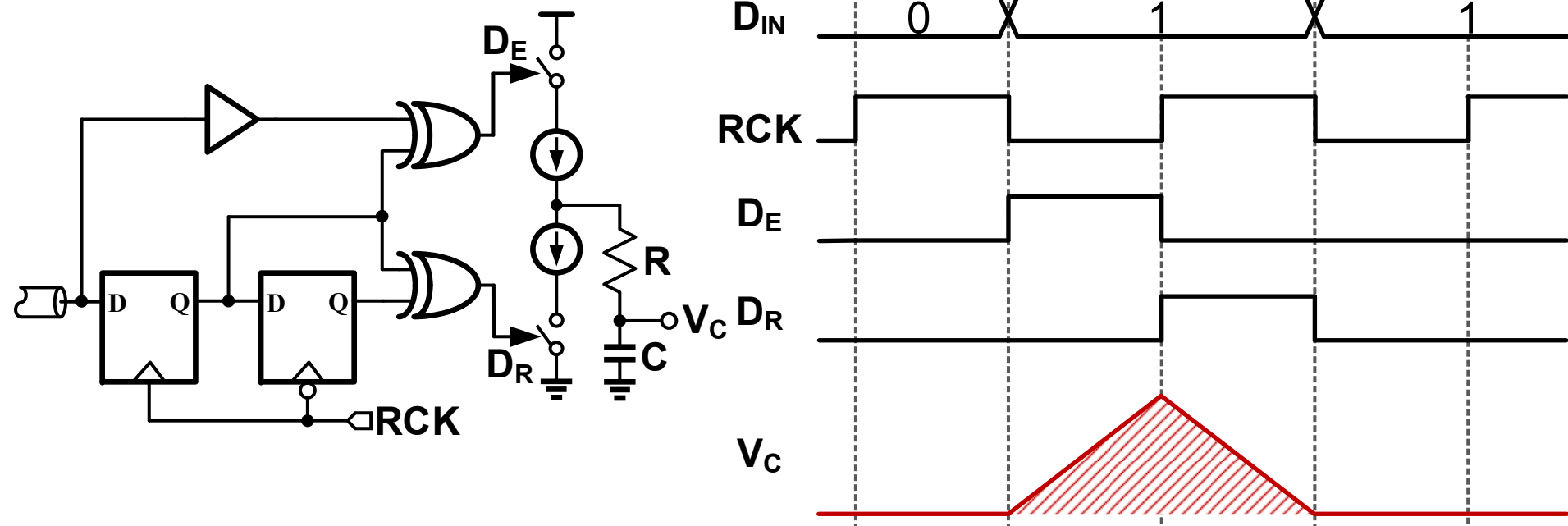


- D_E/D_R pulses not aligned in time ↑ causing VCO $f \uparrow$
 - "Tri-wave" on V_C causes Data Dependent Jitter (DDJ)
- See [2] for modified Hogge PD to mitigate DDJ

Bang-Bang Phase Detector (I)

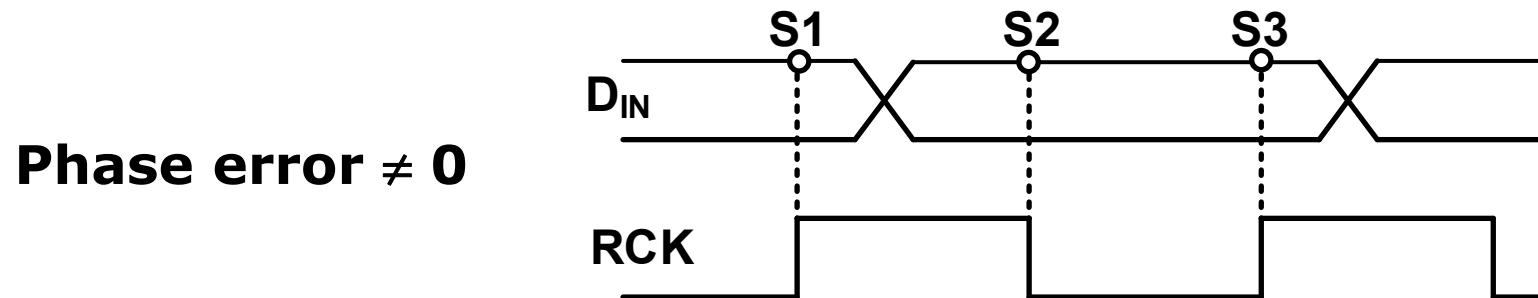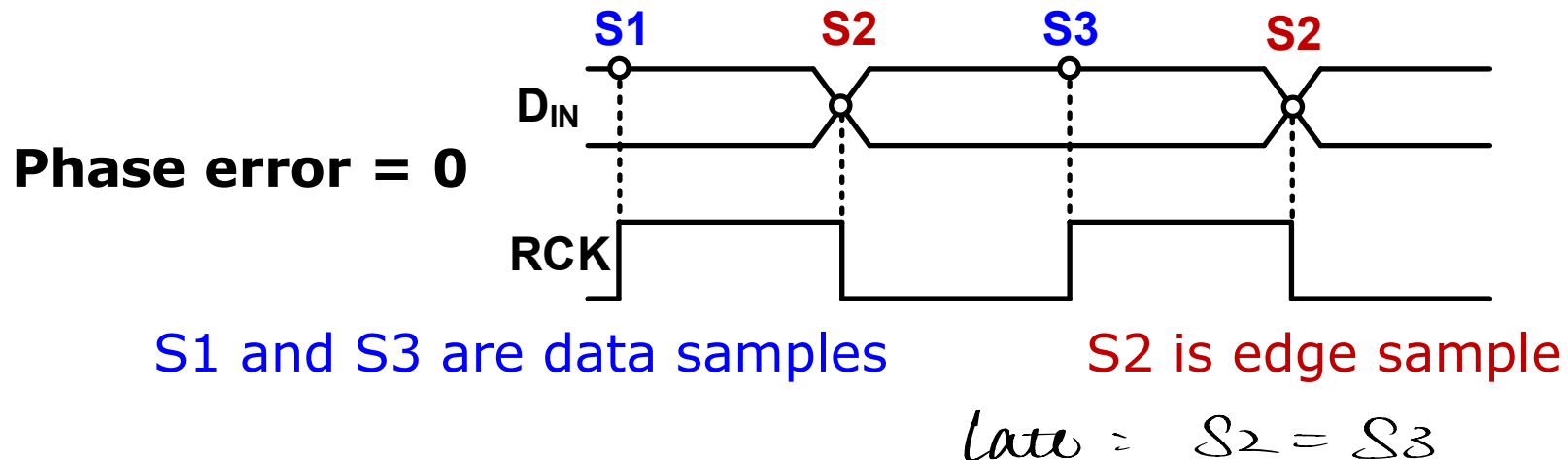
□ Can we detect phase error from sampled data?



Bang-Bang Phase Detector (II)^[3]

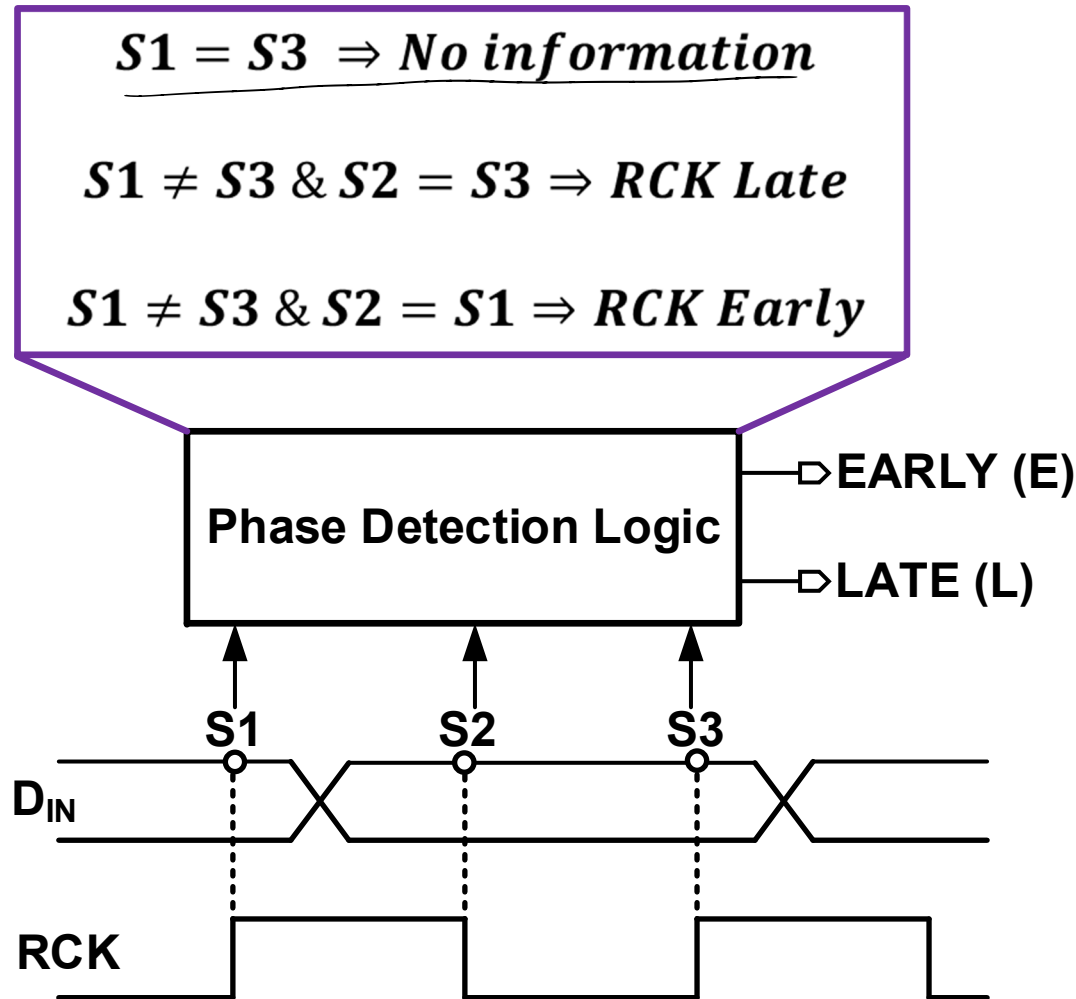

BBPD Characteristics: w/o Jitter

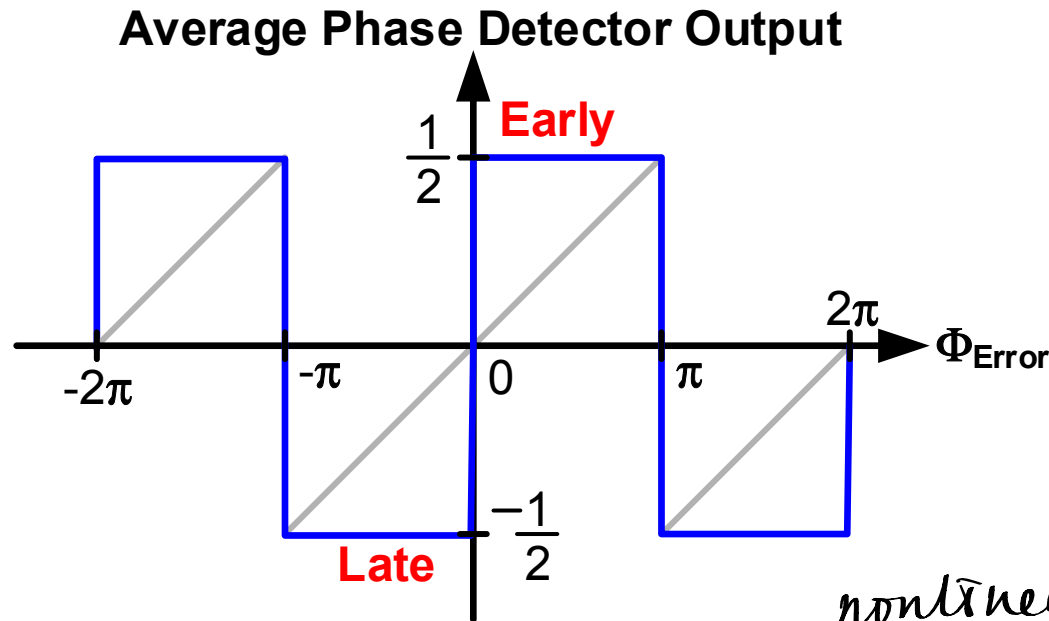


nonlinear


Useful range : $\pm\pi$

Gain $K_{PD}|_{\Delta T=0} = \infty$

BBPD Characteristics: w/Jitter (I)^[4]

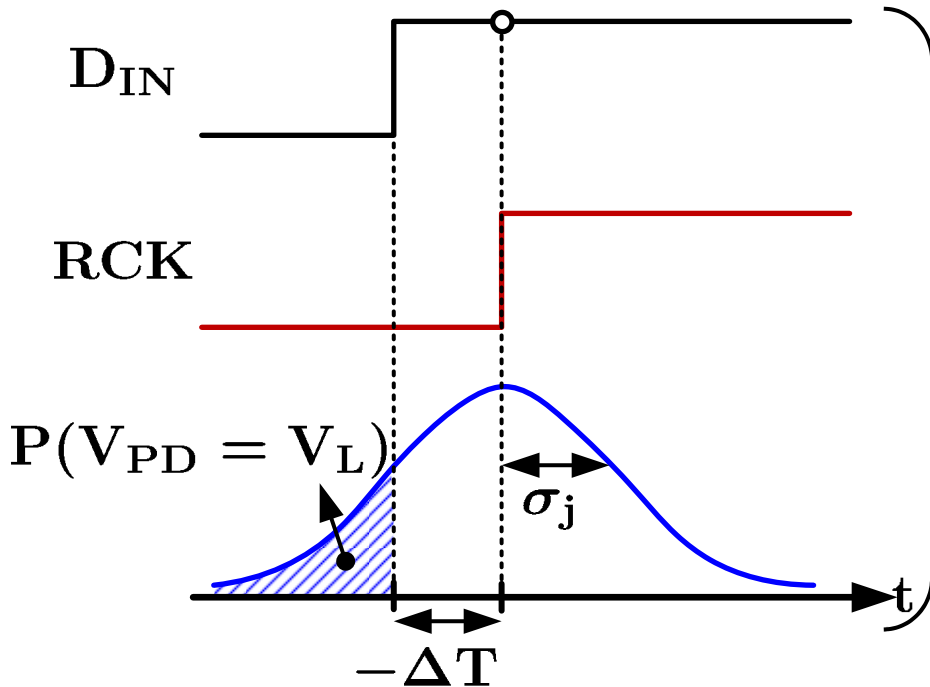

Discrete PDF of BBPD output

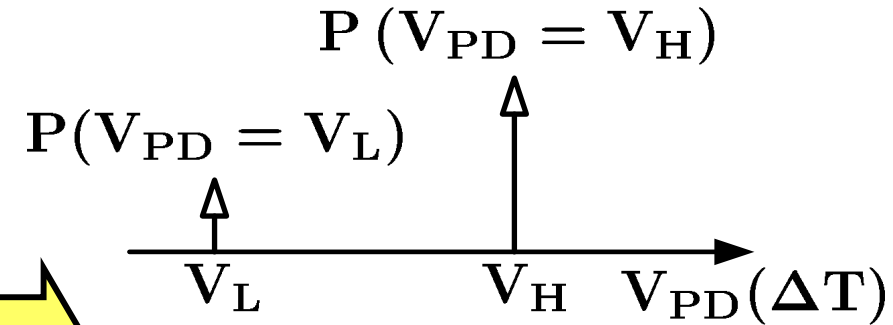

$$P(V_{PD} = V_L) = \int_{-\infty}^{-\Delta T} p(x) dx$$

$$P(V_{PD} = V_H) = \int_{-\Delta T}^{\infty} p(x) dx$$

$$\overline{V_{PD}(\Delta T)} = V_L \cdot P(V_{PD} = V_L) + V_H \cdot P(V_{PD} = V_H)$$

BBPD Characteristics: w/ Jitter (II)


$$\overline{V_{PD}(\Delta T)} = 2V_o \cdot \text{erf} \left(\frac{\Delta T}{\sigma_j} \right)$$

$$\text{erf}(x) = \frac{1}{\sqrt{2\pi}} \int_0^x e^{-y^2} dy$$

$$\text{Gain } K_{PD}|_{\Delta T=0} = \frac{2V_o}{\sqrt{2\pi}\sigma_j}$$


Linear range : $\pm 2\sigma_j$

linearized due to jitter.

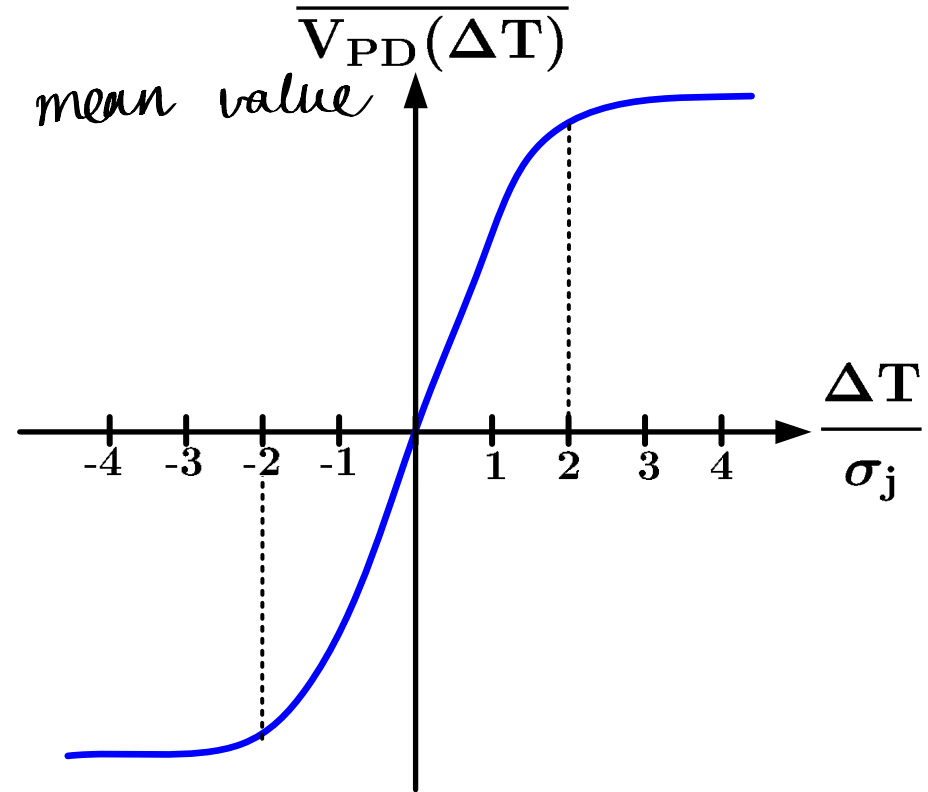

$$K_{PD} = \frac{d\overline{V_{PD}(\Delta T)}}{d\Delta T} = \frac{2V_o}{\sqrt{2\pi}\sigma_j} e^{\left(-\frac{\Delta T}{\sqrt{2}\sigma_j}\right)^2}$$

Full-rate Bang-Bang CDR

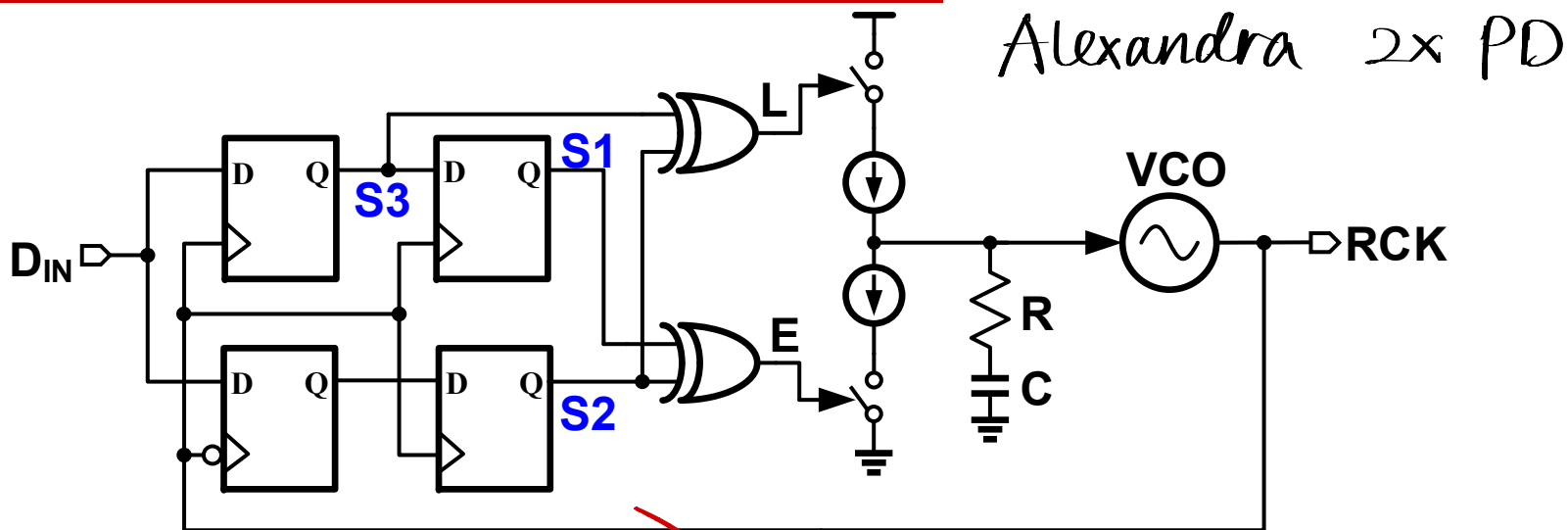


- ❑ Type-II response
- ❑ Near-zero static phase offset
- ❑ Insensitive to charge-pump non-idealities
- ❑ VCO & PD operate at full-rate ($F_{VCO} = F_{DIN}$)
 - Could become a speed bottleneck
 - Solution: Half-rate bang-bang CDR


sub-rate CDR

because K_{PD} is large!
 might be a PDK limitation

Half-rate CDR Waveforms

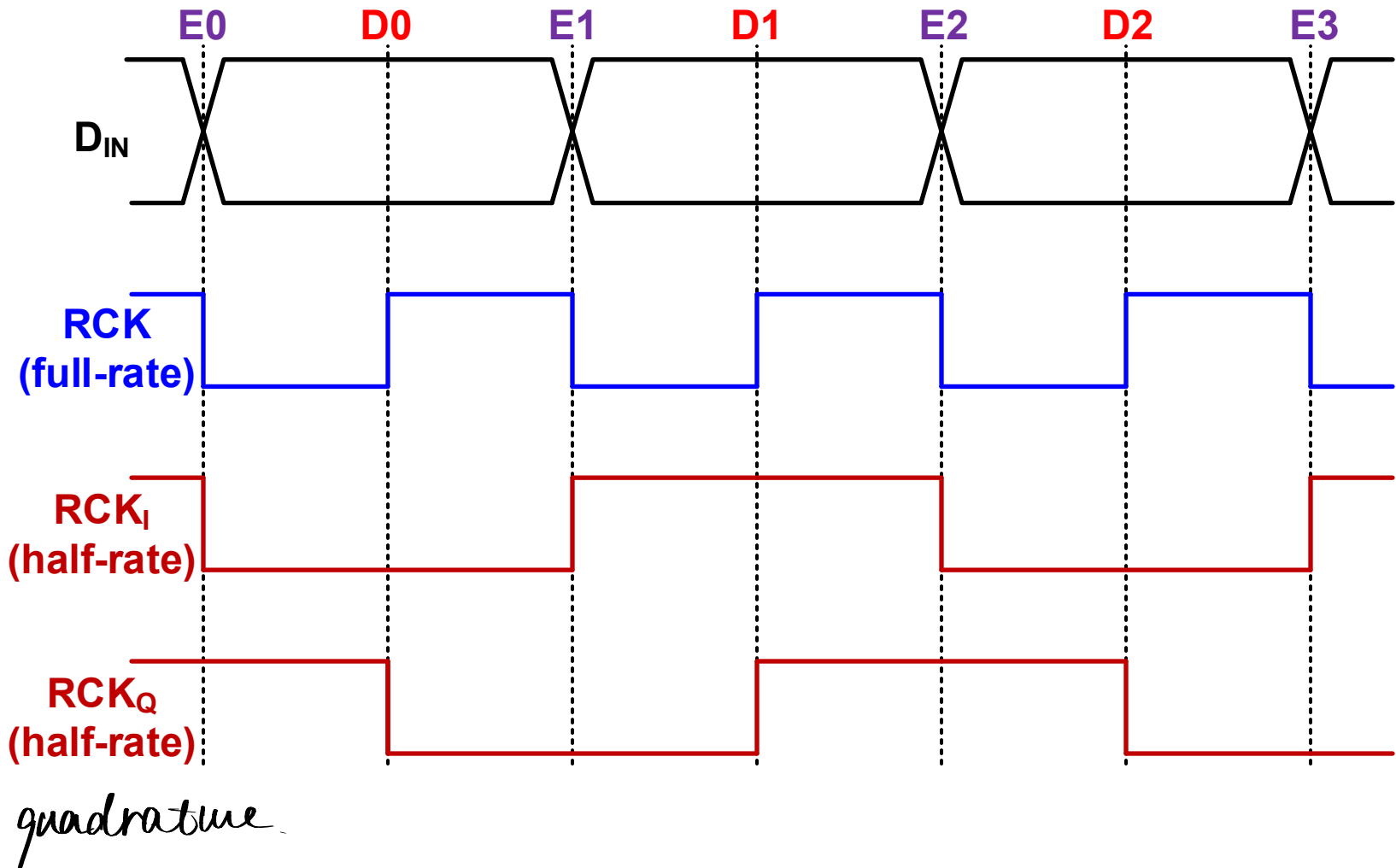


Half-Rate Bang-Bang CDR

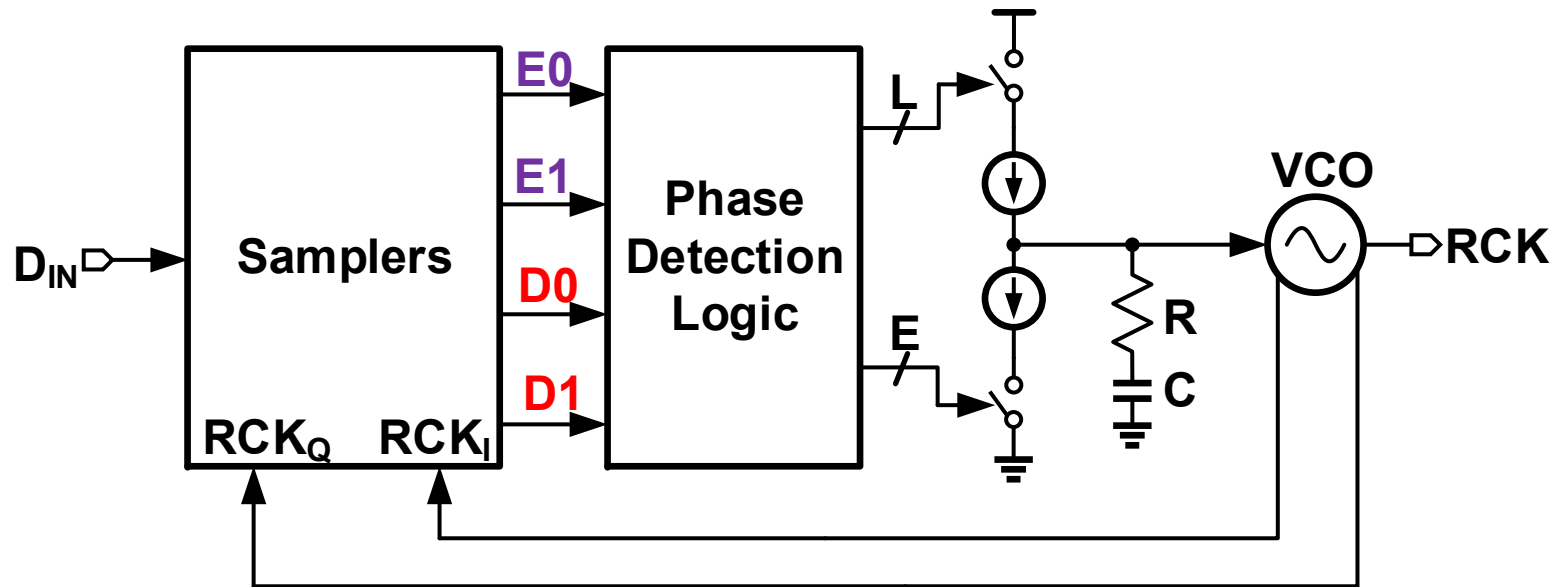

- Topology same as full-rate architecture
 - Same phase detection logic as full-rate
- Requires quadrature VCO
- Lower loop update rate → higher loop latency

Choosing Loop Parameters^[5]

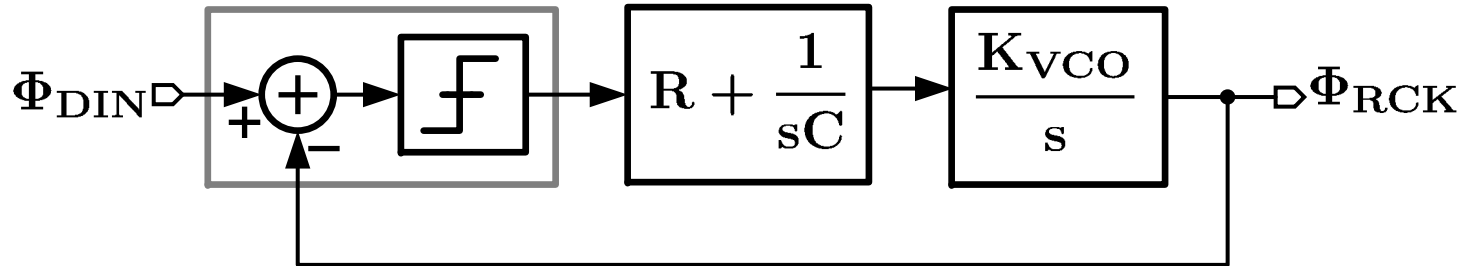

$$\text{Damping factor } \xi = \frac{\Delta\Phi_{RCK} \text{ due to prop. path}}{\Delta\Phi_{RCK} \text{ due to integ. path}} = \frac{2RC}{T_{UPDATE}} \gg 1$$



- BBPD makes the loop non-linear
 - Cannot use transfer function analysis
 - Loop gain is infinite $\rightarrow$ unstable in “linear sense”

- Ensure stability by choosing large damping factor
 - Relatively independent proportional and integral paths


Bang-Bang CDR Drawbacks

- ❑ Coupled JTRAN and JTOL
 - ❑ Jitter peaking
 - ❑ Large loop filter area
- } Similar to linear CDR
-
- ❑ **JGEN caused by limit cycles** (*nonlinear behavior*)
 - ❑ **JTRAN dependence on input jitter**

Steady-State Limit Cycles (I)

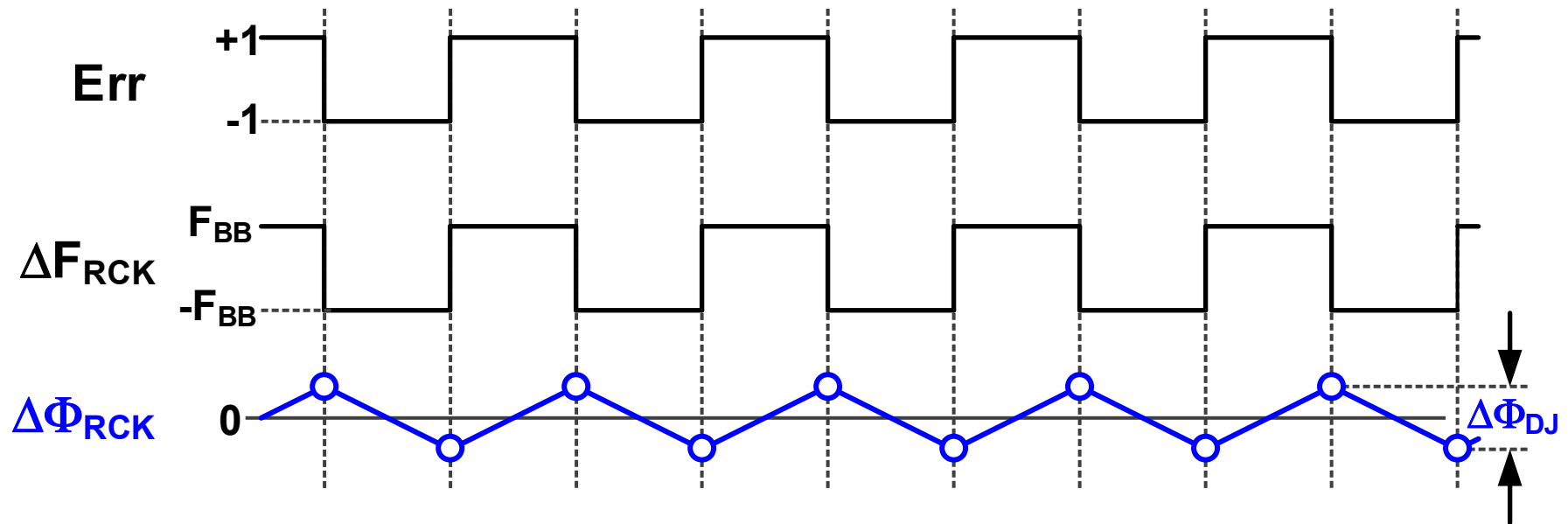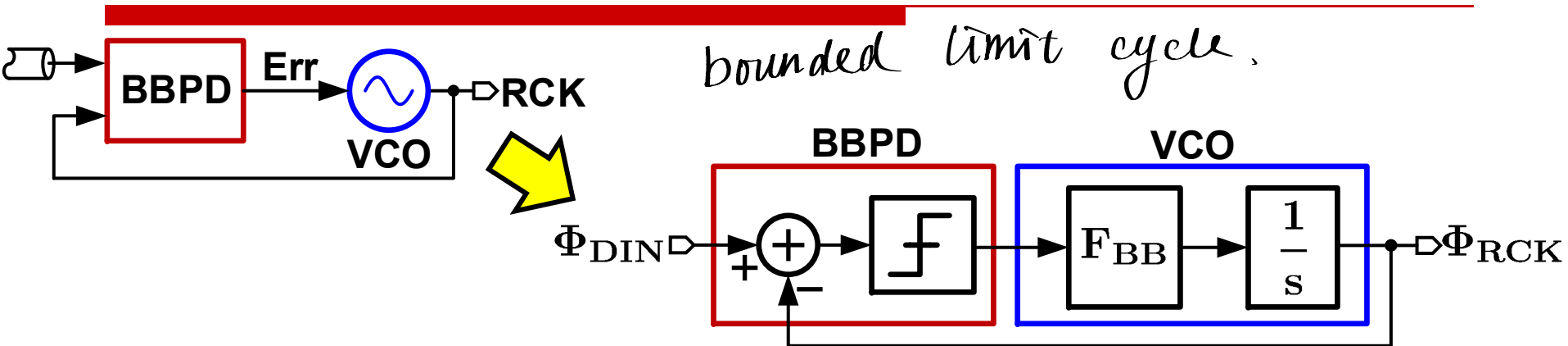



Steady-State Limit Cycles (II)

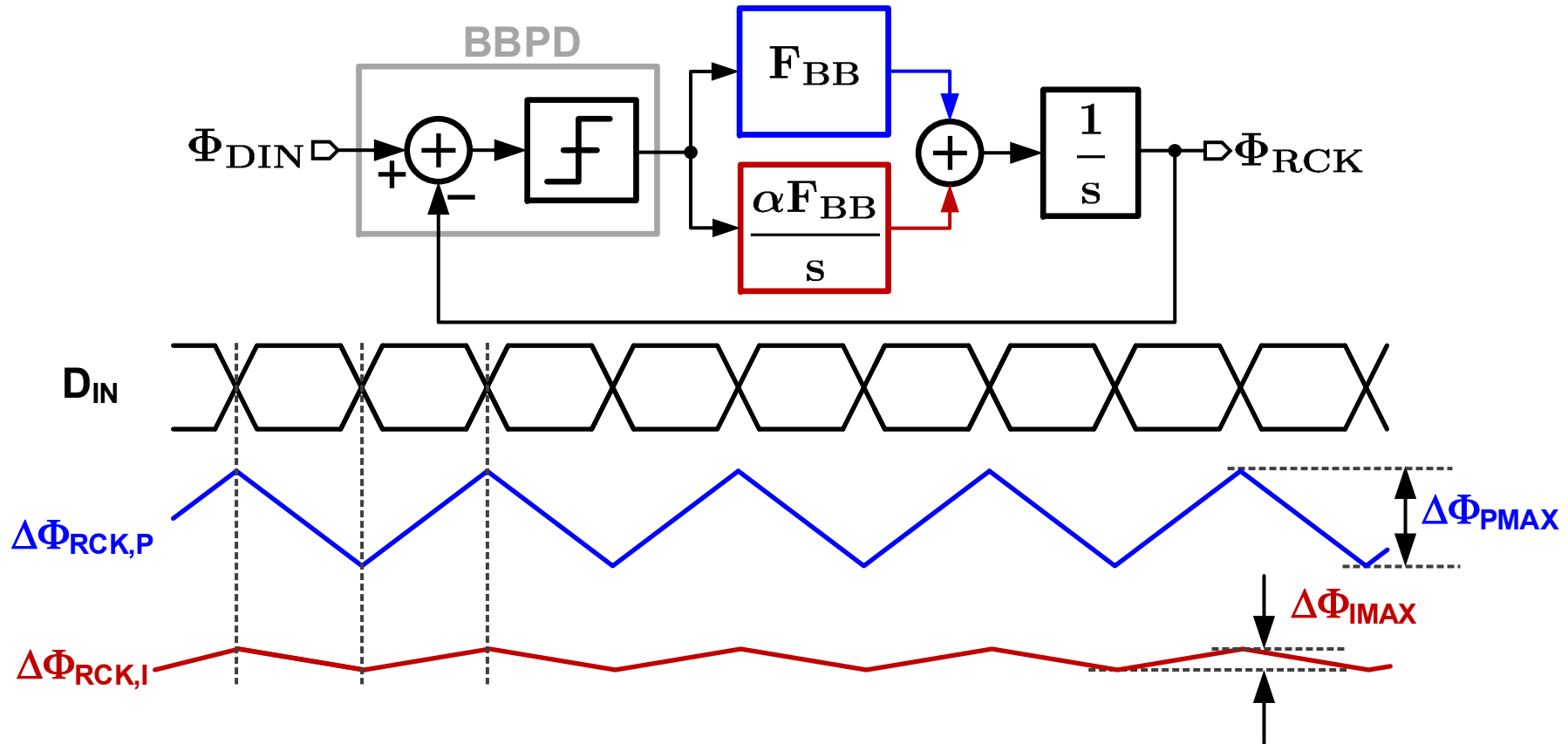


Proportional path dominates dithering jitter

I path suppress low f drifts

Loop Delay Increases JGEN

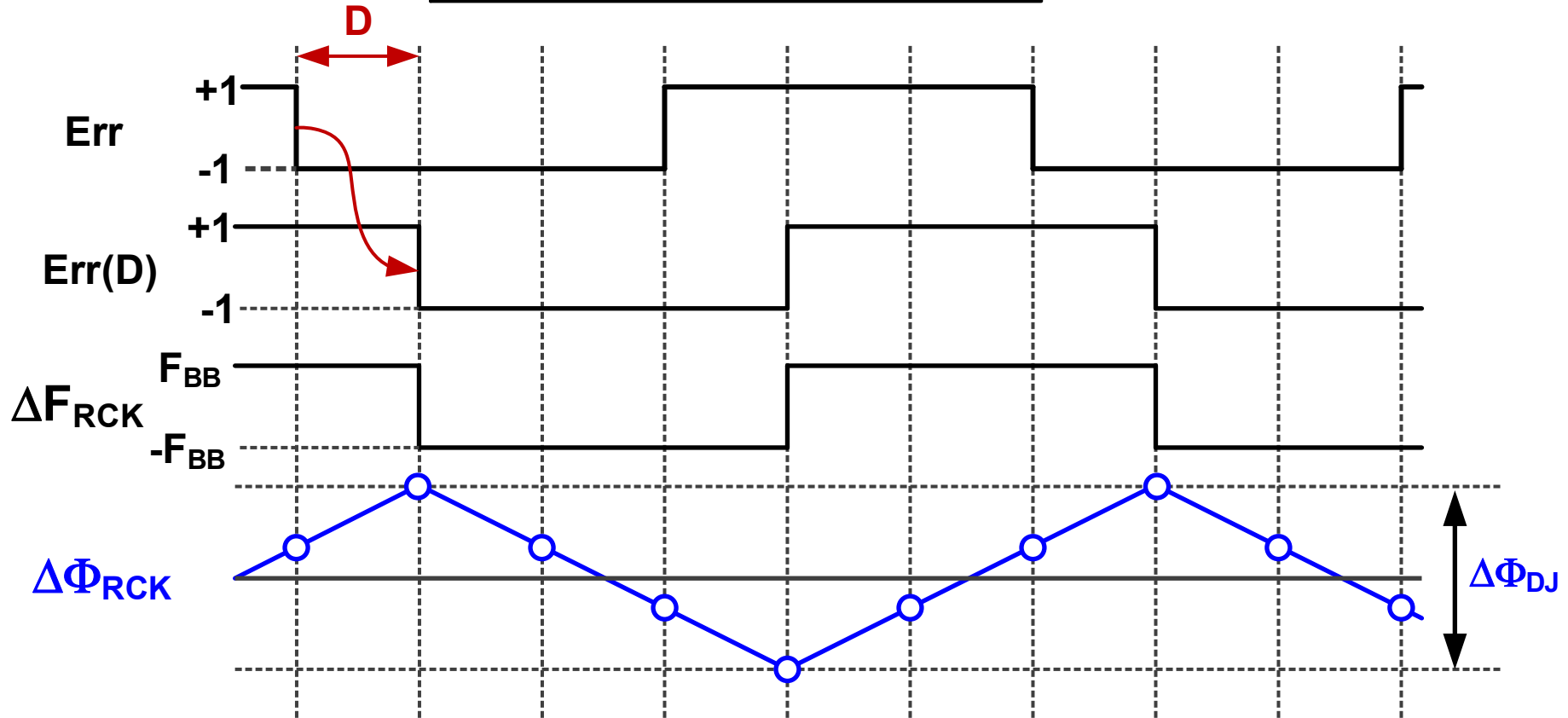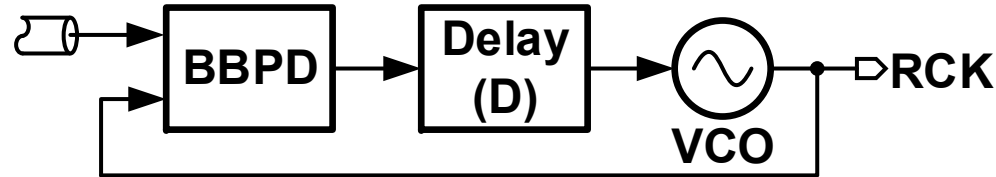

JGEN vs. Bang-Bang Step Size

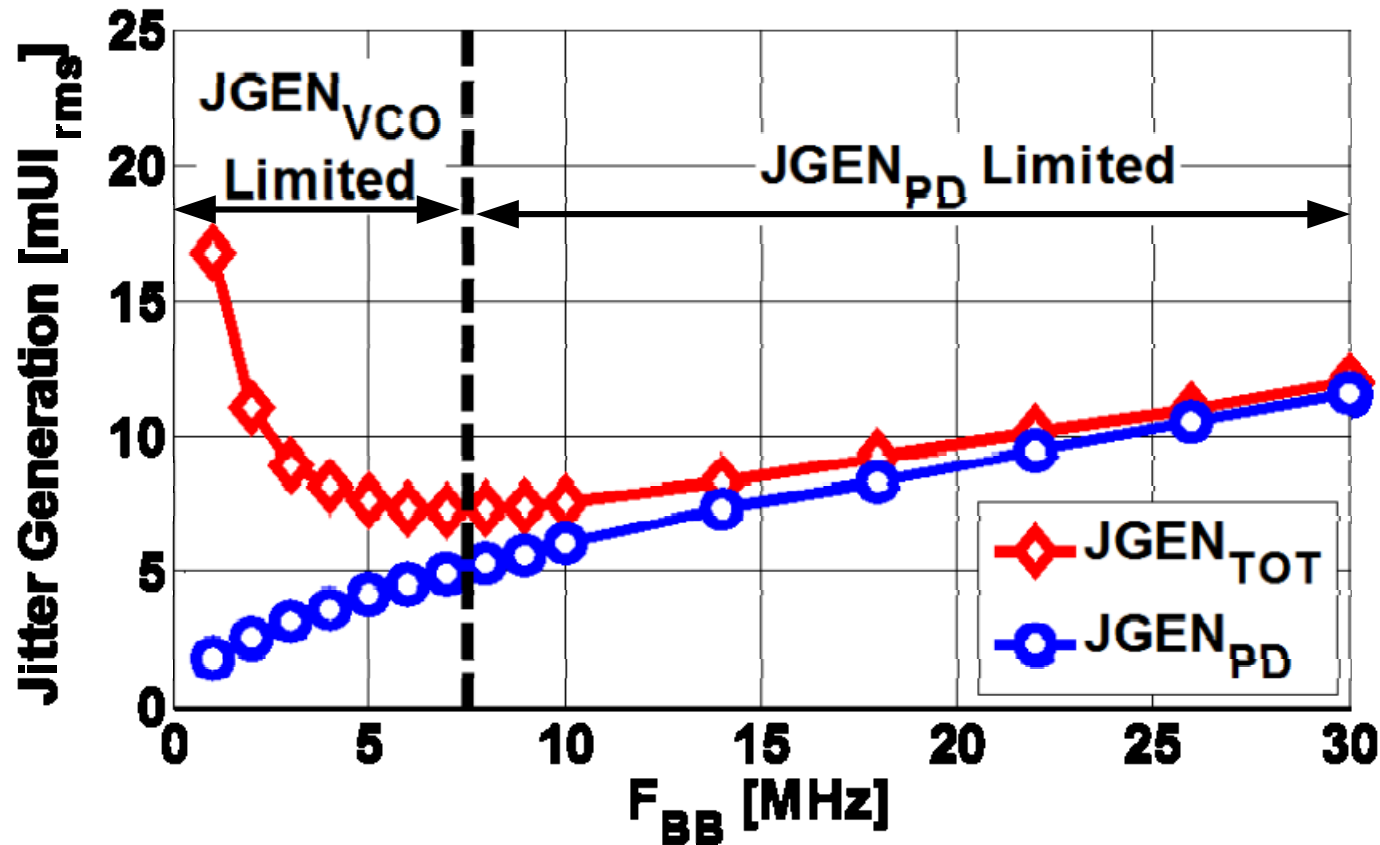

- As bang-bang step size increases:
 - Contribution of PD noise to output noise increases
 - Contribution of VCO noise to output noise decreases

JTRAN Dependence on Jitter

$$\text{JTRAN BW} \approx K_{PD} \cdot K_P \cdot K_{VCO}$$

$$\text{Gain } K_{PD}|_{\Delta T=0} = \frac{2V_o}{\sqrt{2\pi}\sigma_j} \implies \text{JTRAN BW} \propto \frac{1}{\sigma_j}$$

- JTRAN is inversely proportional to input jitter
 - Difficult to predict *a priori*
- Set JTRAN for minimum input jitter condition
 - Makes it more susceptible to VCO phase noise


Tutorial Roadmap

- Performance metrics
 - **Basic architectures**
 - **Linear/Bang-bang**
 - **Digital**
 - **Hybrid**
 - Application-specific CDRs
 - Multi-lane chip-to-chip links
 - Repeaters for optical and active cables
 - Summary
-

Eliminating Loop Filter Capacitor

Just like digital PLL

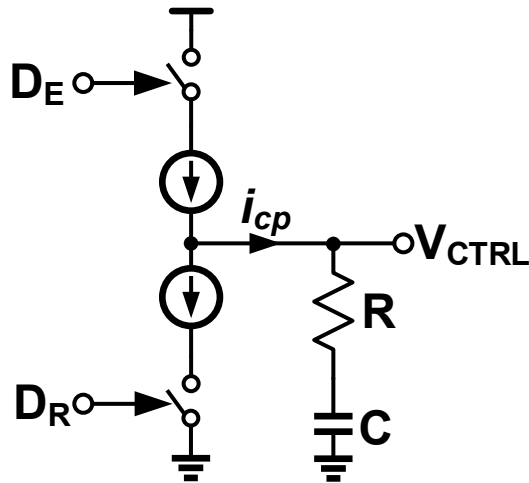
- Map CP + LF into digital domain directly



$$i_{cp}R + \frac{i_{cp}}{Cs} \Rightarrow i_{cp}R + \frac{i_{cp}T}{C} \frac{z^{-1}}{1-z^{-1}}$$

- Digital accumulator replaces loop filter capacitor
 - Large time constant with small area
 - Infinite DC gain → ideal Type-II behavior
 - PVT insensitive
 - Easy to reconfigure for loop dynamics control

Simple Digital CDR^[6]

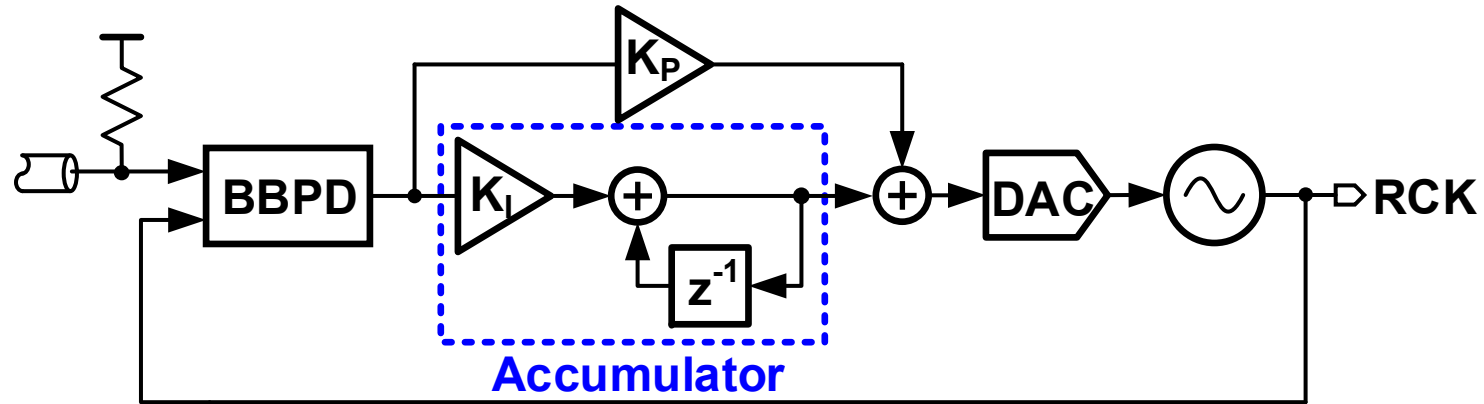


□ Loop filter must operate at data rate

□ **Need:**


- Wide operand high-speed adders
- High speed/resolution **D**igital to **A**nalog **C**onverter (**DAC**)

Reducing Speed Requirements (I)

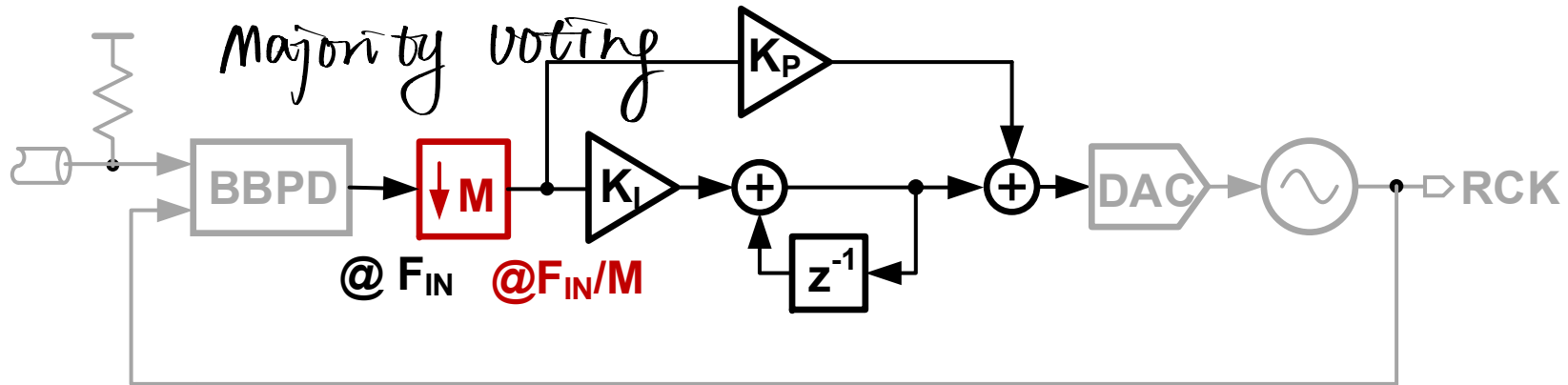


- ❑ Decimation eases speed requirements
- ❑ Lower update rate $\rightarrow$ increases loop latency
 - Loop latency increases dithering jitter
- ❑ Observation: Proportional path dominates jitter

Reducing Speed Requirements (II)

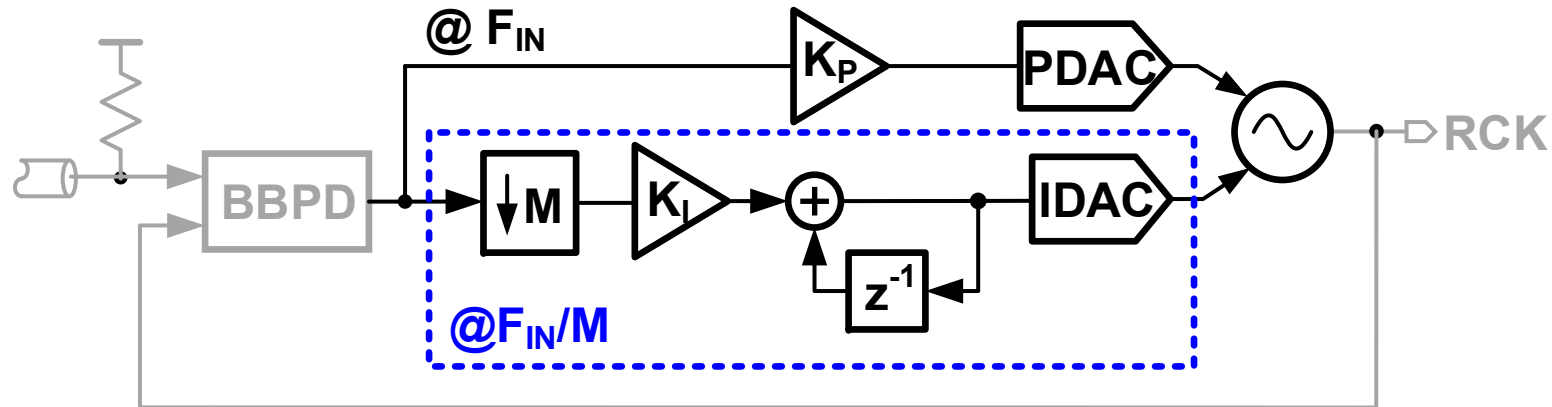

- Fast proportional path *no latency*
 - Minimize latency → reduce dithering jitter
- High resolution integral path
 - Minimize tracking jitter
- Minimal hardware penalty
 - Needs only 2-level high-speed PDAC

Practical Digital CDR

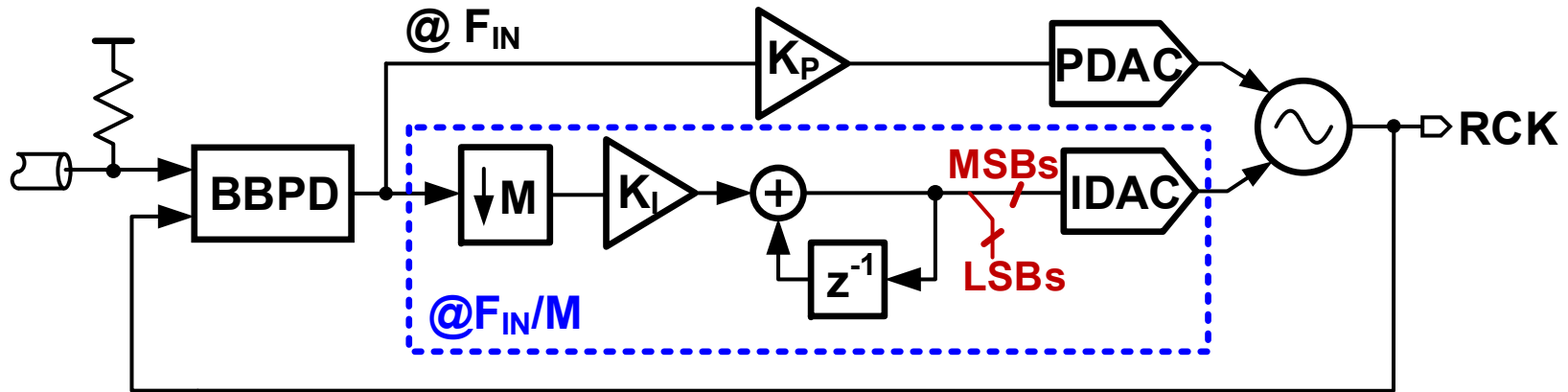


- ❑ Loop delay increases integral path dithering jitter
 - Reduce gain by dropping lower LSBs
- ❑ IDAC implemented using $\Delta\Sigma$ techniques
- ❑ Proportional and integral controls summed in VCO
- ❑ Area efficient $\rightarrow$ can be fully integrated

Digital CDR Drawbacks


- ❑ Coupled JTRAN and JTOL
 - ❑ Jitter peaking
 - ❑ ~~Large loop filter area~~
- } Similar to linear CDR
-
- ❑ JGEN vs bang-bang step size tradeoff
 - ❑ JTRAN dependence on input jitter
- } Similar to BB CDR
-
- ❑ **Sensitive to Consecutive Identical Digits (CIDs)**

Impact of CIDs^[7]

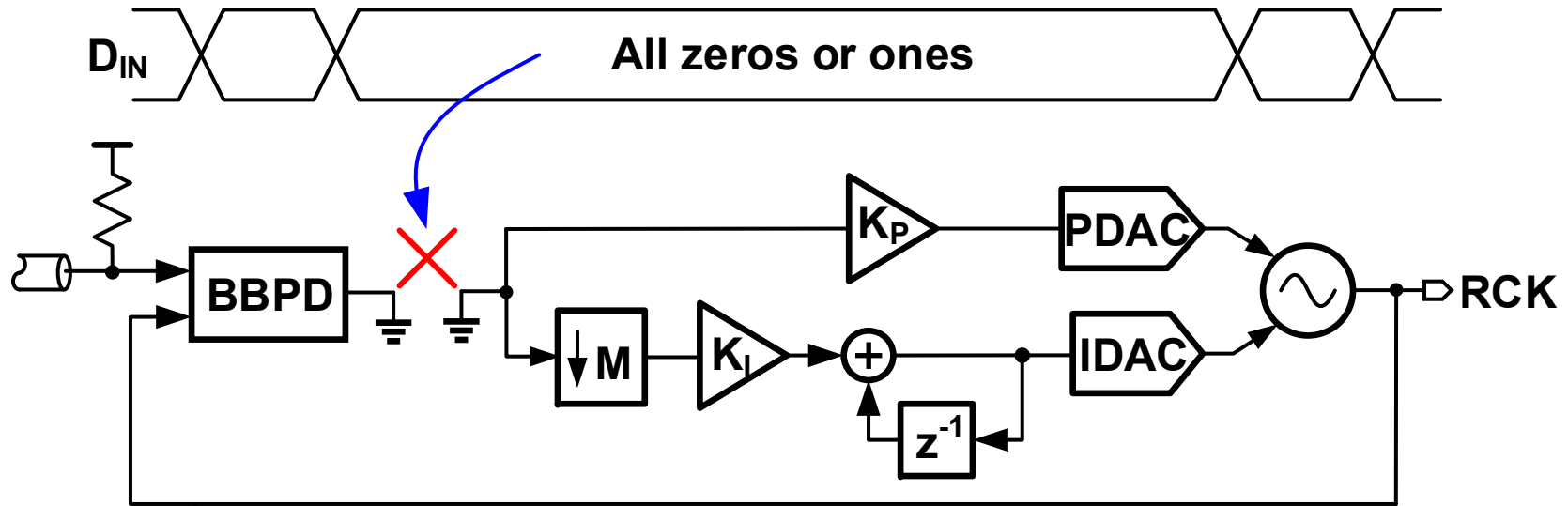

- ❑ BBPD output is zero for the duration of CIDs
 - CDR operates in open loop
- ❑ All benefits of feedback are lost
 - Noise, leakage, PVT sensitivity, ...

JGEN due to CIDs

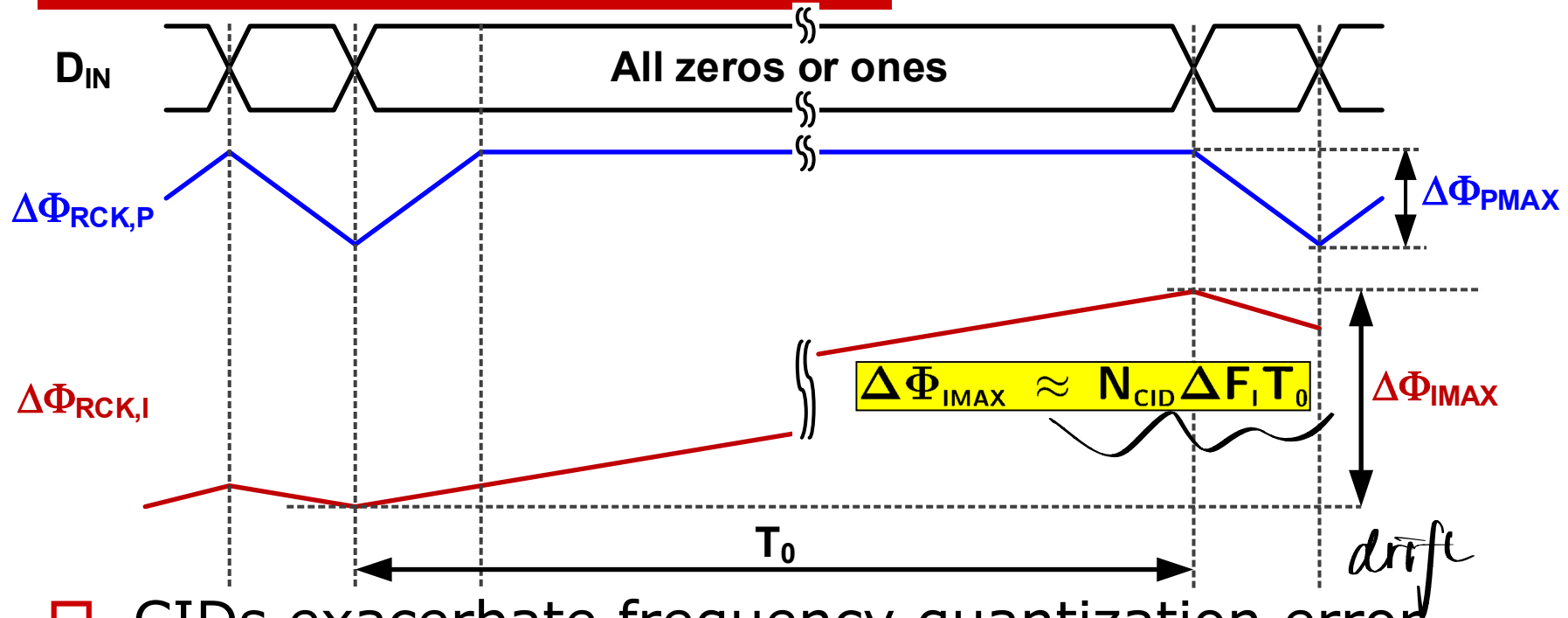

- CIDs exacerbate frequency quantization error
 - Output phase drifts at a rate proportional to freq. error
- Impact on JGEN depends on:
 - Number of CIDs (N_{CID})
 - Integral path frequency quantization error (ΔF_I)


Analog vs. Digital CDRs

- Analog CDR using linear PD
 - Well-controlled loop dynamics
 - PD non-idealities degrade timing margin/BER
 - Large loop filter capacitor

- Digital CDR using bang-bang PD
 - Non-linear loop dynamics (JTRAN depends on jitter)
 - Bang-bang PD maximizes timing margin
 - No large capacitor (small area)

- Can we combine the advantages?


Hybrid Analog/Digital CDR^[8]

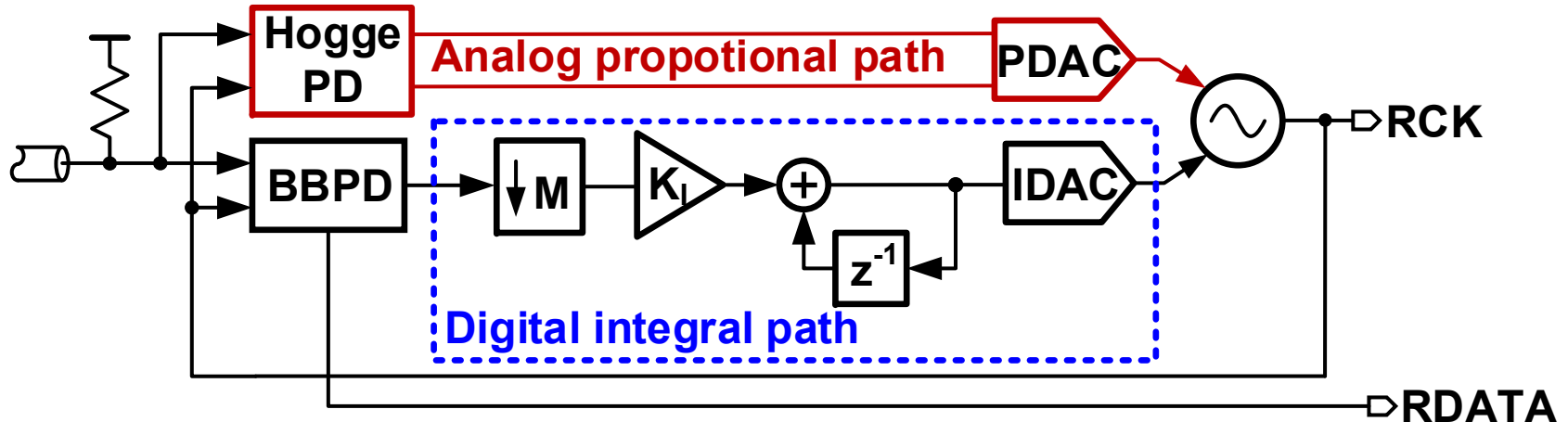

- Proportional path sets loop bandwidth (JTRAN)
 - Fixed gain leads to linear loop dynamics
 - Eliminates phase quantization error
- Digital integral path sets steady state
 - Makes it insensitive to linear PD phase offset
 - Accumulator filters BBPD quantization error
 - Causes ripple on the proportional path

Hybrid CDR JTRAN Characteristics


- JTRAN independent of jitter amplitude

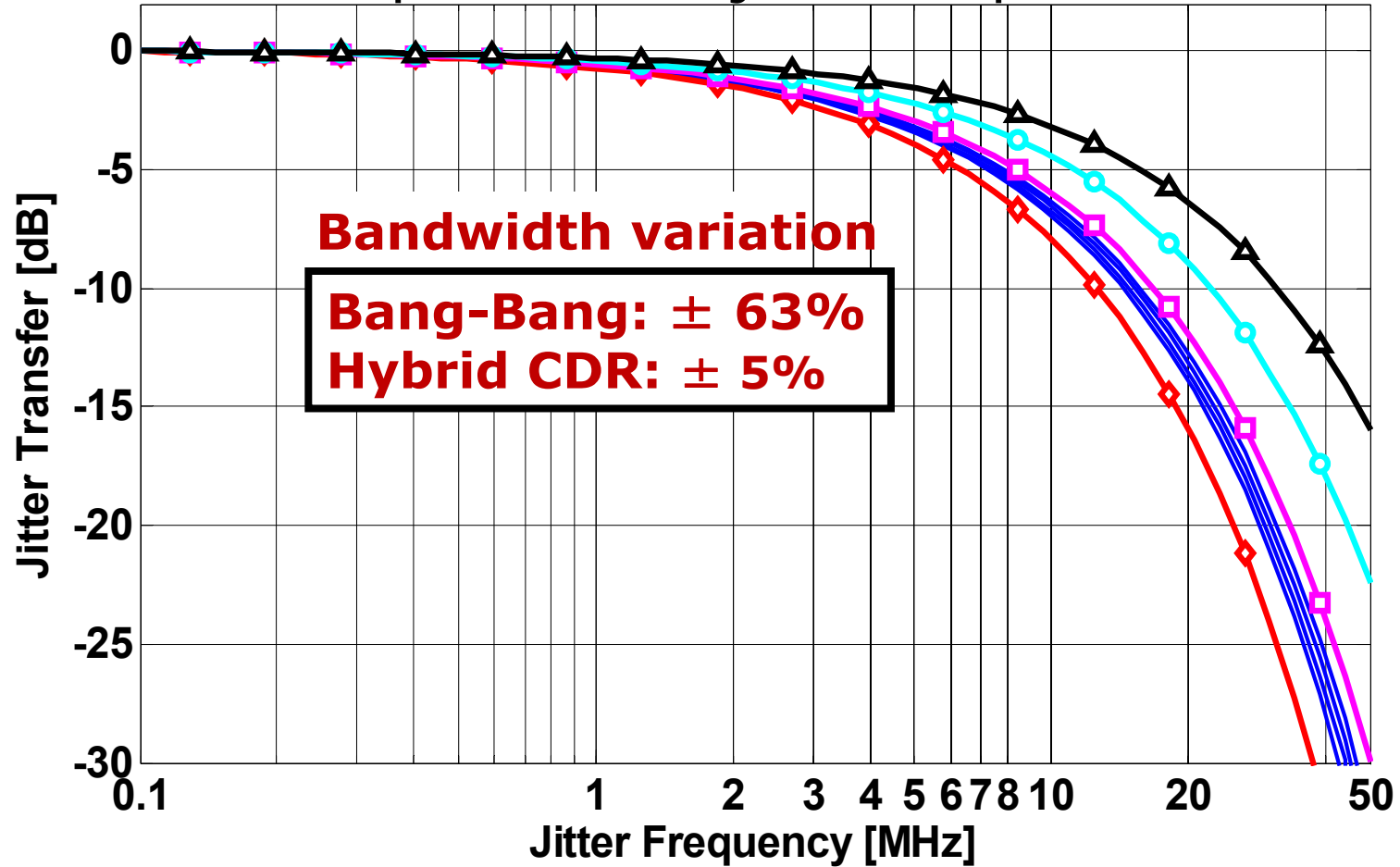

Tutorial Roadmap


- Performance metrics
 - Basic architectures
 - Linear/Bang-bang
 - Digital
 - Hybrid
 - **Application-specific CDRs**
 - **Multi-lane chip-to-chip links**
 - **Repeaters for optical links and active cables**
 - Summary
-

Multi-lane Chip-to-Chip Links

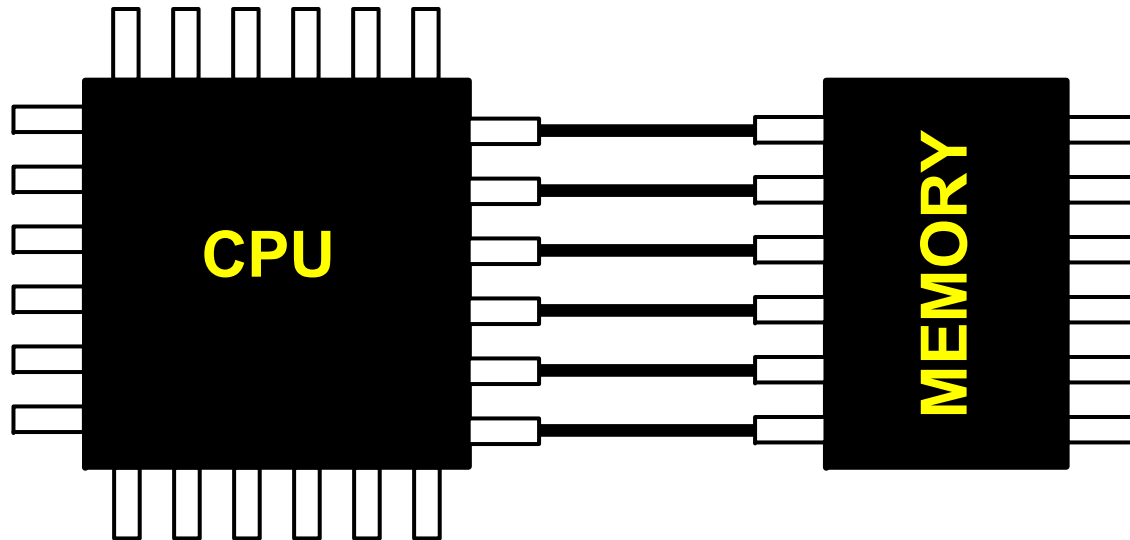

- ❑ Source synchronous clocking is common
clock forwarding
- ❑ BUT many standards mandate embedded clocking
 - Examples: PCIe, XAUI, SATA, etc.

Multi-Lane CDR Challenges

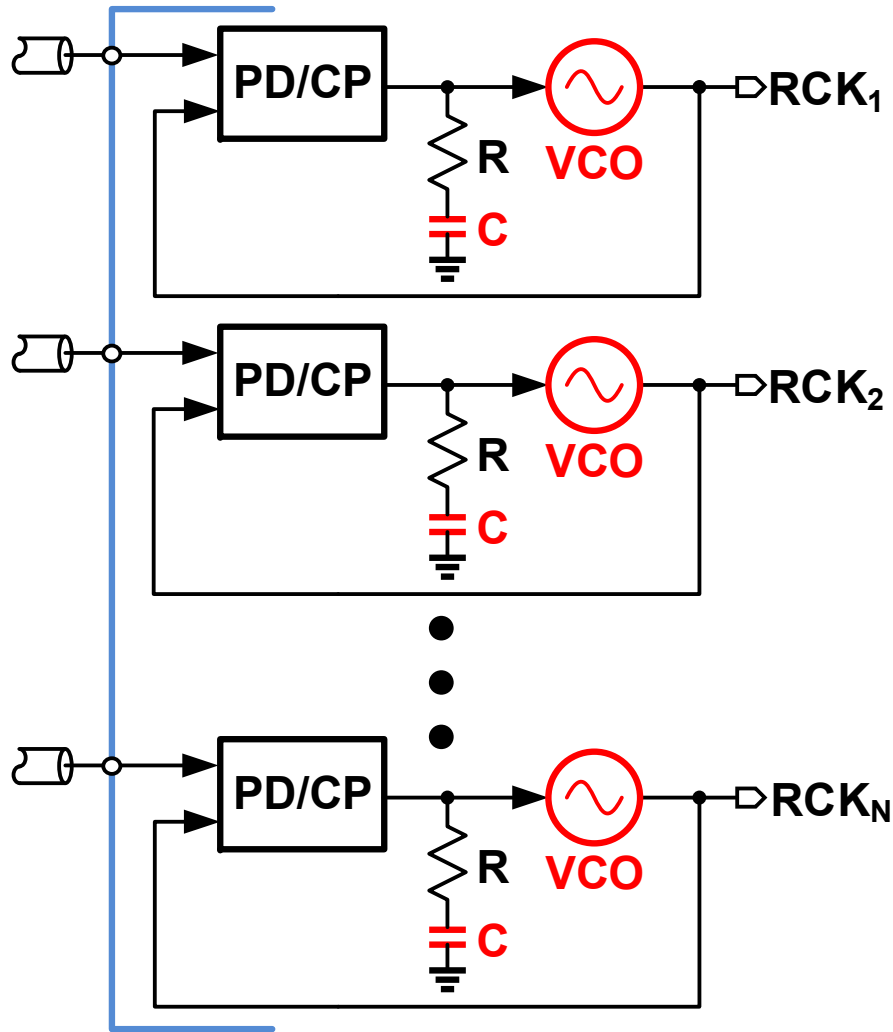


- Many VCOs & capacitors
- Large area
- Harmonic locking


Multi-Lane CDR Solution

Digital Phase Accumulator (DPA)

8-10 phases

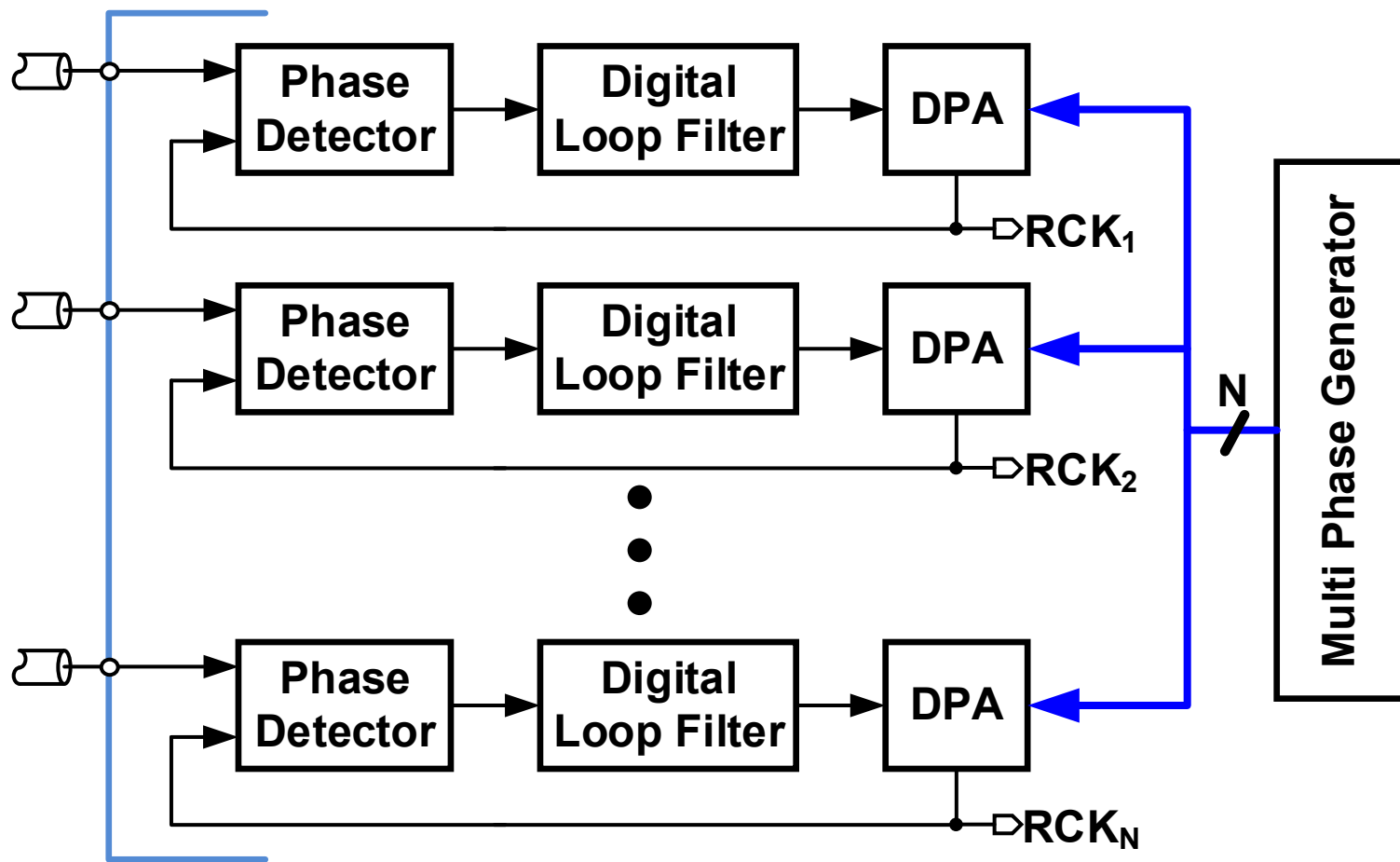


Digital Phase Accumulator (DPA)

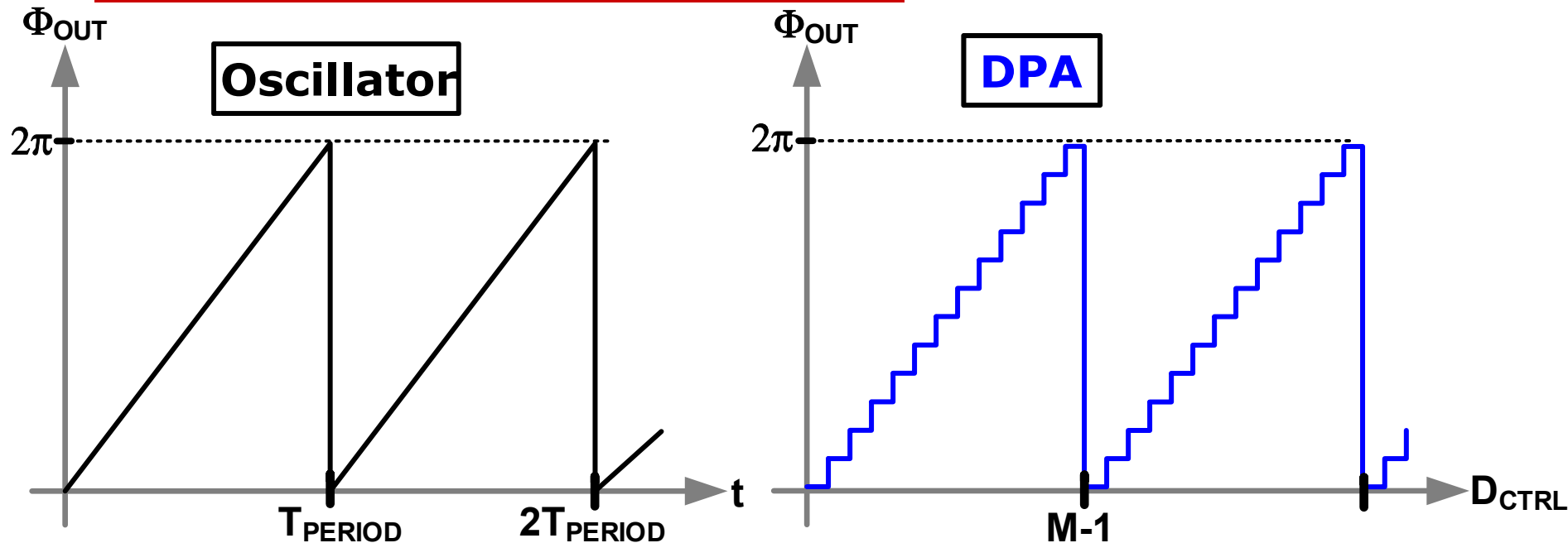


- ❑ Oscillators are phase accumulators
 - Modulo 2π accumulation
- ❑ Mimic oscillator operation
 - Explicit phase accumulation
 - Infinite phase shifting by modulo accumulation

Conceptual DPA Realization

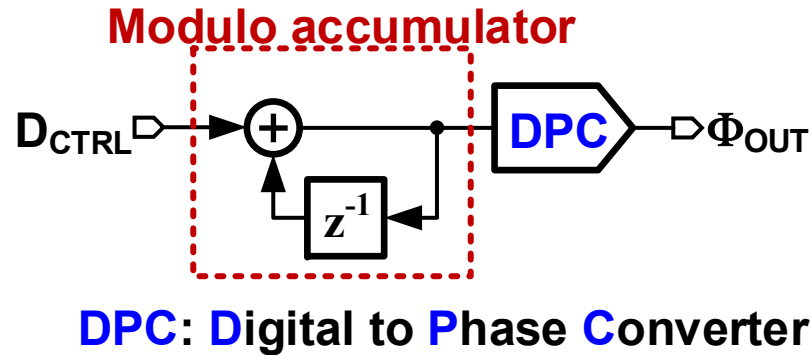

- Digital accumulator mimics phase accumulation
 - Rate governed by clock frequency
 - Modulo arithmetic maps 2π phase to 0
- DPC generates output phase
 - DPC non-idealities directly appear at the output

Practical DPA Realization

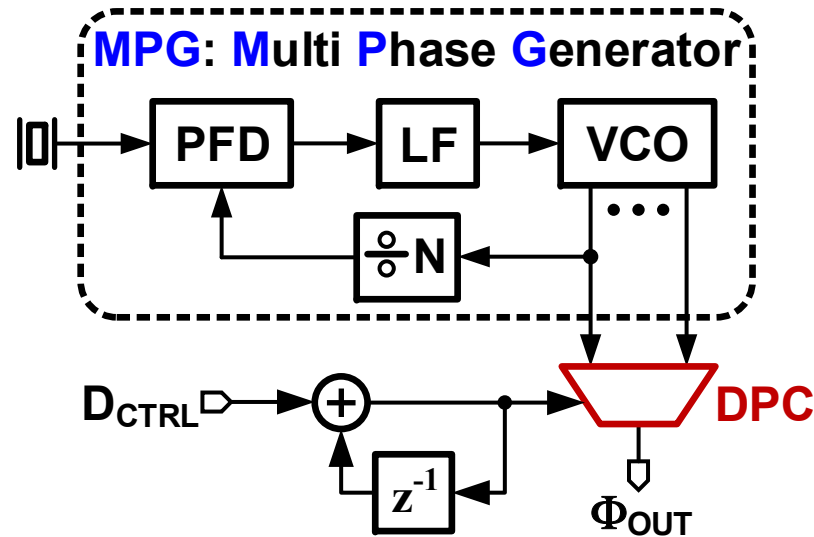


□ DPC implemented using a mux

$$\Phi_{OUT} = \Phi_{VCO} + D_{CTRL} \cdot K_{DPC}$$


$$\text{For M-phase VCO : } K_{DPC} = \frac{2\pi}{M}$$

Dual-Loop CDR^[9]

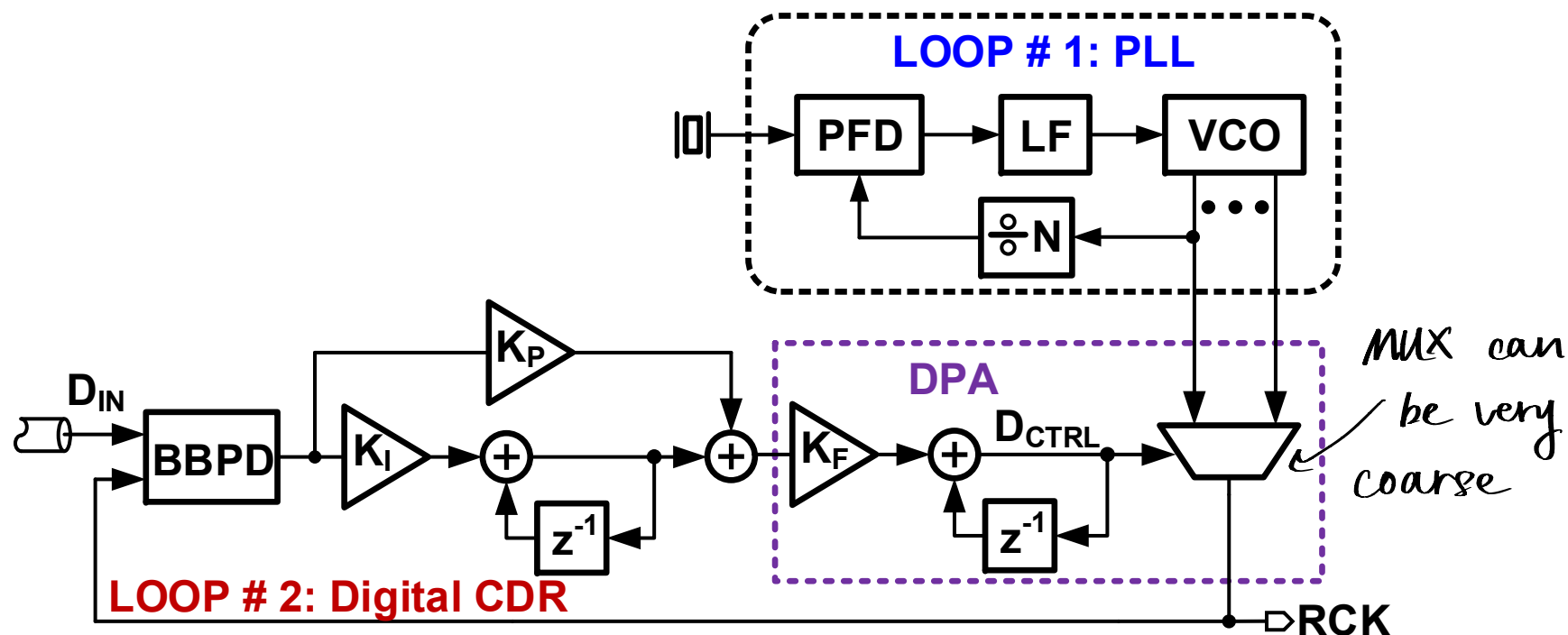



- ❑ Dual loop: Loop # 1: PLL(MPG), Loop # 2: CDR
- ❑ DPA replaces DCO in the CDR
- ❑ PLL guarantees frequency locking

Practical Dual-Loop CDR^[10]

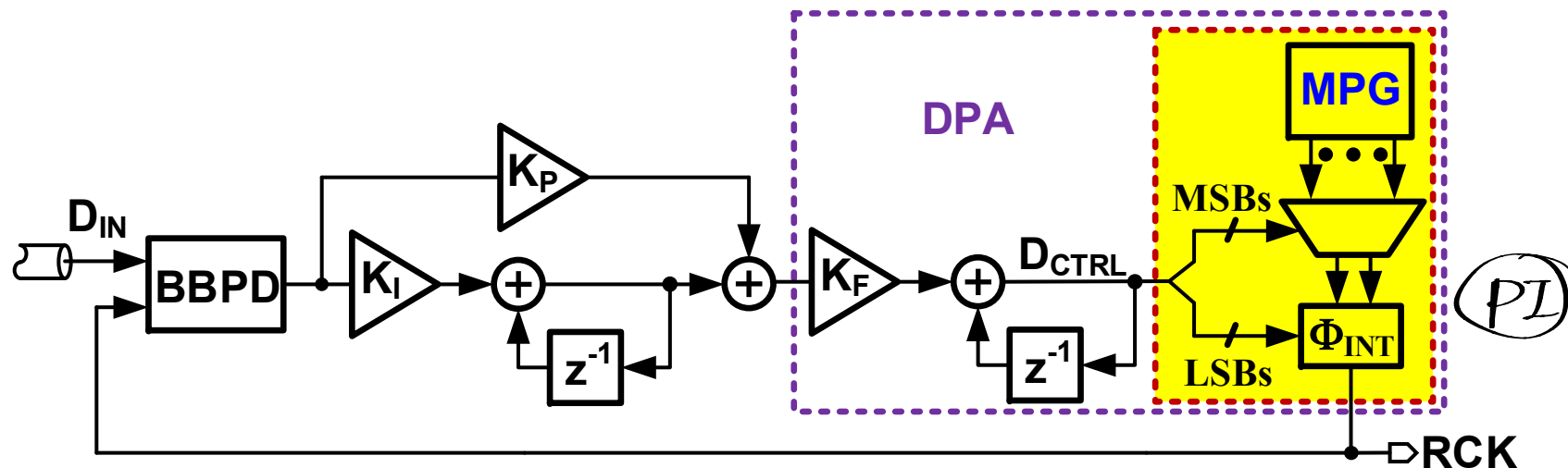




- ❑ Phase interpolator (Φ_{INT}) improves DPA resolution
 - Better JGEN
- ❑ PI resolution depends on many factors
 - Input rise time, input phase spacing, PI BW,...

Long-Haul Communication

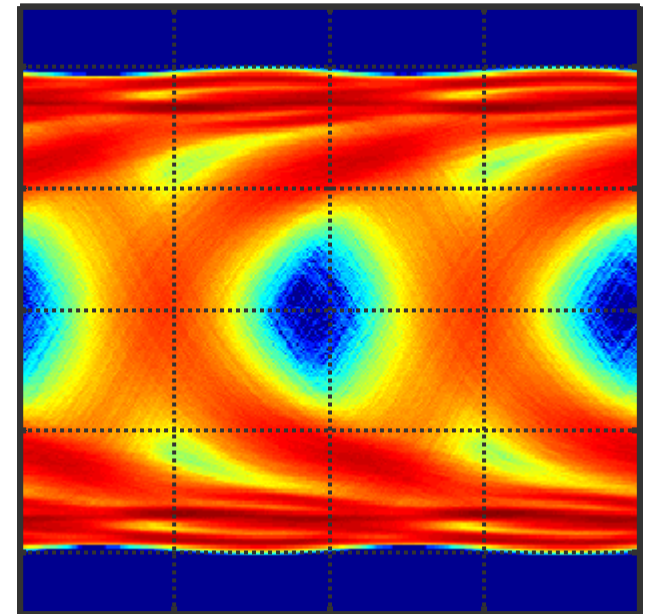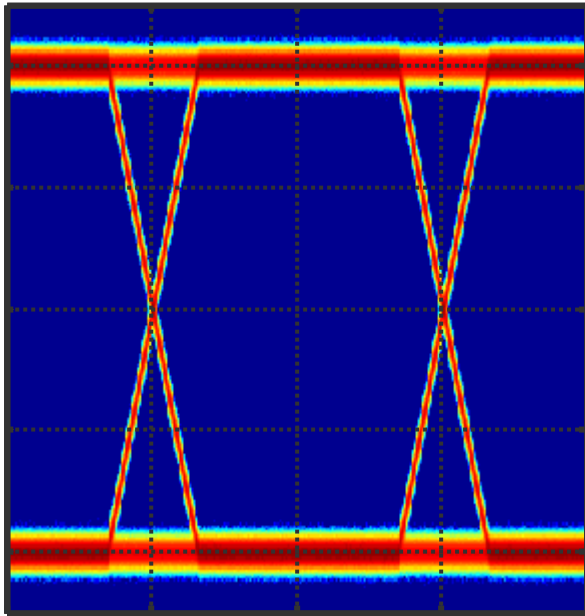

- Difficult to achieve error-free operation

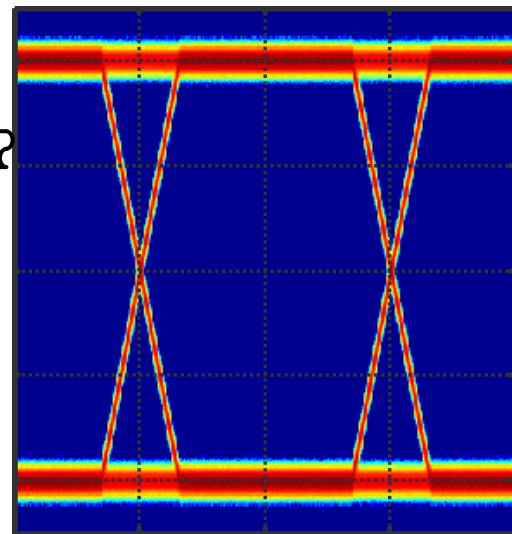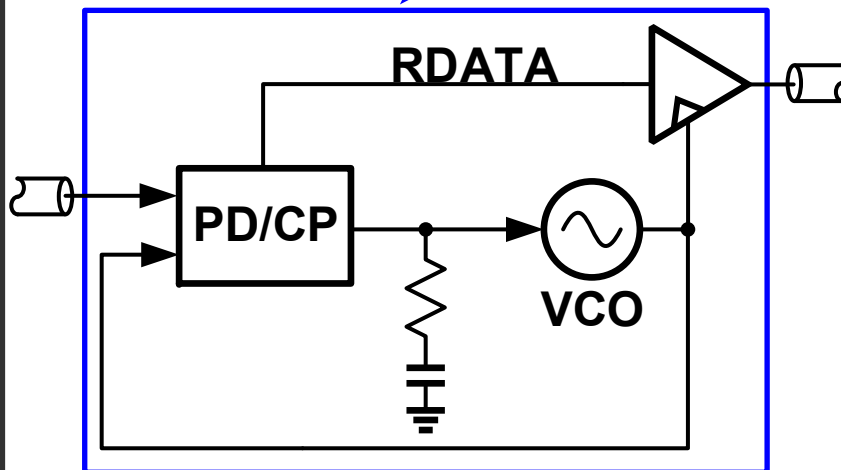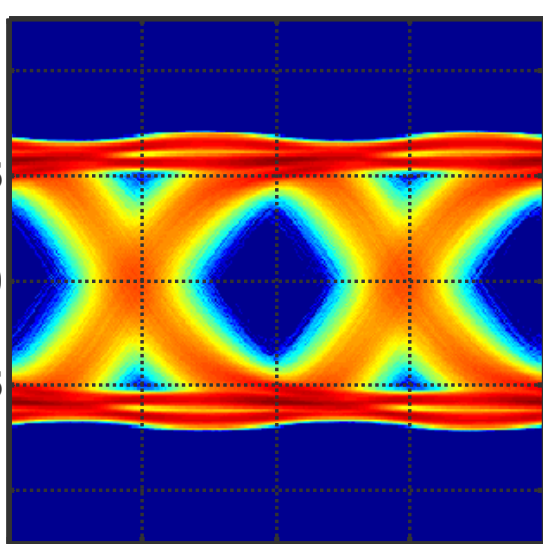
Active Repeaters *= receive, denoise, retransmit*



□ Repeater requirements

- Tolerate large input jitter (high JTOL)
- Filter input jitter (low JTRAN) w/ minimal peaking
- Re-transmit with low jitter (Low JGEN)


How About Conventional CDR?

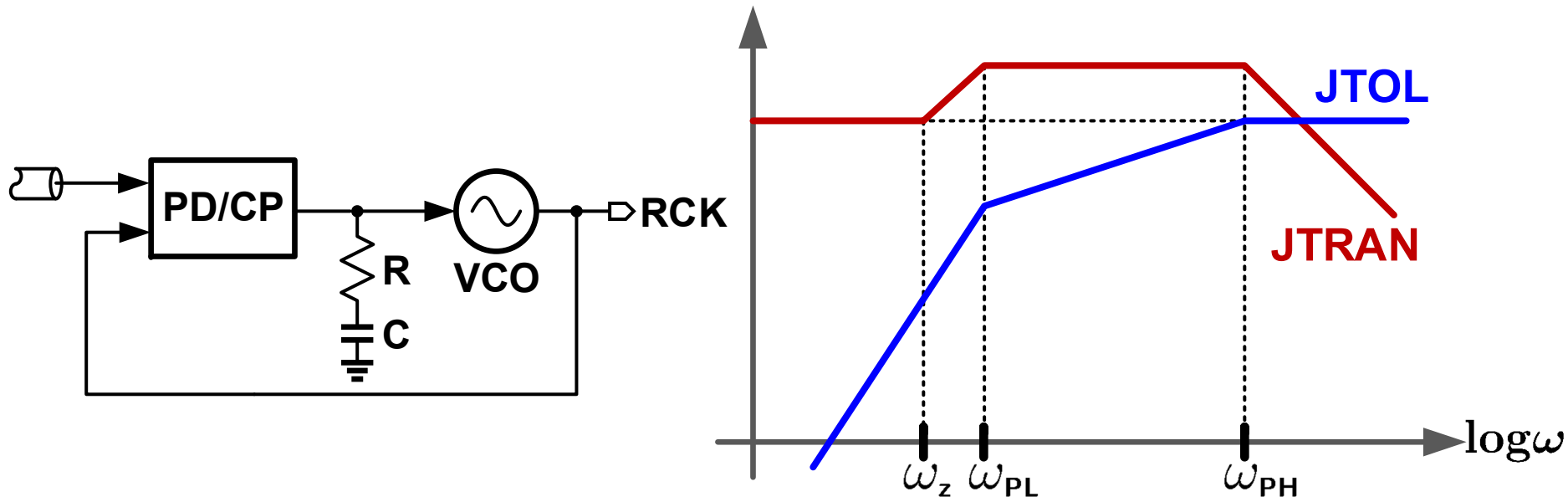


- ❑ Jitter peaking $\rightarrow$ large loop filter capacitor
small jitter peaking.
- ❑ High JTOL $\rightarrow$ high JTRAN *due to coupling*
 - Cannot adequately filter i/p jitter $\rightarrow$ degrades RCK jitter

How to Eliminate Jitter Peaking?

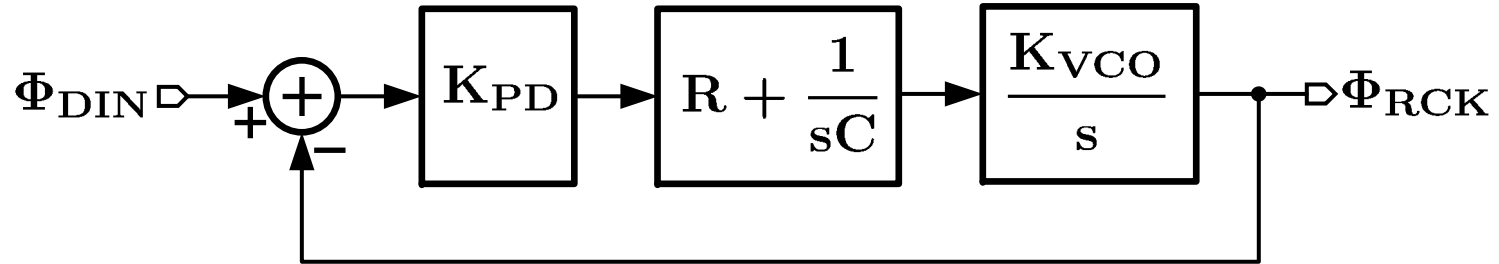- **Main idea:** Remove zero in feed-forward path





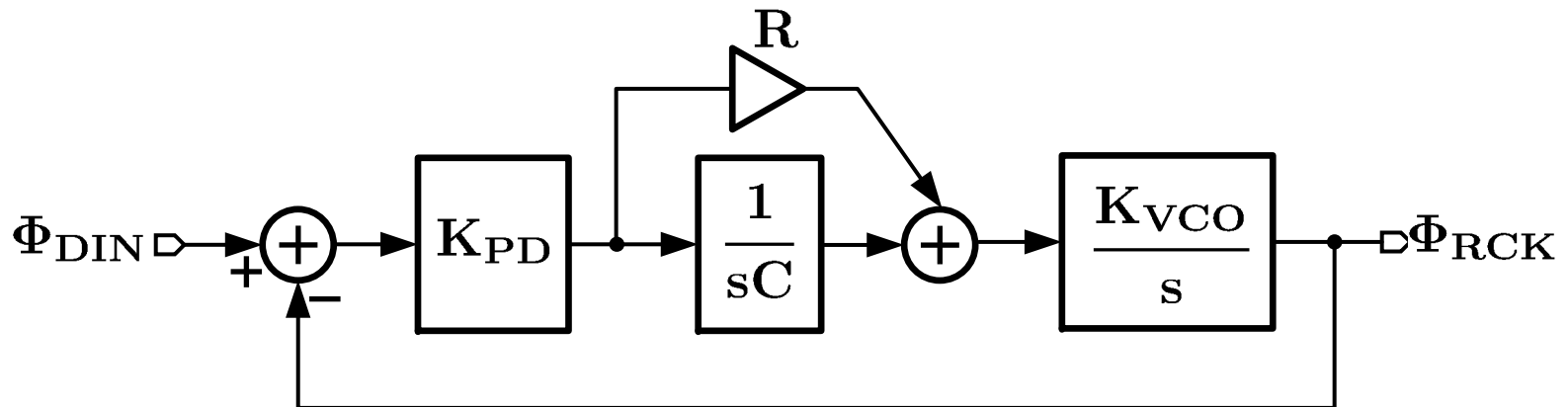Feed-forward across **current** integrator




Eliminate Jitter Peaking (I)^[11]

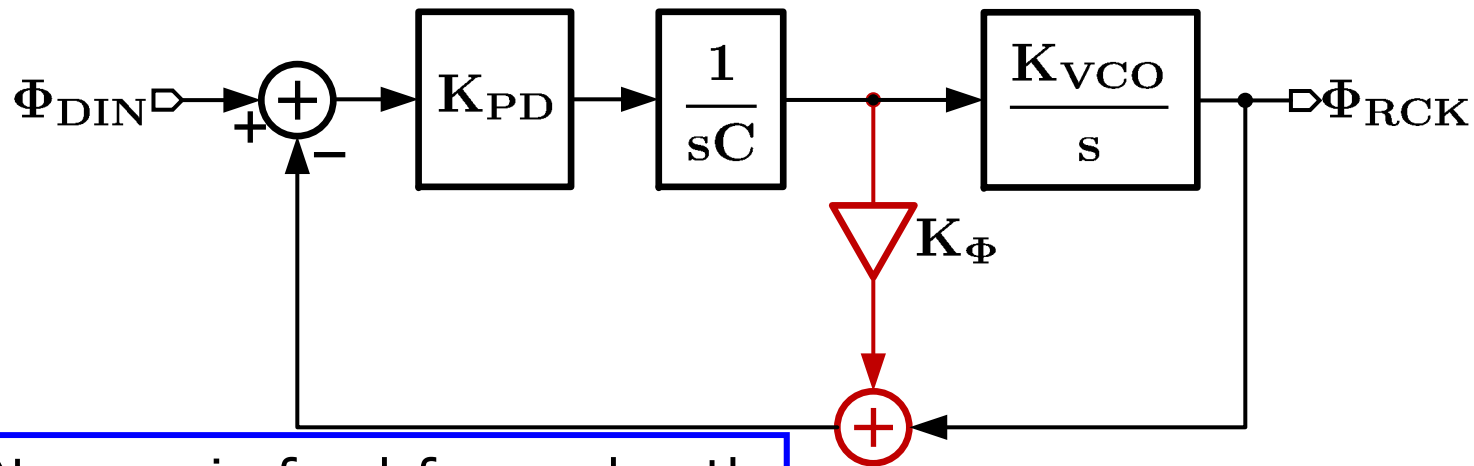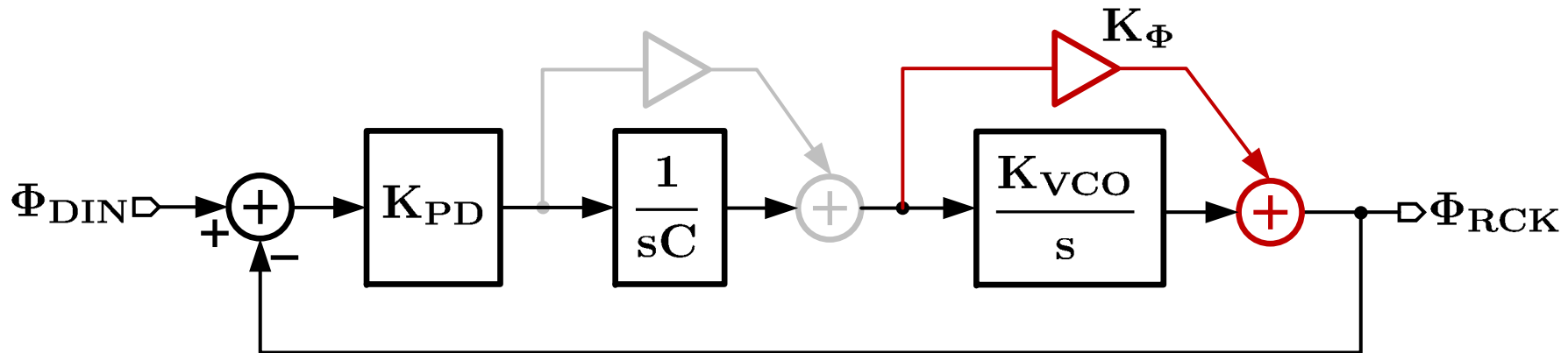Feed-forward across **phase** integrator (VCO)





No zero in feed-forward path


Eliminate Jitter Peaking (II)

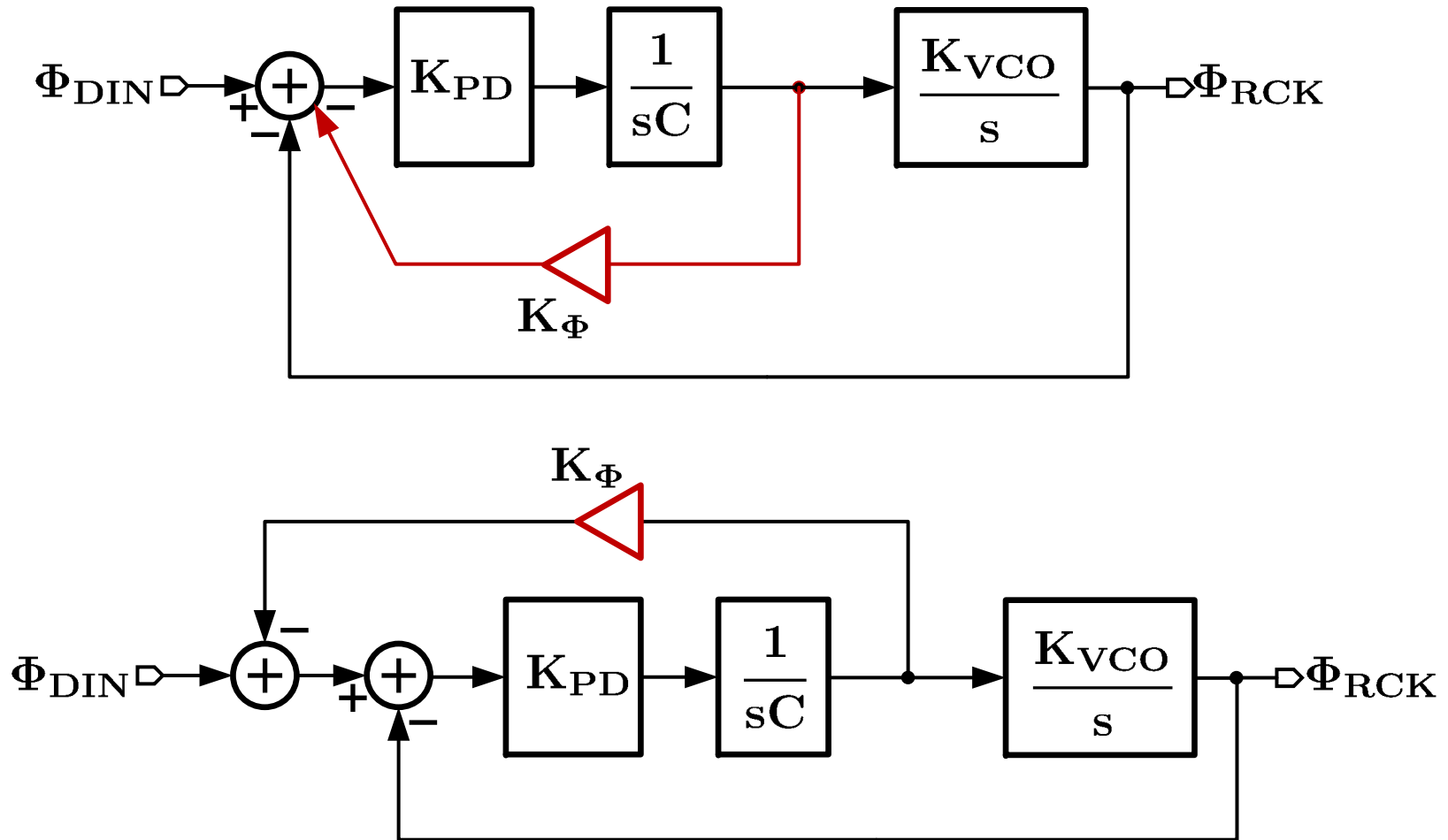

Country	Year	Value
Algeria	2010	0.0000
Algeria	2011	0.0000
Algeria	2012	0.0000
Algeria	2115	0.0000
Algeria	2116	

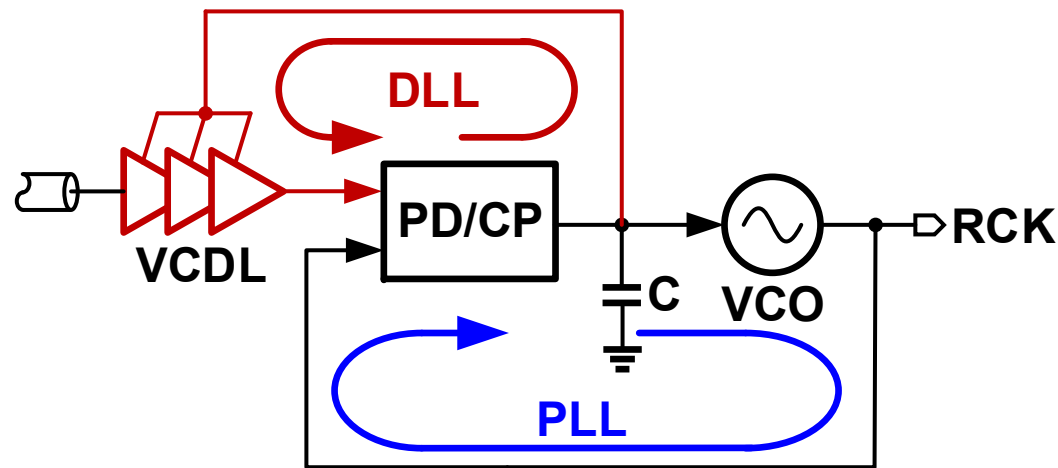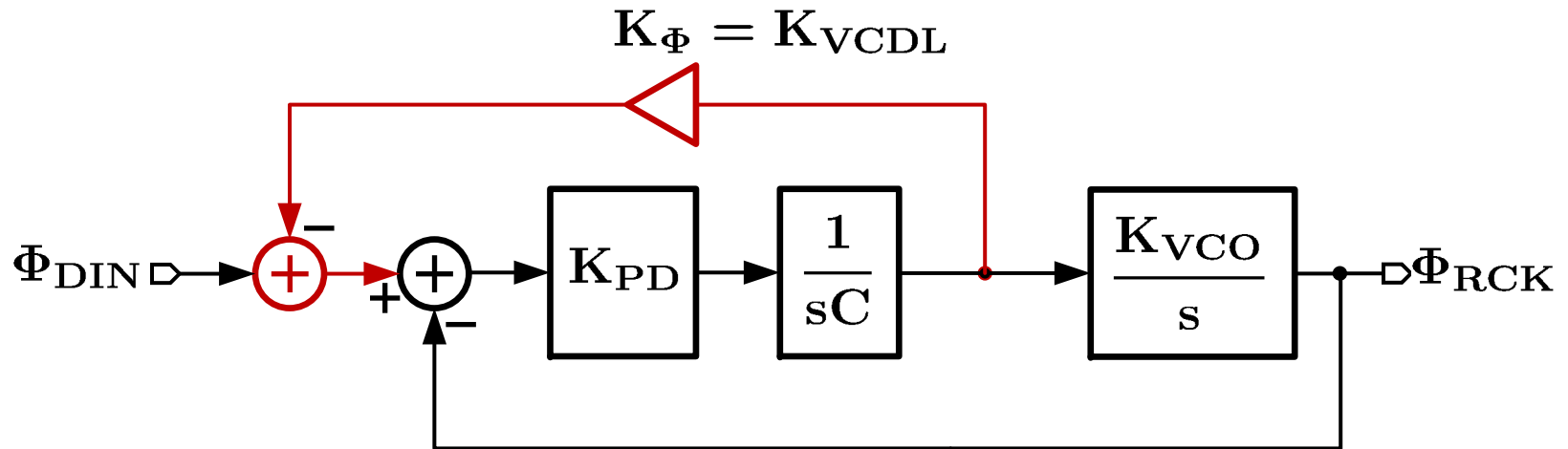

D/PLL CDR Jitter Transfer (I)

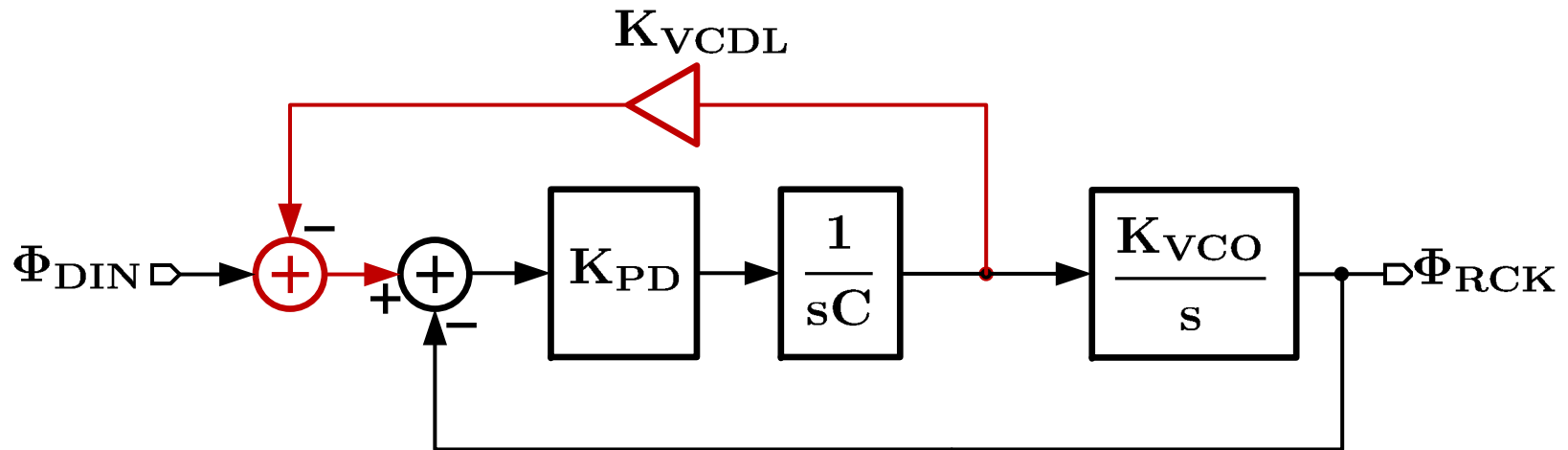

$$\mathbf{LG}_{\text{PLL}}(s) = K_{\text{PD}} \cdot \frac{1}{sC} \cdot \frac{K_{\text{VCO}}}{s}; \quad \mathbf{LG}_{\text{DLL}}(s) = K_{\text{PD}} \cdot \frac{1}{sC} \cdot K_{\text{VCDL}}$$

$$\begin{aligned} \mathbf{H}_{\text{JTRAN}}(s) &= \frac{\Phi_{\text{RCK}}(s)}{\Phi_{\text{DIN}}(s)} = \frac{\mathbf{LG}_{\text{PLL}}(s)}{1 + \mathbf{LG}_{\text{PLL}}(s) + \mathbf{LG}_{\text{DLL}}(s)} \\ &= \frac{1}{1 + s \cdot \frac{K_{\text{VCDL}}}{K_{\text{VCO}}} + s^2 \cdot \frac{C}{K_{\text{VCO}}K_{\text{PD}}}} \end{aligned}$$

no zero, no peaking if overdamped.

D/PLL CDR Jitter Transfer (II)


$$\mathbf{H}_{\text{JTRAN}}(\mathbf{s}) = \frac{1}{1 + \mathbf{s} \cdot \frac{\mathbf{K}_{\text{VCDL}}}{\mathbf{K}_{\text{VCO}}} + \mathbf{s}^2 \cdot \frac{\mathbf{C}}{\mathbf{K}_{\text{VCO}}\mathbf{K}_{\text{PD}}}} \equiv \frac{1}{(1 + \mathbf{s}/\omega_{\text{PL}})(1 + \mathbf{s}/\omega_{\text{PH}})}$$

$$\Rightarrow \omega_{\text{PL}} \approx \mathbf{K}_{\text{VCO}}/\mathbf{K}_{\text{VCDL}}; \omega_{\text{PH}} \approx \mathbf{K}_{\text{VCDL}} \cdot \mathbf{K}_{\text{PD}}/\mathbf{C}$$


$$\mathbf{JTRAN\ BW} = \omega_{-3\text{dB}} \approx \omega_{\text{PL}} = \mathbf{K}_{\text{VCO}}/\mathbf{K}_{\text{VCDL}}$$

□ No jitter peaking if damping factor > 0.707

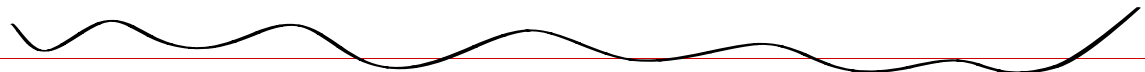□ JTRAN BW = lower of the 2 pole frequencies



D/PLL CDR Jitter Tolerance (I)

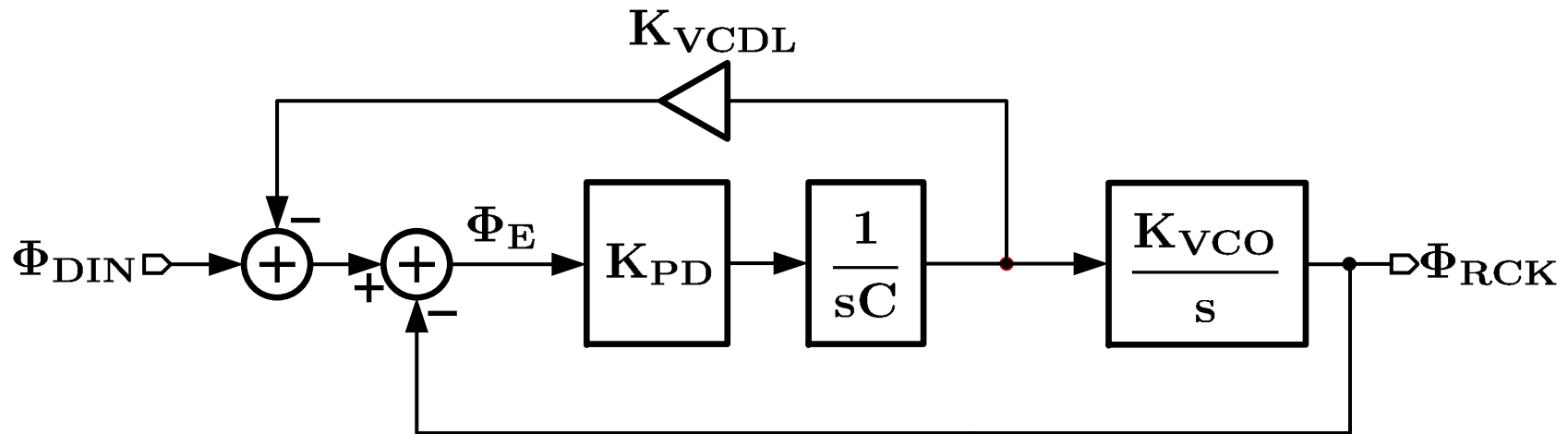

$$\begin{aligned}
 H_{JTRACK}(s) &= \frac{\Phi_E(s)}{\Phi_{DIN}(s)} = \frac{1}{1 + LG_1(s) + LG_2(s)} \\
 &= \frac{s^2 \cdot \frac{C}{K_{VCO}K_{PD}}}{1 + s \cdot \frac{K_{VCDL}}{K_{VCO}} + s^2 \cdot \frac{C}{K_{VCO}K_{PD}}} \\
 &\equiv \frac{s^2 / \omega_{PL}\omega_{PH}}{(1 + s/\omega_{PL})(1 + s/\omega_{PH})}
 \end{aligned}$$

D/PLL CDR Jitter Tolerance (II)


$$\mathbf{H}_{\text{JTRACK}}(s) = \frac{s^2 \cdot \frac{C}{K_{\text{VCO}}K_{\text{PD}}}}{1 + s \cdot \frac{K_{\text{VCDL}}}{K_{\text{VCO}}} + s^2 \cdot \frac{C}{K_{\text{VCO}}K_{\text{PD}}}} \equiv \frac{s^2 / \omega_{\text{PL}}\omega_{\text{PH}}}{(1 + s/\omega_{\text{PL}})(1 + s/\omega_{\text{PH}})}$$
$$\implies \omega_{\text{PL}} \approx K_{\text{VCO}}/K_{\text{VCDL}}; \omega_{\text{PH}} \approx K_{\text{VCDL}} \cdot K_{\text{PD}}/C$$

$$\text{JTRACK/JTOL Corner} = \omega_{-3\text{dB}} \approx \omega_{\text{PH}} \approx K_{\text{VCDL}} \cdot K_{\text{PD}}/C$$

□ JTOL corner = **higher** of the 2 pole frequencies




D/PLL CDR JTRAN vs. JTOL

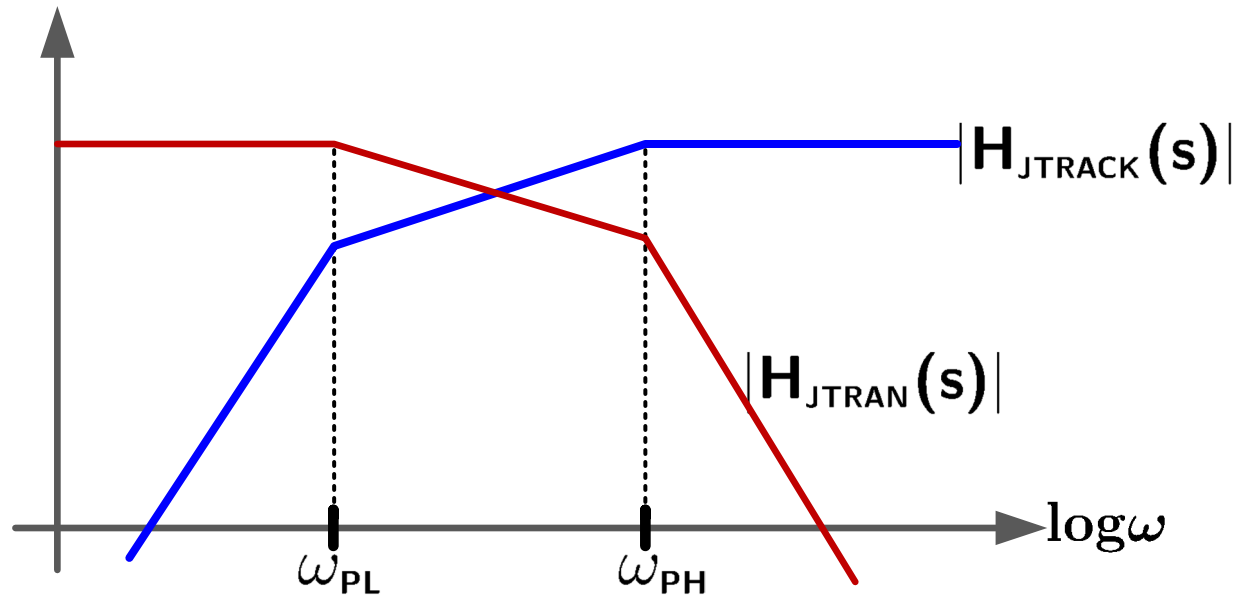

□ Decoupled JTRAN and JTOL


- ω_{PL} sets JTRAN BW
- ω_{PH} sets JTOL corner frequency

A Practical D/PLL CDR

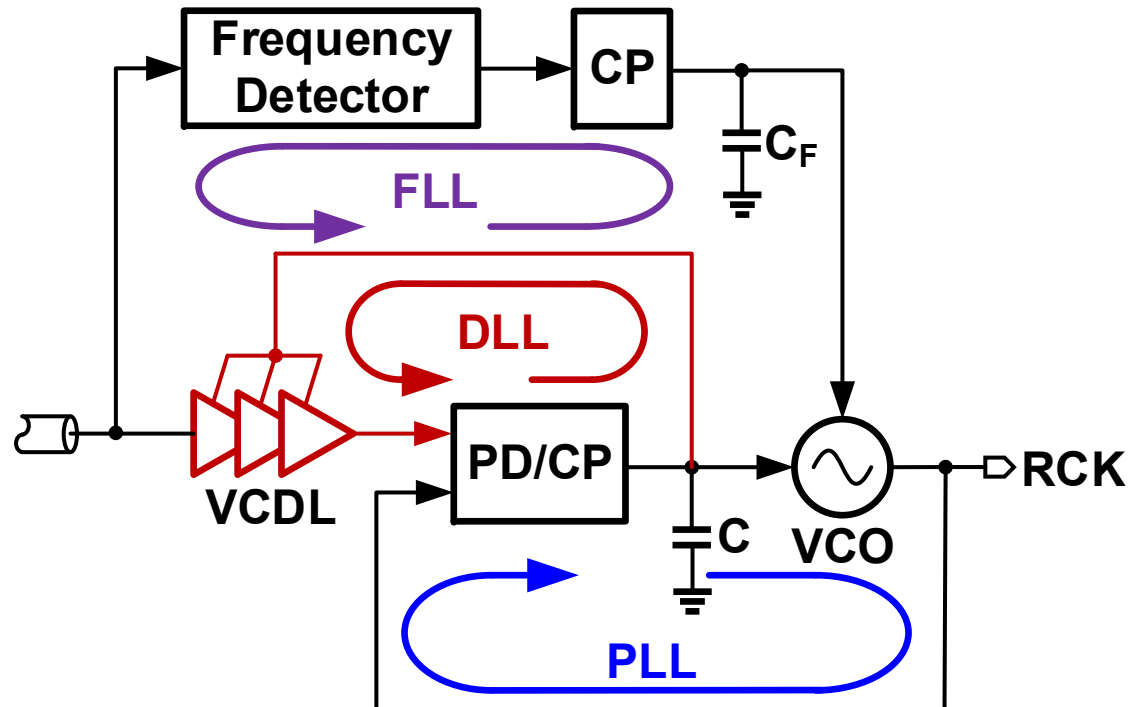

- Additional frequency-locking loop (FLL)
- Challenges:
 - Frequency detection of random data
 - Interaction between FLL and PLL

Limited Capture Range

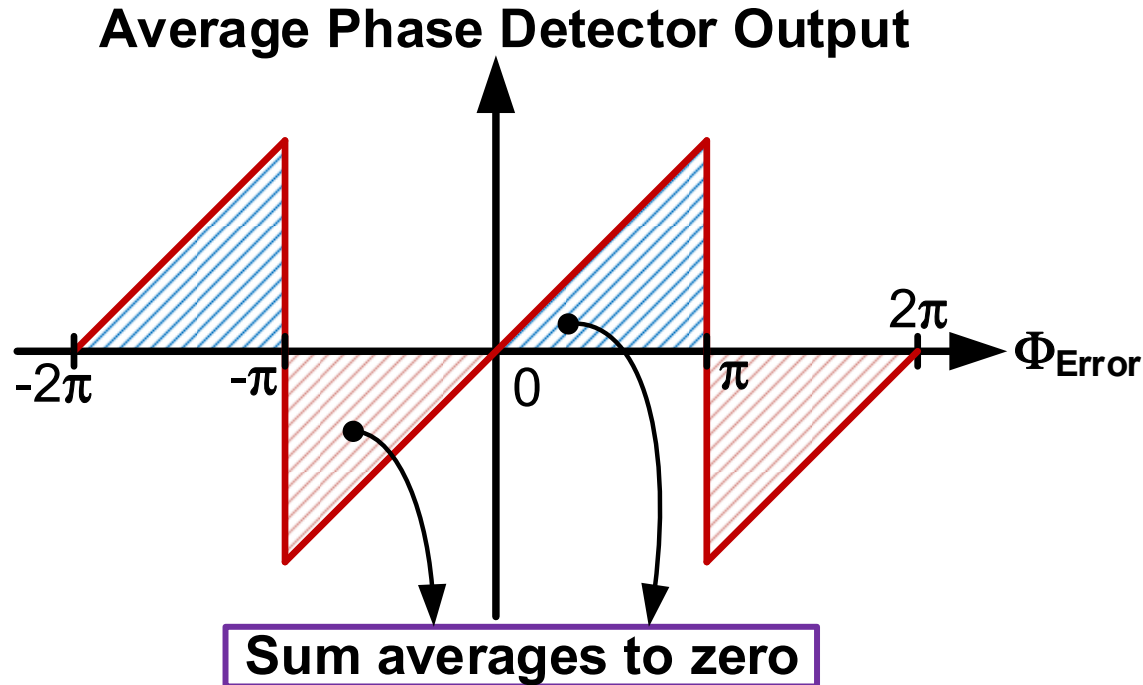


- Symmetric PD transfer characteristic
- Avg. PD output becomes zero w/ frequency error
 - PD cannot detect large frequency error

Frequency Detectors

- Rotational frequency detector^[12-14]
- Quadri-correlator frequency detector^[15-16]
- Stochastic reference clock generator^[17]
- Miscellaneous FDs
 - Strobed linear PD^[18]
 - Counting BBPD outputs ^[19]

Summary

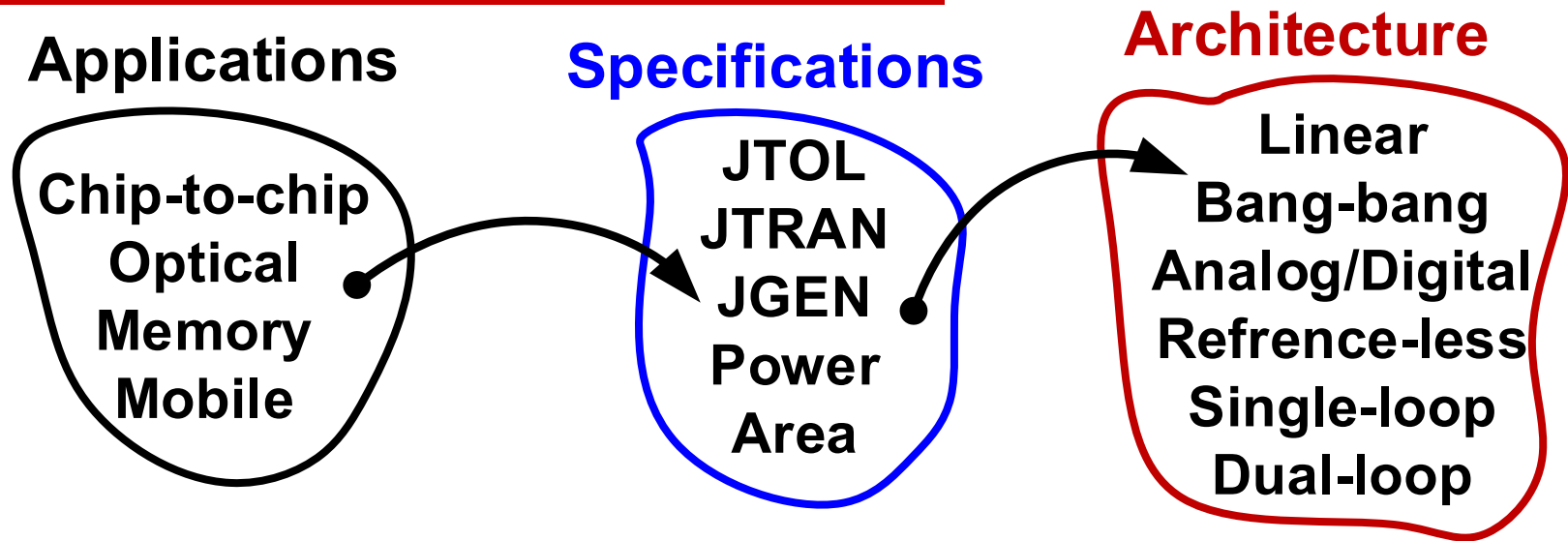

- Understanding of CDR specifications
 - What are the important jitter metrics for a given app.?
- Understanding of CDR architectures
 - What is the best architecture for a given app.?
- CDR design techniques
 - How to choose the loop parameters?

Selected References (I)

1. C. Hogge, "A self correcting clock recovery circuit," *J. Lightwave Technol.*, pp. 1312-1314, Dec. 1985.
2. L. DeVito, "A versatile clock recovery architecture and monolithic implementation," in *Monolithic Phase-Locked Loops and Clock Recovery Circuits*, B. Razavi, Ed. Wiley-IEEE Press, 1996, pp. 405-420.
3. J. Alexander, "Clock recovery from random binary signals," *Electr. Lett.*, pp. 541-542, Oct. 1975.
4. J. Lee and B. Razavi, "Analysis and modeling of bang-bang clock and data recovery circuits," *IEEE J. Solid-State Circuits*, pp. 1571-1580, Sep. 2004.
5. R. Walker, et al., "A 2-Chip 1.5 Gigabaud serial link interface," *IEEE J. Solid-State Circuits*, pp. 1805-1811, Dec. 1992.
6. J. Sonntag and J. Stonick "A digital clock and data recovery architecture for multi-gigabit/s binary links", *IEEE J. Solid-State Circuits*, pp.1867-1875, Aug. 2006.

Selected References (II)

7. M. Talegaonkar, R. Inti, P. Hanumolu, "Digital clock and data recovery circuit design: Challenges and tradeoffs", *IEEE Custom Integrated Circuits Conference*, 2011.
8. W. Yin, R. Inti, A. Elshazly, and P. Hanumolu, "A TDC-less 7mW 2.5Gb/s digital CDR with linear loop dynamics and offset-free data recovery," in *ISSCC Dig. Tech. Papers*, pp. 440-442, Feb. 2011.
9. J. Sonntag and R. Leonowich "A monolithic CMOS 10 MHz DPLL for burst-mode data retiming", *IEEE ISSCC Dig. Tech. Papers*, pp.194 -195, Feb. 1990
10. S. Sidiropoulos and M. Horowitz, "A semidigital dual delay-locked loop," *IEEE J. Solid-State Circuits*, 1683–1692, 1997.
11. T. Lee and J. Bulzacchelli, "A 155-MHz clock recovery delay-and phase-locked loop," *IEEE J. Solid-State Circuits*, pp. 1736-1746, Dec. 1992.

Freq. Detector References (I)

12. D. Richman, "Color-Carrier Reference Phase Synchronization Accuracy in NTSC Color Television," Proceedings of the IRE, vol. 42, no.1, pp.106-133, Jan. 1954.
13. A. Pottbacker, et al., "A Si bipolar phase and frequency detector IC for clock extraction up to 8 Gb/s," *IEEE J. Solid-State Circuits*, pp.1747,1751, Dec 1992
14. D. Dalton, et al., "A 12.5-Mb/s to 2.7-Gb/s continuous-rate CDR with automatic frequency acquisition and data-rate readback," *IEEE J. Solid-State Circuits*, pp. 2713–2725, Dec. 2005.
15. F. M. Gardner, "Properties of frequency difference detectors," *IEEE Trans. Comm.*, vol. COM-36, no. 2, pp. 131–138, Feb. 1985.
16. N. Kocaman, et al., "An 8.5–11.5-Gbps SONET transceiver With reference-less frequency acquisition," *IEEE J. Solid-State Circuits*, pp. 1875–1884, Aug. 2013.

Freq. Detector References (I)

17. R. Inti, et al., "A 0.5-to-2.5 Gb/s reference-less half-rate digital CDR with unlimited frequency acquisition range and improved input duty-cycle error tolerance," *IEEE J. Solid-State Circuits*, pp. 3150–3162, Dec. 2011.
18. S. Huang, et al., "An 8.2-to-10.3 Gb/s full-rate linear reference-less CDR without frequency detector in 0.18 μ m CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb 2014, pp. 152–153.
19. G. Shu, et al., "A 4-to-10.5 Gb/s 2.2 mW/Gb/s continuous-rate digital CDR with automatic frequency acquisition in 65 nm CMOS," in *IEEE ISSCC Dig. Tech. Papers*, Feb 2014, pp. 150–151.

Related ISSCC 2015 Papers

- Papers 22.7 & 22.8: Reference-less CDRs for beyond 25Gb/s optical links
- 22.1 & 3.7: Fast locking CDR for burst-mode applications
- 3.1: Quarter-rate dual loop CDR
- 10.5: Baud-rate CDR

Acknowledgements

- Jack Kenney, Ali Sheikholeslami, Guanghua Shu, and Mrunmay Talegoankar for reviewing and providing detailed feedback
- Ajith Amarasekara and Ali Sheikholeslami for coordination
- Seong-Joong Kim for assistance with preparation